

Reg. No. :

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Question Paper Code : 23501

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2018.

Fourth Semester

Electrical and Electronics Engineering

EE 2254 — LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

(Common to Instrumentation and Control Engineering and Electronics and Instrumentation Engineering)

(Regulations 2008)

(Also common to PTEE 2254 – Linear Integrated Circuits and Applications for B.E. (Part-Time) Third Semester – EEE – Regulations 2009)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. List advantages of IC's over discrete components.
2. State why buried layer is needed.
3. Mention the ideal characteristics of an operational amplifier.
4. For the opamp shown in Fig. 4 determine the voltage gain.

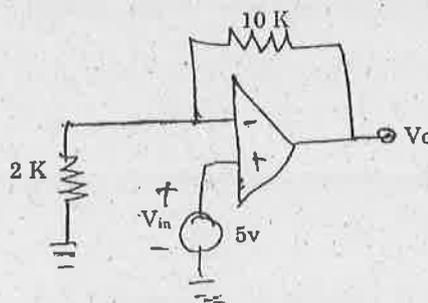


Fig. 4

5. Give any four important features of an instrumentation amplifier.
6. Write down the advantages of Flash type A/D converters.
7. Why invariably a suitable value of capacitor is connected to the pin 5 of 555 Timer applications?

8. Draw the block diagrammatic representation of a frequency multiplier using PLL.
9. What is the principle of switch mode power supplies?
10. How many resistors are required in a 12-bit weighted resistor DAC?

PART B — (5 × 16 = 80 marks)

11. (a) Explain about the following:
- (i) Epitaxial growth and diffusion. (8)
 - (ii) Photolithography masking and Photo etching. (8)

Or

- (b) Discuss briefly about the fabrication methods for transistors and diodes. (16)
12. (a) List the six characteristics of an ideal op-amp and explain in detail. Give the practical op-amp equivalent circuit.

Or

- (b) Explain in detail about DC characteristics of op-amp.
13. (a) (i) Illustrate the working principle of dual slope type A/D converter. What are the advantages and limitations? (10)
- (ii) Design a second order Butterworth HPF with cut-off frequency of 4 KHz and draw the designed circuit. (6)

Or

- (b) (i) Explain a R-2R ladder type D/A converter, (12)
- (ii) State the advantages and applications of sample and hold circuits. (4)
14. (a) (i) Draw the functional block diagram and explain the Characteristics of IC 555. (12)
- (ii) Write a short note on Analog multiplier. (4)

Or

- (b) (i) Explain the functioning of IC 566 as a PLL. (12)
- (ii) Explain the application of PLL as a frequency translator. (4)

15. (a) Design a Voltage regulator using IC 723 regulator to satisfy the following specifications
- (i) $V_o = 12\text{ V}$,
 - (ii) $I_o = 500\text{ mA}$,
 - (iii) $V_{in} = 18 \pm 20\%$,
 - (iv) $I_{sc} = 600\text{ mA}$,
 - (v) $V_{sense} \approx 0.7\text{ V}$. Give the complete schematic diagram. (Assume and Justify if any data required).

Or

- (b) Discuss in detail the operation and applications of the following circuits.
- (i) Isolation amplifier. (8)
 - (ii) Optocoupler. (8)

