

PART B — (5 × 16 = 80 marks)

11. (a) Simply using Quine McCluskey method and verify your result using K-map $F = \Sigma(0,1,2,5,7,8,9,10,13,15)$. (16)

Or

- (b) (i) Express the Boolean functions $F = A + \overline{B}C$ in a sum of minterms. (10)
- (ii) Simplify the following Boolean expression using Boolean algebra.
- (1) $\overline{x} \overline{y} z + \overline{x} y z + x \overline{y}$ (3)
- (2) $x y z + \overline{x} z + y z$. (3)
12. (a) (i) Design a 4*1 multiplexer circuit. (8)
- (ii) Implement the function using multiplexer $F = \Sigma(0,1,3,4,8,9,15)$. (8)

Or

- (b) (i) Draw the logic diagram of Binary to octal decoder and explain the working in detail. (8)
- (ii) How is the carry look ahead adder faster than a ripple carry adder? Explain in detail with neat sketches. (8)
13. (a) Using D flipflops design a synchronous counter which counts in the sequence. 000, 001, 010, 011, 100, 101, 110, 111, 000. (16)

Or

- (b) (i) Discuss the working of a 4 bit Johnson counter with neat block diagram. (8)
- (ii) Explain the functioning of a recirculating shift register with various modes of operation. (8)
14. (a) (i) Explain memory decoding. Compare the RAM, ROM, PROM & EPROM. (8)
- (ii) Draw a RAM Cell and explain its working in detail. (8)

Or

- (b) Write short notes on with suitable schematic (16)
- (i) Programmable Logic Array (PLA).
- (ii) Field Programmable Gate Arrays (FPGA).
15. (a) (i) Explain how a state graph for a sequential machine can be converted to an equivalent ASM chart. (8)
- (ii) Derive the ASM chart for binary multiplier. (8)

Or

- (b) (i) When is a sequential machine said to be strongly connected. (2)
- (ii) Design a sequential pattern detector that receives a stream of input bits. The circuit should recognize the pattern 010 and produce an output whenever this pattern is received. (14)