

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 41029**

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2024.

Third Semester

Electrical and Electronics Engineering

EE 3302 — DIGITAL LOGIC CIRCUITS

(Regulations 2021)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define Propagation Delay.
2. Show  $(377)_{10}$  in Octal and Hexa-Decimal equivalent.
3. Simplify the Expression  $Z = AB' + AB(A'C)'$ .
4. What is K-map?
5. What is flip-flop?
6. Differentiate Mealy and Moore models.
7. What is Static Hazard and Dynamic Hazard?
8. State the difference between Static 0 and Static 1 Hazard.
9. Expand the following acronyms.
  - (a) VHDL
  - (b) VHLSI.
10. What is sequential circuit?

PART B — (5 × 13 = 65 marks)

11. (a) (i) Explain the numbering system in detail. (7)  
(ii) Encode the Binary Word 1011 into Seven Bit Even Parity Hamming Code. (6)

Or

- (b) (i) Explain hamming code with an example. State its advantage over parity codes. (7)  
(ii) Design a TTL logic circuit for a 3 input NAND gate. (6)
12. (a) (i) Draw the logic diagram of a 4 bit carry look ahead adder and explain how this adder is advantageous over the ripple carry adder. (7)  
(ii) Explain with the suitable example how a multiplexer is used to implement the Boolean function. (6)

Or

- (b) (i) With Block Diagram, Explain the Full Subtractor in detail with logic diagrams. (7)  
(ii) Design a Full Adder using two half adders and an OR gate. (6)
13. (a) (i) Explain the operation of Master-Slave JK flipflop in detail. (7)  
(ii) Design a 5-bit ring counter and explain with its logic diagrams. (6)

Or

- (b) Illustrate with Appropriate Truth Tables and Equations the 4-bit BCD ripple counters.
14. (a) Explain the various types of hazards in sequential circuit design and the methods to eliminate them. Give suitable examples.

Or

- (b) (i) Find a circuit that has no static hazards and implement Boolean function  $F(A, B, C, D) = \sum(0, 2, 6, 7, 8, 10, 12)$ . (7)  
(ii) Explain the different types of programmable logic devices with neat sketch and compare them. (6)

15. (a) Design a 3-bit Magnitude Comparator and Write the VHDL coding to realize it using Structural Modelling.

Or

- (b) (i) Explain in detail the various programming constructs used in VHDL for designing a logic circuit. (7)  
(ii) Discuss the various packages. Write a VHDL code for the implementation of Decoder/De-Multiplexer. (6)

PART C — (1 × 15 = 15 marks)

16. (a) Design a CMOS inverter and explain its operation. Comment on its characteristics such as Fan-in, Fan-out power dissipation, propagation delay and noise margin. Compare its advantages over other logic families.

Or

- (b) Explain in detail with neat illustrations, Design a Full Adder using 4×1 multiplexer; also write its truth table and logical diagram.
-