

- 1) A 100 kVA, 3300V / 240V, 50 Hz, single phase transformer has 400 turns on the primary. calculate the number of turns on the secondary and the approximate value of primary and secondary full load currents.

Data : 100 kVA ,  $E_1 = 3300 \text{ V}$ ,  $E_2 = 240 \text{ V}$  ,  $N_1 = 990$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \Rightarrow \frac{3300}{240} = \frac{990}{N_2} \Rightarrow N_2 = 72$$

$$T_{\text{FL}} = \frac{V_A}{E_1} = \frac{100 \times 10^3}{3300} = 30.303 \text{ A}$$

$$I_2 (\text{FL}) = \frac{V_A}{E_2} = \frac{100 \times 10^3}{240} = 416.67 \text{ A}$$

- 2) The b.m.f per turn of a single-phase, 6.6 kV, 440 V, 50 Hz transformer is approximately 120 u. calculate number of turns in the HV and LV windings and the net cross-sectional area of the core for a maximum flux density of 1.5 T.

Data :  $E_1 = 6.6 \text{ kV}$ ,  $E_2 = 440 \text{ V}$ ,  $f = 50 \text{ Hz}$ , el tension = 120 V,

$$B_m = 1.5 \text{ T}$$

$$E_1 = \left[ \frac{\text{e.m.f}}{\text{turn}} \right] \times N_1 \Rightarrow 6.6 \times 10^3 = 12 N_1 \Rightarrow N_1 = 550$$

Turns on HV side

$$E_2 = \left[ \frac{\text{e.m.f}}{\text{turn}} \right] \times N_2 \Rightarrow 440 = 12 N_2 \Rightarrow N_2 = 36.66 \approx 37$$

Turns on LV side

$$E_1 = 1.44 \Phi m f N_1$$

$$6.6 \times 10^3 = 1.44 \times \Phi m \times 50 \times 550$$

$$\Phi m = 0.054 \text{ wb}$$

$$B_m = \frac{\Phi m}{A}$$

$$1 = \frac{\Phi m}{B_m} = \frac{0.054}{1.5} = 0.036 \text{ Wb}^{-1} = 360 \text{ cm}^2$$

- 3) A single phase, 50 Hz, 1000 kVA transformer has a ratio of 12000 / 240V ratio has a maximum flux density of 1.2 wb/m<sup>2</sup> and an effective cross section of 300 cm<sup>2</sup>, the magnetising current (I<sub>MN</sub>) is 0.2 A. estimate the inductance of each wire on open circuit.

Data:  $\Phi = 50 \text{ Hz}$ ,  $B_m = 1.2 \text{ wb/m}^2$ ,  $A = 300 \text{ cm}^2$ ,  $Z = 0.25$

$$E_1 = 4.44 B_m A N_1$$

$$\Phi_m = B_m A = 1.2 \times 300 \times 10^{-4} = 0.036 \text{ wb}$$

$$12000 = 4.44 \times 0.036 \times 50 \times N_1$$

$$N_1 = 1501.5 \approx 1500$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \Rightarrow \frac{\Phi_2}{\Phi_1} = \frac{N_2}{N_1} \Rightarrow N_2 = 30.04 \approx 30$$

$$L_1 = \frac{N_1 \Phi}{I} = \frac{1500 \times 0.036}{0.2} = 270.36 \text{ H}$$

$$L_2 = \frac{N_2 \Phi}{I} = \frac{30 \times 0.036}{0.2} = 5.44 \text{ H}$$

The voltage per turn of a single phase transformer is 11 volt when the primary winding is connected to a 220 volt, 50 Hz secondary. The secondary voltage is found to be 550 volt. Find the primary and secondary turns and core area if maximum flux density is 1.1 tesla.

Data:  $\Phi_1 = 1.1 \text{ V}$ ,  $E_1 = 220 \text{ V}$ ,  $\Phi_2 = 50 \text{ HZ}$ ,  $\Phi_m = 550 \text{ V}$ ,

$$B_m = 1.2 \text{ T}$$

$$E_1 = \left[ \frac{\text{e.m.f}}{\text{turn}} \right] \times N_1 \Rightarrow 220 = 550 \text{ N}_1 \Rightarrow N_1 = 400$$

$$E_2 = \left[ \frac{\text{e.m.f}}{\text{turn}} \right] \times N_2 \Rightarrow 550 = 1.1 N_2 \Rightarrow N_2 = 500$$

$$E_1 = 4.44 B_m A N_1$$

$$220 = 4.44 \times 1.2 \times 500 \times A \times 200$$

$$\Phi_m = 5 \times 10^{-3}$$

$$B_m = \frac{\Phi_m}{A} \Rightarrow A = \frac{\Phi_m}{B_m}$$

$$A = \frac{5 \times 10^{-3}}{1.1} = 4.5 \cdot 10^{-3} \text{ m}^2 = 45.04 \text{ cm}^2$$

5) A 1-phase transformer has 360 turns and 180 turns respectively in the secondary and primary windings. The resistances in the secondary and primary are 0.233 and 0.069. Calculate the equivalent resistance of

- 1) The primary in terms of the secondary winding
- 2) The secondary in terms of the primary winding
3. The total resistance of the transformer in terms of the primary

Data :  $N_2 = 360$ ,  $N_1 = 180$ ,  $R_2 = 0.233 \Omega$ ,  $R_1 = 0.069 \Omega$

$$k = \frac{N_2}{N_1} = \frac{360}{180} = 2$$

as secondary turns are more, secondary winding has high voltage side, hence the secondary side resistance values are high.

$$(1) R'_1 = k^2 R_1 = 4 \times 0.069 = 0.269 \Omega$$

$$(2) R'_2 = \frac{R_2}{k^2} = \frac{0.233}{4} = 0.05825 \Omega$$

$$(3) R_{12} = R_1 + R'_2 = 0.069 + 0.05825 = 0.12535 \Omega$$

6) A 100kVA, 100/200 volt single phase transformer has the following parameters.  $r_1 = 0.1 \Omega$ ,  $x_1 = 0.3 \Omega$ ,  $r_2 = 0.004 \Omega$ ,  $x_2 = 0.012 \Omega$ . Find equivalent resistance and leakage reactance as referred to high voltage winding.  
Data:  $V_1 = 1100V$ ,  $V_2 = 200V$ ,  $r_{12} = 0.1 \Omega$ ,  $x_{12} = 0.3 \Omega$ .

$$r_2' = 0.004 \Omega, x_2' = 0.012 \Omega$$

$$k = \frac{V_2}{V_1} = \frac{200}{1100} = 0.1818$$

On high voltage side the impedance is high

$$R_{12}' = \frac{R_2}{k^2} = \frac{0.004}{(0.1818)^2} = 0.121 \Omega$$

$$R_{12} = r_1 + r_{12}' = 0.1 + 0.121 = 0.221 \Omega$$

$$X_{12}' = \frac{x_2}{k^2} = \frac{0.012}{(0.1818)^2} = 0.363 \Omega$$

$$X_{12} = x_1 + x_{12}' = 0.3 + 0.363 = 0.663 \Omega$$

4) A single phase transformer with 10:1 turns ratio and rated at 50 kVA, 2400 V / 50 Hz is used to step down the voltage to a distribution system. The low tension voltage is kept constant at 240V. find the value of load impedance on the low tension side so that the transformer will be loaded fully. find the value of maximum flux inside the core if the low tension side has 92 turns

$$\text{data: } V_2 = 240V, \quad V_1 = 50 kV, \quad \theta = 50^\circ, \quad N_2 = 92$$

$$I_2(\text{F.L}) = \frac{V_2}{V_1} = \frac{50 \times 10^3}{240} = 208.333A$$

$$Z_L (\text{F.L}) = \frac{V_2}{I_2(\text{F.L})} = \frac{240}{208.333} = 1.152 \Omega$$

$$V_2 = 41.44 + j0 V$$

$$240 = 41.44 + 50 \times \theta + j0 \times 240$$

$$\theta = 0.647 \text{ rad}$$

8) A single phase transformer takes 10A and on no-load at 0.2 p.f lagging. the turns ratio 4:1 (high down). If the load on the secondary is 300 A at 0.6 p.f lagging, find the primary current and power factor. also draw the phasor diagram.

data:  $I_0 = 10A$ ,  $\cos \phi_0 = 0.2$ ,  $\frac{N_1}{N_2} = \frac{4}{1}$ ,  $\theta_2 = 200^\circ$ ,  $\cos \phi_2 = 0.85$

$$\theta_2 = \frac{N_2}{N_1} = \frac{1}{4} = 0.25$$

$$I_2' = 6I_2 = \frac{1}{4} \times 60000 = 150A$$


$$\theta_2 = 68.46^\circ - 16.95^\circ = 31.98^\circ$$

$I_1'$  is an anti phase with  $I_2$  which lags  $I_2$  by  $31.98^\circ$ .

$$\cos \phi_0 = 0.2$$

$$\phi_0 = 72.463^\circ$$

$$I_1 = I_2' + I_0$$

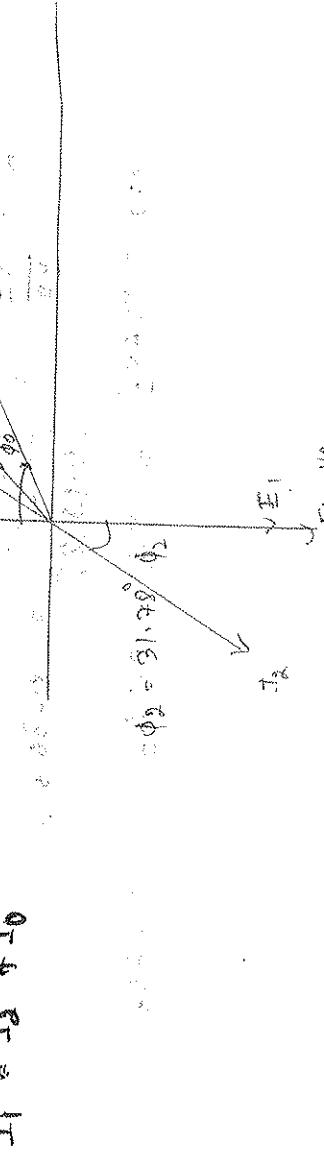


Remove  $\tau_2^1$  and  $\tau_0$  into two components, along  $\phi$  and in quadrature with  $\phi$

$$\text{Horizontal component of } \tau_0 = \tau_0 \cos \phi = 9.998$$

Vertical component of  $\tau_0 = \tau_0 \sin \phi = 26.3388$
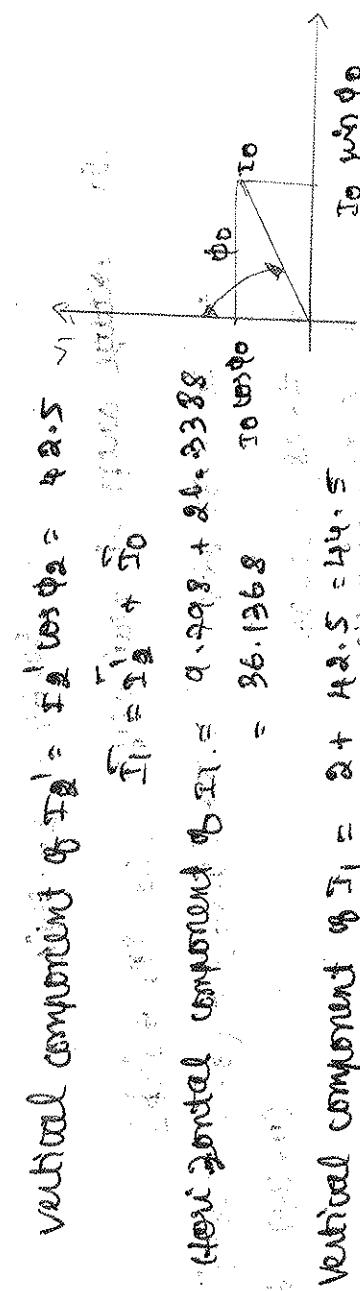
$$\text{Horizontal component of } \tau_2^1 = \tau_2^1 \cos \phi_2 = 42.5$$



$$\text{Horizontal component of } \tau_2^1 = 9.998 + 26.3388$$


$$= 36.1368 \quad \text{To wind 10}$$

$$\text{Vertical component of } \tau_2^1 = 2 + 42.5 = 44.5 \quad \text{To wind 10}$$

$$|I_{21}| = \sqrt{(36.1368)^2 + (44.5)^2} = 57.3246$$

As  $\phi_1$  is the angle made by  $I_1$  with  $V_1$ , which is  $90^\circ$

$$\tan \phi = 36.1368$$

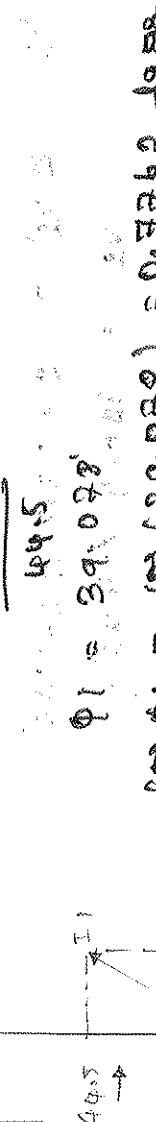

$$\phi_1 = 39.073^\circ$$

$$\cos \phi_1 = \cos(39.073^\circ) = 0.7762 \text{ degrees}$$



$$36.1368$$

$$44.5$$

- q) The parameters of approximate equivalent circuit of a 4 kVA, 300/1400 V, 50 Hz transformer are  $R_p = 0.15\Omega$ ,  $X_p^1 = 0.37\Omega$ ,  $\tau_0 = 600 \mu s$ ,  $\tau_m = 300 \mu s$ . If a voltage of 200V is applied to primary, a current of 10A at lagging power factor of 0.8 flows in the secondary winding. Calculate  
 i) the current in the primary IP  
 ii) the terminal voltage at the secondary side

$$\text{Data : } I_2 = 10 \text{ A, } \cos \phi = 0.8 \text{ lagg, } \text{, } R = \frac{V_2}{I_2} = \frac{400}{200} = 2$$

$$I_2^1 = V_2 = 2 \times 10 = 20 \text{ A at } 0.8 \text{ lagging}$$

$$I_m = \frac{V_1}{X_m} = \frac{200}{300} = 0.666 \text{ A}$$

$$I_2^1 = 20.6 - 10 \times 0.8 = 20.6 - 36 \times 0.869 = 16.312 \text{ A}$$

$$I_m = \frac{V_1}{X_m} = \frac{200}{300} = 0.666 \text{ A}$$

(5)

$$Z_C = \frac{V_1}{R_0} = \frac{200}{600} = 0.333 \Omega$$

$$I_P = (Z_C + jX_B) I_M = (0.333 + j0.866) 10 = 10.393 - j12.866 \text{ A}$$

$$V_{10} = 16.393 - j12.866 + 100 = 106.393 - j12.866 \text{ V}$$

(ii) voltage drop in primary  $= -Z_2' R_p + jX_p'$

$$\begin{aligned} &= (200 - 36.869^\circ) + (0.15 + j0.37) = (204.36869^\circ) \\ &\quad = 4.98 \angle 31.86^\circ \text{ V} \\ &\quad = 6.836 + j4.117 \text{ V} \end{aligned}$$

$$\begin{aligned} V_2' &= V_1 - \text{voltage drop} \\ &= (200 + j0) - (6.836 + j4.117) \\ &= 193.164 - j4.117 \text{ V} \end{aligned}$$

$$V_2 = |V_2'| \angle -1.22^\circ = 193.2 \angle -1.22^\circ \text{ V}$$

$$V_2 = |V_2| \angle 8 \times 1.93.2 \angle -1.22^\circ$$

$$V_2 = 336.4 \angle -1.22^\circ \text{ V}$$

- 10) A 100 kVA, 6.6 kV / 415 V single-phase transformer has an effective impedance of  $(3+j8)\Omega$  referred to 415 V side. Estimate the full load voltage regulation at 0.8 pf lagging and 0.8 pf leading.

Data: The primary is 415 V,  $Z_{10} = 3+j8\Omega$ ,  $R_{10} = 3\Omega$ ,  $X_{10} = 8\Omega$

$$\begin{aligned} Z_{10} &= \frac{415}{6.6 \times 10^3} = 0.06289 \Omega \\ (Z_1)_{FL} &= \frac{V_A}{V_1} = \frac{100 \times 10^3}{6.6 \times 10^3} = 15.154 \Omega \\ (Z_2)_{FL} &= \frac{V_A}{V_2} = \frac{100 \times 10^3}{415} = 240.96384 \Omega \end{aligned}$$

$$\begin{aligned} R_{20} &= k^2 R_{10} = 0.01185 \Omega \\ X_{20} &= k^2 X_{10} = 0.031622 \Omega \end{aligned}$$

(i)  $\cos \phi = 0.8$  lagging full load,  $\sin \phi = 0.6$

$$Y_R = (1)_{FL} \text{ primary reactance} + X_{10} \sin \phi = 11.652 \frac{\Omega}{V}$$

$$\gamma R = \frac{(I_2)_{FL} [R_{22} \cos\phi + X_{22} \sin\phi] \times 100}{V_2} = 1.65\% \quad (1)$$

(ii)  $\gamma R = 0.8$  radians, full load,  $\sin\phi = 0.6$

$$\gamma.R = \frac{15.1515 [73 \times 0.8 - 36 \times 0.6]}{60 \times 10^3} = -0.5509\%$$

- (iii) At 30 kVA, 2500 V, single phase transformer has the following parameters:

HV winding:  $\gamma_1 = 8\Omega$  and  $X_1 = 17\Omega$   
 LV winding:  $\gamma_2 = 0.3\Omega$  and  $X_2 = 0.7\Omega$   
 find the voltage regulation and the secondary terminal voltage at full load for a pf of 0.8 lagging and 0.8 leading. The primary voltage is held constant at 2500V  
 data:  $V_1 = 2500V$ ,  $V_2 = 500V$ ,  $R = \frac{V_2}{V_1} = 0.2$

$$R_{22} = \gamma_2 + R^2 \sin\phi = 0.3 + (0.2)^2 \times 8 = 0.62\Omega$$

$$X_{22} = \gamma_2 + R^2 \gamma_1 = 0.3 + (0.2)^2 \times 17 = 1.38\Omega$$

$$I_2(FL) = \frac{V_A}{V_2} = \frac{20 \times 10^3}{500} = 40A$$

$$\cos\phi = 0.8 \text{ lag}$$

$$\gamma.R = I_2(FL) [R_{22} \cos\phi + X_{22} \sin\phi] \times 100 = 10.592\%$$

$$V_2 = 500 - I_2(FL) [R_{22} \cos\phi + X_{22} \sin\phi]$$

$$V_2 = 497.04 \text{ V}$$

$$(i) \cos\phi = 0.8 \text{ lead}$$

$$\gamma.R = \frac{I_2(FL) [R_{22} \cos\phi + X_{22} \sin\phi] \times 100}{V_2} = -2.65\%$$

$$V_2 = 500 - I_2(FL) [R_{22} \cos\phi + X_{22} \sin\phi] = 513.28 \text{ V}$$

- (ii) A single phase transformer on full load has an impedance drop of 10V. Calculate the value of power factor when its regulation will be 28%.

For 20% voltage regulation

$$F_2 = V_2 \text{ and } \gamma.R = 0$$

power factor is leading for zero voltage regulation

$$\gamma.R = \frac{\gamma_1 R_2 \cos\phi - \gamma_1 X_2 \sin\phi}{V_1 \times 100} = 0$$

7

$$T_1 R_{12} - T_1 X_{12} \sin \phi = 0$$

$$T_1 R_{12} = \text{resistive drop} = V_R = 10V$$

$$T_1 X_{12} = \text{impedance drop} = V_2 = 20V$$

$$\tan \phi = \frac{V_R}{V_2} = \frac{10}{19.3205} = 0.5473$$

$\phi = 36^\circ$

$\cos \phi = 0.866$  lagging

This is the power factor from zone one voltage regulation

(3)

The primary and secondary windings of 500 kVA transformer have resistance of 0.4 ohm and 0.001 ohm respectively.

The primary and secondary voltages are 6600 V and 400 V respectively. The iron loss is 3 kW. Calculate the efficiency on full load, the load factor being 0.8 lagging.

Data: 500 kVA,  $R_1 = 0.4 \Omega$ ,  $R_2 = 0.001 \Omega$ ,  $V_1 = 6600V$ ,  $V_2 = 400V$

$$P_1 = \text{iron loss} = 3kW$$

$$T_1(FL) = \frac{V_R}{V_1} = \frac{500 \times 10^3}{6600} = 75.75A$$

$$R = \frac{V_2}{V_1} = \frac{400}{6600} = 0.0606 \quad R_2' = \frac{R_2}{k_2} = \frac{0.001}{0.0606} = 0.24925$$

$$R_{12} = R_1 + R_2' = 0.4 + 0.24925 = 0.64225 \Omega$$

$$(P_{out})_{FL} = \text{when loss on full load} = [T_1(FL)]^2 R_{12}$$

$$= (75.75)^2 \times 0.64225$$

$$2858.1764W$$

$$\eta_{FL} = \frac{VA_{out}\phi}{VA_{out}\phi + P_1 + P_{out}(FL)} \times 100$$

$$= \frac{500 \times 10^3 \times 0.8}{500 \times 10^3 \times 0.8 + 3 \times 10^3 + 3858.1764} \times 100$$

$$= 98.3143\% \text{ full load efficiency}$$

full load obtain by

(4) A 600 kVA, single phase transformer when working at V.P.F has an efficiency of 92% at full load and also at half load. Determine the efficiency when it operates at unity P.F and 60% full load.

Data : 600 kVA, cosφ = 1, η<sub>FL</sub> = 92%, η<sub>HL</sub> = 92%.

$$\therefore \eta_{FL} = \frac{(kVA \times 10^3) \cos \phi}{(kVA \times 10^3) \cos \phi + (Pcu) FL + Pi} \times 100$$

$$0.92 = \frac{600 \times 10^3}{600 \times 10^3 + Pcu) FL + Pi}$$

$$Pcu) FL + Pi = 52173.913 \rightarrow ①$$

For half load, n =  $\frac{1}{2} = 0.5$

$$\therefore \eta_{HL} = \frac{n \times (kVA \times 10^3) \cos \phi}{n \times (kVA \times 10^3) \cos \phi + n^2 (Pcu) FL + Pi} \times 100$$

$$0.92 = \frac{0.5 \times 600 \times 10^3}{0.5 \times 600 \times 10^3 + Pcu) FL + Pi}$$

$$0.25 (Pcu) FL + Pi = 26086.9565 \rightarrow ②$$

Solving equation ① & ②  
 $Pcu) FL = 34782.608 \text{ W}$

$$Pi = 17391.304 \text{ W}$$

To find η at 60% of full load at cosφ = 1, n = fraction of load = 0.6

$$\therefore \eta = \frac{n \times (kVA \times 10^3) \cos \phi}{n \times (kVA \times 10^3) \cos \phi + n^2 (Pcu) FL + Pi} \times 100$$

$$= \frac{0.6 \times 600 \times 10^3 \times 1}{0.6 \times 600 \times 10^3 \times 1 + 0.36 \times 34782.608 + 17391.304} \times 100$$

$$= 92.3282\%$$

(5) Calculate the efficiency at half, full load of a 1000 VA transformer for no-load factor 30%, unity and 0.8. The copper loss is 1000W at full load and iron loss is 1000 W

Data : 1000 kVA, (Pcu) FL = 1000 W, Pi = 1000 W

(i)  $\cos \phi = 1$ , full load

$$\eta_{FL} = \frac{VA \cos \phi}{VA \cos \phi + (P_{cu} + P_i)} \times 100$$
$$= \frac{100 \times 10^3 \times 1}{100 \times 10^3 \times 1 + 1000 + 1000} \times 100$$
$$= 98.04\%$$

(ii)  $\cos \phi = 0.8$ , full load

$$\eta_{FL} = \frac{100 \times 10^3 \times 0.8}{100 \times 10^3 \times 0.8 + 1000 + 1000} \times 100$$
$$= 97.56\%$$

For half load, copper loss =  $n^2 (P_{cu}) \cdot F.L$  where  $n = 0.5$

$$\eta_{FL} = \frac{nVA \cos \phi}{nVA \cos \phi + n^2 (P_{cu}) F.L + P_i} \times 100$$

(i)  $\cos \phi = 1$ , half load

$$\eta_{FL} = \frac{0.5 \times 100 \times 10^3 \times 1}{0.5 \times 100 \times 10^3 + 1 + (0.5)^2 \times 1000 + 1000} \times 100$$
$$= 96.96\% \text{ (Ans)}$$

(ii)  $\cos \phi = 0.8$ , half load

$$\eta_{FL} = \frac{0.5 \times 100 \times 10^3 \times 0.8}{0.5 \times 100 \times 10^3 \times 0.8 + (0.5)^2 \times 1000 + 1000} \times 100$$
$$= 96.96\% \text{ (Ans)}$$

6. A 200V, single phase transformer has an efficiency of 98% at full load, 97.8% being due to the maximum efficiency occurs at three quarters full load. Calculate the iron loss and full load copper losses. Data: 200 kVA,  $\eta_{FL} = 98\%$ ,  $\cos \phi = 0.8$  kVA

$$\eta_{FL} = \frac{VA \cos \phi}{VA \cos \phi + P_i + (P_{cu}) F.L} \times 100$$

$$0.98 = \frac{200 \times 10^3 \times 0.8}{200 \times 10^3 \times 0.8 + P_i + (P_{cu}) \cdot F.L} \times 100$$
$$P_i + (P_{cu}) F.L = 3265.3061 \rightarrow ①$$

$$\text{KVA at } \eta_{max} = \frac{3}{4} \text{ full load kva}$$

$$\text{but } \text{KVA at } \eta_{max} = \text{KVA rating} \times \sqrt{\frac{P_i}{(P_{cu}) F.L}}$$

$$\frac{3}{4} \times \text{VA}_{\text{max}} = \text{VA}_{\text{max}} \times \sqrt{\frac{P_i}{P_{\text{max}}}} \Rightarrow 0.75 \sqrt{7} = \frac{P_i}{(\text{VA}_{\text{max}})_{\text{PL}}}$$

$$P_{\text{max}} (\text{F.L.}) = 1.73778 \text{ P}_i = 3285.36 \text{ W} \quad \rightarrow (2)$$

$$\text{At } \eta_{\text{max}}, \text{ P}_i = \text{P}_{\text{max}} \quad \text{Ans}$$

$$\text{VA}_{\text{max}} (\text{F.L.}) = 1175.51 \text{ VA}$$

$$P_{\text{max}} (\text{F.L.}) = 2089.8 \text{ W}$$

17. A 500 kVA transformer has core loss of 2200 W and a full load copper loss of 7500 W. If the power factor of the load is 0.9 lagging, calculate the full load efficiency and the kVA load at which maximum efficiency occurs.

$$\text{Data: } 500 \text{ kVA}, \quad P_i = 2200 \text{ W}, \quad P_{\text{cu}} (\text{F.L.}) = 7500 \text{ W}, \quad \cos \phi = 0.9$$

$$\eta_{\text{PL}} = \frac{\text{VA}_{\text{max}} \Phi}{\text{VA}_{\text{max}} \Phi + P_i + P_{\text{cu}} (\text{F.L.})} \times 100$$

$$= \frac{500 \times 10^3 \times 0.9 \times 100}{500 \times 10^3 + 0.9 + 2200 + 7500} = 97.89\%$$

$$\text{KVA for } \eta_{\text{max}} = \text{VA}_{\text{max}} \times \sqrt{\frac{P_i}{P_{\text{max}} (\text{F.L.})}}$$

$$= 500 \times \sqrt{\frac{2200}{7500}}$$

$$= 270.80 \text{ kVA}$$

18. The maximum efficiency of a single phase 250VA, 2000 1250 V transformer occurs at 80% full load and is equal to 97.5%. at 0.8 p.f. determine the efficiency and regulation von full load at 0.8 p.f. Lagging. If the impedance of the transformer is a percent value : 250 kVA, 2000 1250 V = fraction of load = 80%.

$$\eta_{\text{max}} = 95.8\%, \quad \cos \phi = 0.8$$

$$\text{At } \eta_{\text{max}}, \quad \text{P}_i = \text{P}_{\text{max}}$$

$$\eta_{\text{max}} = \frac{\text{VA}_{\text{max}} \times 10^3 \text{ cos} \phi}{\text{VA}_{\text{max}} \times 10^3 \text{ cos} \phi + 2P_i} \times 100$$

$$0.975 = \frac{0.8 \times 250 \times 10^3}{0.8 \times 250 \times 10^3 + 2000 \times 1250 \times 0.8} \times 100$$

$$0.8 \times 250 \times 10^3 \times 0.975 = 0.8 \times 250 \times 10^3 \times 0.8 + 2P_i$$

(11)

$P_i = 4102.564 \text{ W} = \text{From lesser side}$   
At 80% load

$$(0.8)^2 (P_{ui})_{F.L.} = 4102.564 \quad \text{As no n.m.m.}$$

$$(P_{ui})_{F.L.} = 6410.2564 \text{ W}$$

$$\eta_{F.L.} = \frac{kVA \times 10^3 \times 0.8}{kVA \times 10^3 \times 0.8 + (P_{ui})_{F.L.} \times 100} \times 100$$

$$= \frac{250 \times 10^3 \times 0.8}{250 \times 10^3 \times 0.8 + 6410.2564} \times 100 \\ = 95\%$$

$$(Z_1)_{F.L.} = \frac{kVA \times 10^3}{V_1} = \frac{250 \times 10^3}{2000} = 125 \Omega$$

$\rho_{eq} = \text{equivalent resistance referred to primary}$

$$= \frac{(P_{ui})_{F.L.}}{(I_1)_{F.L.}^2} = \frac{6410.2564}{(125)^2} \approx 0.4102 \Omega$$

$$\text{Resistance} = \frac{V_R}{I_1} = \frac{(P_{ui})_{F.L.}}{V_1} = \frac{125 \times 0.4102 \times 100}{2000} \\ = 2.563 \Omega$$

n. impedance = 9% given

$$\text{n. reactance} = V_x = \sqrt{100^2 - (2.563)^2} = 8.6273 \Omega$$

$$\text{n. regulation} = [V_{x100\phi} + V_{x100\theta}] \times 100$$

$$= [0.02563 \times 0.8 + 0.086273 \times 0.6] \times 100 \\ = 4.2264\%$$

- Q9). A 100 kVA, 110 kV, 50 Hz, single phase transformer has an iron loss of 1100W. The copper loss with 8A in the high voltage winding is 400 W. Calculate the efficiency at i) 25%. ii) 50%. iii) 100%. If the normal load for power factor of 0.8 and 0.8 - the output terminal voltage being maintained at 10kV. Find also the load for maximum efficiency at both power factors.

$$\text{Data : } 100 \text{ kVA}, V_1 = 1000 \text{ V}, V_2 = 10 \text{ kV}, P_i = 11000 \text{ W}$$

$P_{ui} = 400 \text{ W with } I = 5 \text{ A in high voltage winding}$

$$\text{I}_1(\text{F.L}) = \frac{V_A}{V_1} = \frac{100 \times 10^3}{1000} \approx 100A$$

$$\text{I}_2(\text{F.L}) = \frac{V_A}{V_2} = \frac{100 \times 10^3}{10 \times 10^3} = 10A$$

$$P_{\text{cu}} \propto \pi^2 \cdot \frac{(P_{\text{cu}})'}{P_{\text{cu}}(\text{F.L})} = \frac{\pi^2 r^2}{(\text{I}_{\text{F.L}})^2}$$

$$\frac{400}{P_{\text{cu}}(\text{F.L})} = \left[ \frac{5}{16} \right]^2$$

$$P_{\text{cu}}(\text{F.L}) = 1600 \text{ W}$$

i) 25% load :  $n = 0.25$

$$P_{\text{cu}} = n^2 \times P_{\text{cu}}(\text{F.L}) = (0.25)^2 \times 1600 = 100 \text{ W}$$

$$\eta = \frac{n \cdot V_A \cos \phi}{n \cdot V_A \cos \phi + P_i + P_{\text{cu}}} \times 100 \quad \text{where } P_{\text{cu}} = n^2 P_{\text{cu}}(\text{F.L})$$

$$\eta = 1 \cdot \eta = \frac{0.25 \times 100 \times 10^3 \times 1 + 1100 + 100}{0.25 \times 100 \times 10^3 \times 1 + 100 + 400} \times 100 = 95.42\%$$

$$\text{ii) 50% load : } \eta = 0.5 \cdot \eta = \frac{0.25 \times 100 \times 10^3 \times 1 + 1100 + 100}{0.25 \times 100 \times 10^3 \times 1 + 100 + 400} \times 100 = 96.42\%$$

$$\text{iii) 100% load : } \eta = 0.8 \cdot \eta = \frac{0.25 \times 100 \times 10^3 \times 1 + 100}{0.25 \times 100 \times 10^3 \times 1 + 100} \times 100 = 97.34\%$$

(ii) SOR : power :  $n = 0.5$

$$\begin{aligned} \text{a) } \cos \phi &= 1 \cdot \eta = \frac{0.5 \times 100 \times 10^3 \times 1}{0.5 \times 100 \times 10^3 \times 1 + 100} \times 100 \\ &= 97.08\% \\ \text{b) } \cos \phi &= 0.8 \cdot \eta = \frac{0.5 \times 100 \times 10^3 \times 1}{0.5 \times 100 \times 10^3 \times 1 + 100} \times 100 \\ &= 96.385\% \end{aligned}$$

(iii) 100% load :  $n = 1$

$$\begin{aligned} \text{a) } \cos \phi &= 1 \cdot \eta = \frac{1 \times 100 \times 10^3 \times 1}{1 \times 100 \times 10^3 \times 1 + 100} \times 100 = 97.3\% \\ \text{b) } \cos \phi &= 0.8 \cdot \eta = \frac{1 \times 100 \times 10^3 \times 1}{1 \times 100 \times 10^3 \times 1 + 100 + 1600} \times 100 \\ &= 96.735\% \end{aligned}$$

