



ST. ANNE'S COLLEGE OF ENGINEERING AND TECHNOLOGY

(Approved by AICTE, New Delhi. Affiliated to Anna University, Chennai)
ANGUCHETTYPALAYAM, PANRUTI – 607 106.

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

QUESTION BANK

EE 3591 - POWER ELECTRONICS

V SEMESTER

Prepared by

Mrs. T. ARTHI, AP/EEE

UNIT I - SWITCHING POWER SUPPLIES

SYLLABUS: MOSFET dynamic behavior - driver and snubber circuits - low power high switching frequency switching Power supplies, buck, boost, buck-boost converters – Isolated topologies – resonant converters - switching loss calculations and thermal design.

PART - A

| Q.No | Questions | BT Level | Competence | COs |
|------|----------------------------------------------------------------------------------|----------|---------------|-----|
| 1. | Define the term pinch off voltage of MOSFET. | 1 | Remembering | CO1 |
| 2. | Define Duty cycle. | 1 | Remembering | CO1 |
| 3. | Name any two applications of SMPS. | 1 | Remembering | CO1 |
| 4. | Name the limitation of high frequency operation of a power electronic device. | 1 | Remembering | CO1 |
| 5. | Show the circuit diagram of a boost converter. | 2 | Understanding | CO1 |
| 6. | What is resonant converter? States its advantages. | 2 | Understanding | CO1 |
| 7. | Classify the switched mode regulators and write its advantages. | 3 | Applying | CO1 |
| 8. | Compare ZVS and ZCS. | 5 | Evaluating | CO1 |
| 9. | Why MOSFETs are not preferred for low frequency applications? | 2 | Understanding | CO1 |
| 10. | What do you mean by controlled switch? | 2 | Understanding | CO1 |
| 11. | What is the need of driver circuit? | 2 | Understanding | CO1 |
| 12. | What is the limitation of high frequency operation of a power electronic device? | 2 | Understanding | CO1 |
| 13. | What are the parameter involved in switching loss of power device? | 3 | Applying | CO1 |
| 14. | What are the advantage and disadvantages of buck/boost regulator? | 3 | Applying | CO1 |
| 15. | What is meant by buck regulator? | 3 | Applying | CO1 |
| 16. | What is meant by SMPS? Mention its two advantages. | 4 | Analysing | CO1 |
| 17. | What is meant by boost regulator? | 4 | Analysing | CO1 |
| 18. | What are the circuit configurations used for SMPS? | 4 | Analysing | CO1 |
| 19. | Give the uses of resonant switching. | 5 | Evaluating | CO1 |
| 20. | What is meant by resonant converter? | 2 | Understanding | CO1 |

PART - B

| | | | | |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 1. | Explain the working of buck converter with neat waveform and also derive the expression for peak to peak voltage across the capacitor. (13) | 2 | Understanding | CO1 |
| 2. | With a neat power circuit diagram, explain the operation of boost converter. Draw the load voltage and load current waveforms and derive the expression for the output voltage. (13) | 2 | Understanding | CO1 |
| 3. | Discuss L Type and M type zero current switching resonant converters. (13) | 3 | Applying | CO1 |
| 4. | Draw the power circuit diagram of a buck-boost regulator and explain its operation with equivalent circuit for different modes and its waveforms. (13) | 2 | Understanding | CO1 |

| | | | | |
|-----------------|----------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 5. | What is resonant switching? Explain its concept with relevant circuit diagram. (13) | 2 | Understanding | CO1 |
| 6. | Explain the switching characteristics of MOSFET with the help of neat circuit diagram of waveforms. (13) | 1 | Remembering | CO1 |
| 7. | Explain the operation of flyback converter. (13) | 1 | Remembering | CO1 |
| 8. | Describe the working principle of boost converter with circuit and waveform. (13) | 1 | Remembering | CO1 |
| 9. | Explain the ZVS resonant converter with appropriate circuit and waveforms. (13) | 1 | Remembering | CO1 |
| PART - C | | | | |
| 1. | Explain the switching loss calculation thermal design of MOSFET. (15) | 2 | Understanding | CO1 |
| 2. | With neat diagram and waveform explain resonant DC-DC converter. (15) | 1 | Remembering | CO1 |

UNIT II - INVERTERS

SYLLABUS: IGBT: Static and dynamic behavior - single phase half bridge and full bridge inverters - VSI :(1phase and three phase inverters square wave operation) - Voltage control of inverters single, multi pulse, sinusoidal, space vector modulation techniques– various harmonic elimination techniques-CSI

| Q.No | Questions | BT | Competence | COs |
|------|---------------------------------------------------------------|----|---------------|-----|
| 1. | List the various advantages of using PWM control of inverters | 1 | Remembering | CO4 |
| 2. | What is the advantage of 120 ° mode of inverter operation | 1 | Remembering | CO4 |
| 3. | Define space vector modulation. | 1 | Remembering | CO4 |
| 4. | Tell why diodes should be connected in antiparallel | 1 | Remembering | CO4 |
| 5. | What is harmonic elimination by PWM? | 1 | Remembering | CO4 |
| 6. | What is meant by voltage source inverter? | 1 | Remembering | CO4 |
| 7. | Express the applications of a CSI. | | Understanding | CO4 |
| 8. | Discuss PWM control and types of PW techniques. | 2 | Understanding | CO4 |
| 9. | What is a current source inverter? | 2 | Understanding | CO4 |
| 10. | What are the advantages of PWM control in inverter. | 2 | Understanding | CO4 |
| 11. | What is the function of feedback diodes in bridge inverter. | 3 | Applying | CO4 |
| 12. | Show the methods of reduction of harmonic content. | 3 | Applying | CO4 |

| | | | | |
|-----|------------------------------------------------------------------------------------|---|-------------|-----|
| 13. | What are the main differences between voltage-source and current source inverters? | 3 | Applying | CO4 |
| 14. | Compare SPWM and SVM | 4 | Analysing | CO4 |
| 15. | Differentiate CSI and VSI. | 4 | Analysing | CO4 |
| 16. | List the application of Inverters | 4 | Analysing | CO4 |
| 17. | What is meant by space vector modulation | 5 | Evaluating | CO4 |
| 18. | Evaluate the disadvantages of the harmonics present in the inverter system? | 5 | Evaluating | CO4 |
| 19. | Why thyristors are not preferred for Inverter? | 1 | Remembering | CO4 |
| 20. | State the necessity of return current diodes in inverter. | 1 | Remembering | CO4 |

PART - B

| | | | | |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------|---|-------------|-----|
| 1. | Describe with circuit IGBT static I-V, transfer and turn –on and turn–off characteristics. (13) | 1 | Remembering | CO4 |
| 2. | Describe the operation of 3 phase bridge inverter for 120 degree mode of operation with aid of relevant phase and line voltage waveforms. (13) | | Remembering | CO4 |

| | | | | |
|-----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 3. | Describe the principle of operation of 3 phase voltage source inverter with 180° conduction mode with necessary waveforms and circuits. Also obtain the expression for line to line voltage. (13) | 1 | Remembering | CO4 |
| 4. | State the different methods of voltage control of inverters. Also describe about PWM control. (13) | 1 | Remembering | CO4 |
| 5. | Describe in detail, the various types of PWM methods available for voltage control employed in an inverter. (13) | 1 | Remembering | CO4 |
| 6. | Explain the SPWM and modified SPWM techniques for inverter switching. (13) | 2 | Understanding | CO4 |
| 7. | Describe the operation of 3 phase bridge inverter for 180 degree mode of operation with aid of relevant phase and line voltage waveforms. (13) | 2 | Understanding | CO4 |
| 8. | Explain the Principle of operation of 3-phase auto sequentially commutated CSI with power circuit. Draw the equivalent circuits and relevant waveforms. (13) | 2 | Understanding | CO4 |
| 9. | Examine the operation of single phase capacitor commutated CSI with R load. (13) | 3 | Applying | CO4 |
| 10. | Demonstrate the working of a single phase full bridge inverter supplying R, RL loads with relevant circuit and waveforms. (13) | 3 | Applying | CO4 |
| 11. | (i) Explain Multiple PWM. (7) (ii) Explain Sinusoidal PWM. (6) | 4 | Analysing | CO4 |

| | | | | |
|-----|-------------------------------------------------------------------------------------------------------|---|-----------|-----|
| 12. | Explain the different methods of voltage control adopted in an inverter with suitable waveforms. (13) | 4 | Analysing | CO4 |
|-----|-------------------------------------------------------------------------------------------------------|---|-----------|-----|

PART - C

| | | | | |
|----|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|------------|-----|
| 1. | Explain in detail the different types of harmonic control of inverters. (15) | 5 | Evaluating | CO4 |
| 2. | With neat diagram explain the need for space vector modulations employed in inverters also explain the advantage SPVWM over other technique employed in inverters. (15) | 4 | Analysing | CO4 |

UNIT III - UNCONTROLLED RECTIFIERS

SYLLABUS: Power Diode – half wave rectifier – mid-point secondary transformer based full wave rectifier – bridge rectifier – voltage doubler circuit – distortion factor – capacitor filter for low power rectifiers – LC filters – Concern for power quality – three phase diode bridge.

PART - A

| Q.No | Questions | BT Level | Competence | COs |
|------|----------------------------------------------------------------------------------------------------------|----------|---------------|-----|
| 1. | State applications of uncontrolled rectifiers. | 2 | Understanding | CO2 |
| 2. | What is RF? Why RF of single phase half wave rectifier is high? | 2 | Understanding | CO2 |
| 3. | What is the advantages of freewheeling diode in single phase half wave rectifier feeding inductive load? | 2 | Understanding | CO2 |
| 4. | What is the ripple frequency of single phase half wave converter and single phase full wave converter? | 2 | Understanding | CO2 |
| 5. | For the single phase full bridge rectifier, what is output voltage if supply voltage is 23 V rms. | 3 | Applying | CO2 |
| 6. | What is the ripple frequency of three phase bridge rectifier? | 3 | Applying | CO2 |
| 7. | State the advantages of three phase rectifiers. | 3 | Applying | CO2 |
| 8. | What is the purpose of double rectifier circuit? | 4 | Analyzing | CO2 |
| 9. | Which components of output are filtered by C and LC filters? | 4 | Analysing | CO2 |
| 10 | What is the PIV of single phase center tapped full wave rectifier and single bridge rectifier? | 4 | Analysing | CO2 |
| 11 | What is the transformer utilization factor? | 5 | Evaluating | CO2 |
| 12 | What is power factor? State its formula. | 5 | Evaluating | CO2 |
| 13 | What is rectification efficiency? | 3 | Applying | CO2 |
| 14 | Draw the circuit diagram of half wave rectifier? | 3 | Applying | CO2 |
| 15 | State the disadvantages of three phase rectifiers. | 2 | Understanding | CO2 |
| 16 | Write the difference between center tapped and bridge rectifier. | 2 | Understanding | CO2 |
| 17 | Draw the circuit diagram of three phase bridge rectifier with RL load. | 2 | Understanding | CO2 |
| 18 | Comparison of single phase half wave and full wave rectifiers. | 4 | Analysing | CO2 |
| 19 | What is power diode? | 3 | Applying | CO2 |
| 20 | What are the types of diode? | 3 | Applying | CO2 |

PART - B

| | | | | |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 1. | With the help of suitable diagram. Explain the dynamic characteristics of power diode. (13) | 1 | Remembering | CO2 |
| 2. | Draw the wave forms and explain the separation of single phase full wave rectifier with RL load. Draw the input and output wave forms. (13) | 1 | Remembering | CO2 |
| 3. | Explain the working function of single phase full wave center tapped rectifier with pure resistive load also draw the input and output wave forms. (13) | 1 | Remembering | CO2 |
| 4. | List the performance parameter of single phase bridge rectifier supplying RL load. (13) | 1 | Remembering | CO2 |
| 5. | Explain the operation of three phase star connected rectifier for R load with the help of waveform. (13) | 2 | Understanding | CO2 |

| | | | | |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 6. | With the help of circuit diagram and waveform explain the operation of three phase bridge rectifier for R load also draw its input and output voltage waveform. (13) | 2 | Understanding | CO2 |
| 7. | what is the need of filter circuit , explain LC filters. (13) | 2 | Understanding | CO2 |
| 8. | Draw the waveform and explain the C & LC filters. (13) | 3 | Applying | CO2 |
| 9. | Draw the wave forms and explain the separation of single phase full wave rectifier with RLE load. Draw the input and output wave forms. (13) | 3 | Applying | CO2 |
| 10 | With the help of circuit diagram and waveform explain the operation of three phase bridge rectifier for RL load also draw its input and output voltage waveform. (13) | 4 | Analysing | CO2 |

PART - C

| | | | | |
|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|-------------|-----|
| 1. | Explain the working function of single phase full wave center tapped rectifier with R and RL load also draw the input and output wave forms. (15) | 1 | Remembering | CO3 |
| 2. | With the help of circuit diagram and waveform explain the operation of three phase bridge rectifier for RLE load also draw its input and output voltage waveform. (15) | 1 | Remembering | CO3 |

UNIT IV - CONTROLLED RECTIFIERS

SYLLABUS: SCR-Two transistor analogy based turn- ON – turn ON losses – thermal protection – controlled converters (1 pulse, 2 pulse, 3 pulse, 6 pulse) - displacement factor – ripple and harmonic factor - power factor mitigation, performance parameters – effect of source inductance - inverter angle limit.

PART - A

| Q.No | Questions | BT Level | Competence | COs |
|-----------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|---------------|-----|
| 1. | Define overlap angle. | 1 | Remembering | CO3 |
| 2. | Show the power factor of semi converter is better than full converter. | 1 | Remembering | CO3 |
| 3. | Examine the effect of source impedance on the performance of converter. | 1 | Remembering | CO3 |
| 4. | Express the displacement factor for two pulse converter. | 2 | Understanding | CO3 |
| 5. | Predict the circuits turn –off time for single phase full converter. | 2 | Understanding | CO3 |
| 6. | Classify the various modes of operation of single phase fully controlled bridge converter. | 4 | Analysing | CO3 |
| 7. | Distinguish between symmetric and asymmetric semi converter configuration. | 4 | Analysing | CO3 |
| 8. | Why power factor of semi converter is better than full converter? | 5 | Evaluating | CO3 |
| 9. | | 2 | Understanding | CO3 |
| 10 | List some of the application of converters. | 1 | Remembering | CO3 |
| 11 | A two pulse converter is fed with a 230V, 50 Hz supply. The load on the converter is a pure resistance of $R=10\ \Omega$. Obtain the average output voltage for a firing angle of $\alpha =135^\circ$ | 6 | Creating | CO3 |
| 12 | Examine the harmonic factor for converter. | 3 | Applying | CO3 |
| 13 | Examine the term voltage ripple factor. | 3 | Applying | CO3 |
| 14 | Explain the inversion mode of converter. | 4 | Analysing | CO3 |
| 15 | Summarize the roles of freewheeling diode in a Full converter. | 5 | Evaluating | CO3 |
| 16 | A single phase full converter feeds power to RLE load with $R= 6\Omega$, $E=60V$.The full load inductance value is very large so as to maintain the load current continuous and ripple free .The ac source voltage is 230V and 50Hz. Find the average value of the output voltage for a firing angle delay of 50° . | 6 | Creating | CO3 |
| 17 | Define harmonic factor of the input current. | 2 | Understanding | CO3 |
| 18 | What is freewheeling diode, and what is its purpose? State its advantages. | 2 | Understanding | CO3 |
| 19 | What is the effect of inductive load in the performance of a three phase bridge rectifier? | 2 | Understanding | CO3 |
| 20 | List various applications of phase controlled converters. | 2 | Understanding | CO3 |
| PART - B | | | | |
| 1. | Describe the operation of three phase semi converter with R load and also draw the output voltage waveforms for 30° and 90° . (13) | 1 | Remembering | CO3 |
| 2. | Explain the operation of a single phase full converter with RLE load using relevant waveforms. Obtain the expressions for its average output voltage and RMS value of output voltage. (13) | 1 | Remembering | CO3 |

| | | | | |
|----|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 3. | Analyze the effect of source inductance in the operation of single phase fully controlled converter with relevant diagram and analysis. (13) | 4 | Analysing | CO3 |
| 4. | Discuss the effect of series inductance on the performance of the single phase full converter indicating clearly the conduction of various thyristors during one cycle. (13) | 2 | Understanding | CO3 |
| 5. | A 230 V, 50 Hz supply is connected to load resistance of 12Ω through half wave controlled rectifier. If the firing angle is 60 degree, Calculate (i) Average output voltage. (4) (ii) RMS output voltage. (3) (iii) Ratio of rectification and (3) (iv) Transformer utilization factor. (3) | 3 | Applying | CO3 |
| 6. | Explain the operation of a three phase, fully controlled bridge converter with associated waveforms. (13) | 4 | Analysing | CO3 |
| 7. | Summarize the operation of single phase two pulse midpoint converter with relevant voltage and current waveforms. (13) | 5 | Evaluating | CO3 |

| | | | | |
|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|-----------|-----|
| 8. | (i) A single phase bridge converter is utilized to produce regulated DC output voltage. The input voltage is 230 V and the load current is 8A for a firing angle of 30 degree. (a) Calculate the dc output voltage. (3) (b) Calculate the dc output voltage and current if a freewheeling diode is used at the output for the same firing angle. (4) (ii) Examine the single phase half wave rectifier circuit with RL load and freewheeling diode. (6) | 3 | Applying | CO3 |
| 9. | (i) A three phase full converter charges a battery from a three –phase supply of 230 V, 50Hz. The battery is 200 V and its internal resistance is 0.5Ω . On account of inductance connected in series with the battery, charging current is constant at 20 A. Compute firing angle delay and supply power factor. (7) (ii) Explain briefly the working of dual converter with a neat circuit diagram. (6) | 4 | Analysing | CO3 |
| 10 | A single phase half wave rectifier with an AC voltage of 150V has a pure resistive load of 9Ω . The firing angle of the thyristor is $\pi/2$. Determine the (i) Rectification Efficiency (ii) Form Factor (iii) Transformer derating factor (iv) Peak inverse voltage of the SCR (v) Ripple factor of the SCR. Assume the transformer ratio is 2:1. (13) | 6 | Creating | CO3 |

PART - C

| | | | | |
|----|----------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 1. | Explain the operation of the SCR with the help of two transistor analogy. Also drive an expression for anode current. (15) | 2 | Understanding | CO3 |
|----|----------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|

| | | | | |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 2. | Explain the operation of single phase full wave mid- point converter to RL load , with the help of circuit diagram and waveform. Also explain the effect of freewheeling diode. (15) | 2 | Understanding | CO3 |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|

UNIT V - AC PHASE CONTROLLERS

SYLLABUS: TRIAC triggering concept with positive and negative gate pulse triggering, TRIAC based phase controllers - various configurations for SCR based single and three phase controllers.

PART - A

| Q.No | Questions | BT Level | Competence | COs |
|------|---------------------------------------------------------------------------------------------------------|----------|---------------|-----|
| 1. | What are the two types of ac voltage controllers? Which one of these is preferred and why? | 1 | Remembering | CO5 |
| 2. | List the merits and demerits of AC voltage controller. | 1 | Remembering | CO5 |
| 3. | Why half wave AC voltage regulator not used. | 1 | Remembering | CO5 |
| 4. | List the merits and demerits of ac voltage controller. | 1 | Remembering | CO5 |
| 5. | What is the principle of ON-OFF control of AC controller? | 1 | Remembering | CO5 |
| 6. | Compare on-off and phase-angle ac voltage controllers. | 1 | Remembering | CO5 |
| 7. | Give the expression for RMS and average output voltage of single phase half wave ac voltage controller. | 2 | Understanding | CO5 |
| 8. | Explain the term sequence control of ac voltage controller. | 2 | Understanding | CO5 |
| 9. | Give the advantage of sequence control of ac voltage regulators. | 2 | Understanding | CO5 |
| 10 | List the applications of AC voltage controller. | 2 | Understanding | CO5 |
| 11 | What are the effects of load inductance on the performance of ac voltage controllers? | | Applying | CO5 |
| 12 | What is an ac voltage controller? | 3 | Applying | CO5 |
| 13 | What type of gating signal is used in single phase ac voltage controller with RL load. | 3 | Applying | CO5 |
| 14 | Write any two important applications of ac voltage controllers. | 4 | Analysing | CO5 |
| 15 | Differentiate phase control and sequence control of voltage controller. | 5 | Evaluating | CO5 |
| 16 | Explain the necessity of FACTS Devices in the power system and write its classification | 4 | Analysing | CO5 |
| 17 | What are the different control techniques for ac regulator? | 4 | Analysing | CO5 |
| 18 | Compare integral cycle control and phase control in AC voltage controller. | 5 | Evaluating | CO5 |
| 19 | Why is half wave ac voltage regulator not used? | 4 | Analysing | CO5 |
| 20 | Write the output R.M.S voltage for single phase ac voltage controller with resistance load. | 5 | Evaluating | CO5 |

| PART - B | | | | |
|-----------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 1. | Draw and Describe the circuit diagram of single phase AC voltage controller with RL load. Explain the circuit operation with necessary waveforms. (13) | 1 | Remembering | CO5 |
| 2. | Describe the operation of two stage sequence control of Ac voltage controller. (13) | 1 | Remembering | CO5 |
| 3. | A single phase full wave AC voltage controller has an input voltage of 230V 50Hz and it is feeding a resistive load of 10 Ohms. If the firing angle of thyristor is 110 degree. Calculate the output RMS voltage, input power factor and average current of thyristor. (13) | 2 | Understanding | CO5 |

| | | | | |
|-----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---------------|-----|
| 4. | A resistive load of 5 Ohm is fed through a single phase full wave AC voltage controller from 230V 50 Hz source. If the firing angle of thyristor is 120 degree. Calculate the (i) Output RMS voltage. (5) (ii) Input power factor. (4) (iii) Average current of thyristor. (4) | 2 | Understanding | CO5 |
| 5. | (i) Explain about the construction and working principles of HVDC Systems and also explain about its types (7) (ii) Explain about the working of Welding and its effects (6) | 2 | Understanding | CO5 |
| 6. | With the aid of circuit diagram and waveform explain the operation of power factor control in Ac voltage regulator. (13) | 2 | Understanding | CO5 |
| 7. | Explain with circuit diagram and waveform the principle of operation of three phase AC voltage controller with neat diagram. (13) | 2 | Understanding | CO5 |
| 8. | Design a converter circuit for FACTS Devices and explain the operation with a neat diagram. (13) | 3 | Applying | CO5 |
| 9. | Explain TRIAC triggering concept with positive and negative gate pulse triggering. (13) | 3 | Applying | CO5 |
| 10. | Explain various configurations of SCR based single phase controller. (13) | 3 | Applying | CO5 |

| PART - C | | | | |
|-----------------|-------------------------------------------------------------------------|---|-----------|-----|
| 1. | Explain various configuration of SCR based three phase controller. (15) | 4 | Analysing | CO5 |
| 2. | Explain TRIAC based single phase controller. (15) | 4 | Analysing | CO5 |

Course Outcomes:

| Cos | Course Outcome |
|------------|--------------------------------------------------------------------------------------------------------------------------|
| CO1 | Understand the operation of semiconductor devices and dynamic characteristics and to design & analyze the low power SMPS |
| CO2 | Analyze the various uncontrolled rectifiers and design suitable filter circuits |
| CO3 | Analyze the operation of the n-pulse converters and evaluate the performance parameters |
| CO4 | Understand various PWM techniques and apply voltage control and harmonic elimination methods to inverter circuits. |
| CO5 | Understand the operation of AC voltage controllers and its applications. |