



**ST. ANNE'S COLLEGE OF ENGINEERING AND TECHNOLOGY**

(Approved by AICTE, New Delhi. Affiliated to Anna University, Chennai)

ANGUCHETTYPALAYAM, PANRUTI – 607 106.

**DEPARTMENT OF MECHANICAL ENGINEERING**

**BE 3251 - Basic Electrical and Electronics Engineering**

II SEMESTER

Prepared by

Mrs. J. Arul Martinal, AP/EEE

## Unit I - ELECTRICAL CIRCUITS

### PART A

#### 1. State Ohm's law. (DEC 14)

Ohm's law states that the voltage ( $v$ ) across a resistor is directly proportional to the current ( $i$ ) flowing through the resistor, at constant temperature. ie,  $v \propto i$ ,  $v = iR$ , where  $R$  is the resistance ( $\Omega$ ).

#### 2. State Kirchoff's Current law. (MAY 13)

**KCL** (Kirchoff's Current Law) states that the algebraic sum of currents entering a node (or a closed boundary) is zero. (or) The sum of the currents entering a node is equal to the sum of the currents leaving the node.

#### 3. State Kirchoff's Voltage law. (MAY 13)

**KVL** (Kirchoff's Voltage Law) states that the algebraic sum of all voltages around a closed path (or loop) is zero. (or) Sum of voltage drop = Sum of voltage rise.

#### 4. An Electric iron is rated 1000W, 240V. Find the current drawn & resistance of the heating element.

$$P = V^2/R; R = 240^2/1000 = 57.6 \quad \text{and} \quad I = V/R = 240/57.6 = 4.166 \text{ A}$$

#### 5. Define i) charge ii) electric current iii) power iv) network & v) circuit.

**i) Charge:** Charge is an electrical property of the atomic particles of which matter consists, measured in coulombs(C).

**ii) Electric current** is the time rate of change of charge, measured in amperes(A).  $i = dq/dt$

A direct current (DC) is a current that remains constant with time.

An alternating current (AC) is a current that varies sinusoidally with time

**iii) Power** is the time rate of expending or absorbing energy, measured in watts(w).  $p = dw/dt$   $p$ - Power in watts(w);  $w$ - energy in joules (J);  $t$  - time in seconds (S); (or)  $p = v i$ ,  $v$  - Voltage in volts(V);  $i$  - current in amperes(A);

**iv) Network:** The inter connection of two or more simple circuit elements forms an electrical network.

**v) Circuit :** If the network contains at least one closed path, it is an electric circuit.

#### 6. Define: Node (OR) Junction, Tree & branch

A Node is a point in the network where two or more circuit elements are connected.

**Tree**

A Tree is a complete path including all the nodes.

**Branch**

A branch is a part of the circuit which lies between two junction points.

#### 7. Write down the expression of equivalent resistance for 'n' – number of resistors in series connection.

For 'n' resistors connected in series, the equivalent resistance is given by,

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

#### 8. Write down the expression of equivalent resistance for 'n'- number of resistors in parallel connection.

For 'n' resistors connected in parallel, the equivalent resistance is given by,

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$


#### 9. Write the Algorithm for Nodal Analysis.

Select a node as the reference node. Assign voltages  $V_1, V_2, \dots, V_{n-1}$  to the remaining  $n-1$  nodes. Apply KCL to each of the  $n-1$  nodes. Solve the resulting simultaneous equations to obtain the unknown node voltages.


**10. Write the Algorithm for Mesh Analysis. (DEC, '12)**

Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes. Apply KVL to each of the  $n$  meshes. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

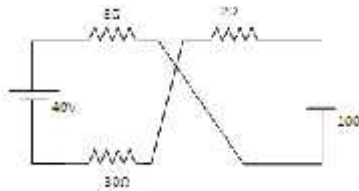**11. Apply KVL and solve (ans:  $I=3.54$ )**



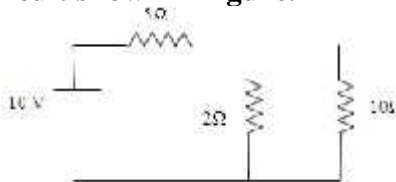**12. Write the Mesh equation for the circuit shown in figure.**



Ans:  $7i_1 - 2i_2 = 10$

$2i_1 - 12i_2 = 0$

**13. Distinguish between a Loop & Mesh of a circuit (DEC, '10)**

The closed path of a network is called a Loop. An elementary form of a loop which cannot be further divided is called a mesh. In other words Mesh is closed path does not contain an other loop within it.

**14. State Thevenins theorem. (NOV 14)**

It states that any linear bilateral network can be replaced by a single current source  $V_{TH}$ , in series with single impedance  $Z_{th}$

**15. State Norton's theorem**

It states that any linear bilateral network can be replaced by a single current source, in parallel with single impedance  $Z_{th}$ .

**16. State maximum power transfer theorem.**

Max power is transferred to load impedance if the load impedance is the complex conjugate of the source impedance.

**17. Sate superposition theorem.**

It states that the response of a linear circuit with multiple sources is given by algebraic sum of response due to individual sources acting alone.

**18. State the steps to solve the super position theorem.**

- Take only one independent voltage or current source.
- Obtain the branch currents.
- Repeat the above for other sources.
- To determine the net branch current just add the current obtained above.

**19. State the steps to solve the Thevenin's Theorem**

- Remove the load resistance and find the open circuit voltage  $V_{oc}$
- Deactivate the constant sources (fro voltage source remove it by internal resistance & for current source delete the source by OC) and find the internal resistance ( $R_{TH}$ ) of the source side looking through the open circuited load terminals
- Obtain the thevenin's equivalent circuit by connecting  $V_{OC}$  in series with  $R_{TH}$
- Reconnect the load resistance across the load terminals.

## 20. State the steps to solve the Norton's theorem.

- Remove the load resistor and find the internal resistance of the source N/W by deactivating the constant source.
- Short the load terminals and find the short circuit current
- Norton's equivalent circuit is drawn by keeping  $R_{TH}$  in parallel with  $I_{SC}$


$$I_L = (I_{sc} \cdot R_{th}) / (R_{th} + R_L)$$

## 21. Write some applications of maximum power transfer theorem.

- Power amplifiers
- Communication system
- Microwave transmission

# PART B
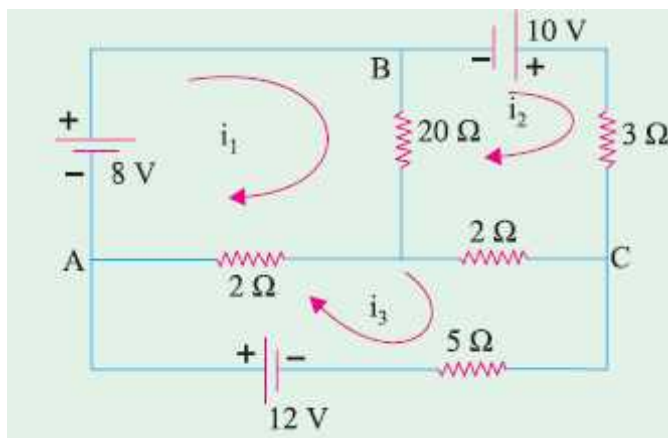
## 1. Determine current in 5ohm resistor by any one method.



### Solution.

Matrix-method for **Mesh analysis** can be used. Mark three loops as shown, in Fig. Resistance-matrix should be evaluated for current in 5-ohm resistor. Only,  $i_3$  is to be found.

$$R_{11} = 3, R_{22} = 6, R_{33} = 9 \quad R_{12} = 1, R_{23} = 2, R_{13} = 2$$


Voltage-source will be a column matrix with entries serially as : + 8 Volts, + 10 Volts, + 12 Volts.

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ -1 & 6 & -2 \\ -2 & -2 & 9 \end{vmatrix} = 3 \times (54 - 4) + 1(-9 - 4) - 2(2 + 12) = 109$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 8 \\ -1 & 6 & 10 \\ -2 & -2 & 12 \end{vmatrix} = 396$$

$$i_3 = \Delta_3 / \Delta = 396 / 109 = 3.633 \text{ amp.}$$

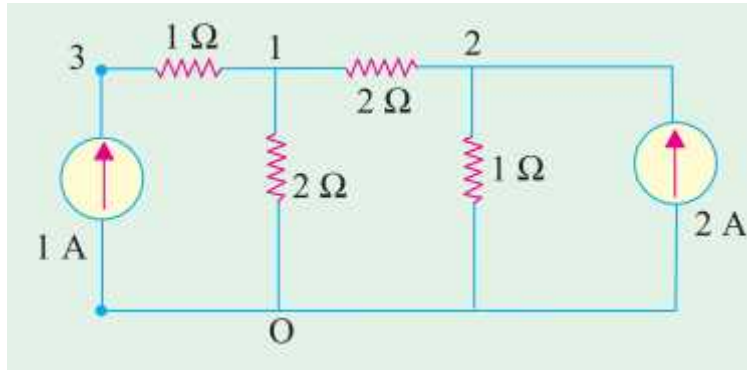2. Determine the voltages 1 and 2 of the network in Fig. by nodal analysis.



**Solution.** Write the conductance matrix for the network, with nodes numbered as 1, 2, 4 as shown.

$$g_{11} = 1 + 0.5 + 0.5 = 2 \text{ mho}, \quad g_{22} = 1 + 0.5 = 1.5 \text{ mho},$$

$$g_{33} = 1 \text{ mho}, \quad g_{12} = 0.5 \text{ mho}, \quad g_{23} = 0, \quad g_{13} = 1 \text{ mho}$$

$$\Delta = \begin{vmatrix} 2 & -0.5 & -1 \\ -0.5 & 1.5 & 0 \\ -1 & 0 & 1.0 \end{vmatrix} = 1.25, \quad \Delta_1 = \begin{vmatrix} 0 & -0.5 & -1 \\ 2 & 1.5 & 0 \\ 1 & 0 & 1 \end{vmatrix} = 2.5$$


$$\Delta_2 = \begin{vmatrix} 2 & 0 & -1 \\ -0.5 & 2 & 0 \\ -1 & 1 & 1.0 \end{vmatrix} = 2.5$$

This gives  $V_1 = \Delta_1/\Delta = 2.50/1.25 = 2$  Volts

And  $V_2 = \Delta_2/\Delta = 2.50/1.25 = 2$  Volts

It means that the 2-ohm resistor between nodes 1 and 2 does not carry current.

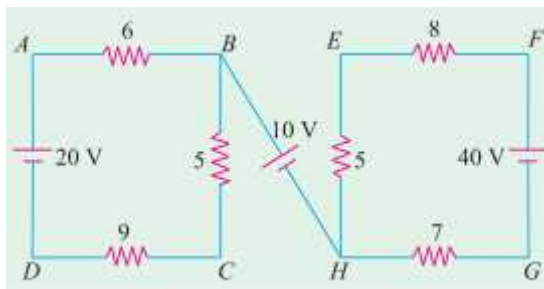3. For the circuit shown in Fig, find VCE and VAG



Consider the two battery circuits of Fig. separately. Current in the 20 V battery circuit ABCD is  $20/(6 + 5 + 9) = 1\text{A}$ . Similarly, current in the 40 V battery circuit EFGH is  $= 40/(5 + 8 + 7) = 2\text{A}$ . Voltage drops over different resistors can be found by using Ohm's law.

i.e. voltage of point  $C$  with respect to point  $E$ , we will start from point  $E$  and go to  $C$  via points  $H$  and  $B$ . We will find the algebraic sum of the voltage drops met on the way from point  $E$  to  $C$ . Sign convention of the voltage drops and battery e.m.fs. would be the same as discussed in Art. 2.3. For finding  $V_{CE}$

$$\therefore V_{CE} = (-5 \times 2) + (10) - (5 \times 1) = -5V$$

The negative sign shows that point  $C$  is negative with respect to point  $E$ .

$$V_{AG} = (7 \times 2) + (10) + (6 \times 1) = 30 V.$$

The positive sign shows that point  $A$  is at a positive potential of 30 V with respect to point  $G$ .

**4. State and explain Kirchhoff's laws. Determine the current supplied by the battery in the circuit shown in Fig.**

**Solution.** Let the current distribution be as shown in the figure. Considering the close circuit  $ABCA$  and applying Kirchhoff's Second Law, we have

$$-100x - 300z + 500y = 0$$

$$\text{or } x - 5y + 3z = 0 \quad \dots(i)$$

Similarly, considering the closed loop  $BCDB$ , we

have

$$-300z - 100(y + z) + 500(x - z) = 0$$

$$\text{or } 5x - y - 9z = 0 \quad \dots(ii)$$

Taking the circuit  $ABDEA$ , we get

$$-100x - 500(x - z) + 100 - 100(x + y) = 0$$

$$\text{or } 7x + y - 5z = 1 \quad \dots(iii)$$

The value of  $x$ ,  $y$  and  $z$  may be found by solving the above three simultaneous equations or by the method of determinants as given below :

Putting the above three equations in the matrix form, we have

$$\begin{bmatrix} 1 & -5 & 3 \\ 5 & -1 & -9 \\ 7 & 1 & -5 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 1 & -5 & 3 \\ 5 & -1 & -9 \\ 7 & 1 & -5 \end{bmatrix} = 240, \Delta_1 = \begin{bmatrix} 0 & -5 & 3 \\ 0 & -1 & -9 \\ 1 & 1 & -5 \end{bmatrix} = 48$$

$$\Delta_2 = \begin{bmatrix} 1 & 0 & 3 \\ 5 & 0 & -9 \\ 7 & 1 & -5 \end{bmatrix} = 24, \Delta_3 = \begin{bmatrix} 1 & -5 & 0 \\ 5 & -1 & 0 \\ 7 & 1 & 1 \end{bmatrix} = 24$$

$$\therefore x = \frac{48}{240} = \frac{1}{5} \text{ A}; y = \frac{24}{240} = \frac{1}{10} \text{ A}; z = \frac{24}{240} = \frac{1}{10} \text{ A}$$

Current supplied by the battery is  $x + y = 1/5 + 1/10 = 3/10 \text{ A}$ .


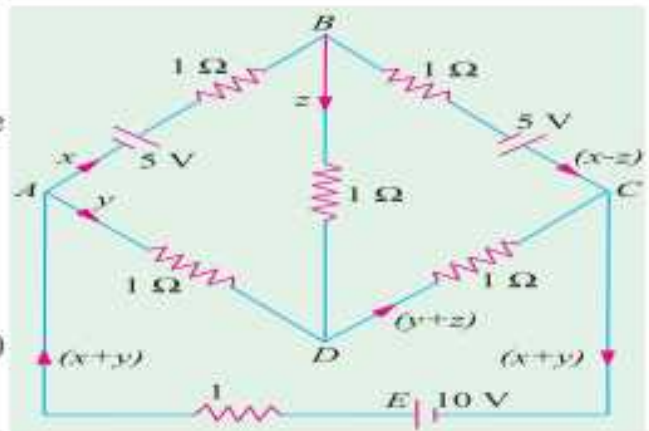


Fig. 2.12 A

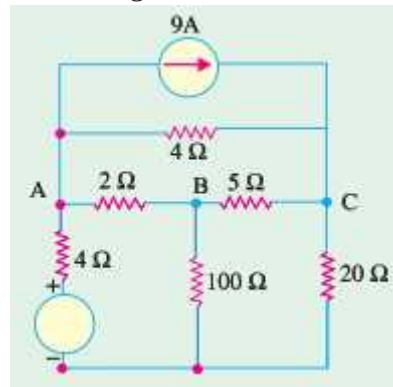5. Use nodal analysis to determine the voltage across 5 ohm resistance and the current in the 12 V source.



**Solution.** Transform the 12-volt and 4-ohm resistor into current-source and parallel resistor.

Mark the nodes  $O$ ,  $A$ ,  $B$  and  $C$  on the diagram. Self-and mutual conductance terms are to be written down next.

$$\text{At } A, G_{aa} = 1/4 + 1/2 + 1/4 = 1 \text{ mho}$$

$$\text{At } B, G_{bb} = 1/2 + 1/5 + 1/100 = 0.71 \text{ mho}$$

$$\text{At } C, G_{cc} = 1/4 + 1/5 + 1/20 = 0.50 \text{ mho}$$

$$\text{Between } A \text{ and } B, G_{ab} = 0.5 \text{ mho,}$$

$$\text{Between } B \text{ and } C, G_{bc} = 0.2 \text{ mho,}$$

$$\text{Between } A \text{ and } C, G_{ac} = 0.25 \text{ mho.}$$

Current Source matrix : At node  $A$ , 3 amp incoming and 9 amp outgoing currents give a net outgoing current of 6 amp. At node  $C$ , incoming current = 9 amp. At node  $B$ , no current source is

connected. Hence, the current-source matrix is : 
$$\begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

The potentials of three nodes to be found are :  $V_A, V_B, V_C$

$$\begin{bmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0.71 & -0.20 \\ -0.25 & -0.20 & 0.5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

For evaluating  $V_A, V_B, V_C$ , following steps are required.

$$\Delta = \begin{vmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0.71 & -0.20 \\ -0.25 & -0.20 & 0.5 \end{vmatrix} = 1 \times (0.71 \times 0.5 - 0.04) + 0.5(-0.25 - 0.05) - 0.25(0.1 + 0.71 \times 0.25)$$

$$= 0.315 - 0.15 - 0.069375 = 0.095625$$

$$\Delta_a = \begin{vmatrix} -6 & -0.5 & -0.25 \\ -0.5 & 0.71 & -0.20 \\ 9 & -0.20 & 0.5 \end{vmatrix} = +0.6075$$

$$\Delta_b = \begin{vmatrix} 1 & -6 & -0.25 \\ -0.5 & 0 & -0.20 \\ -0.25 & 9 & 0.50 \end{vmatrix} = 1.125$$

$$\Delta_c = \begin{vmatrix} 1 & -0.5 & -6 \\ -0.5 & 0.71 & 0 \\ -0.25 & -0.20 & 9 \end{vmatrix} = 2.2475$$

$$V_A = \Delta_a / \Delta = +0.6075 / 0.095625 = 6.353 \text{ volts}$$


$$V_B = \Delta_b / \Delta = 1.125 / 0.095625 = 11.765 \text{ volts}$$

$$V_C = \Delta_c / \Delta = 2.2475 / 0.095625 = 23.503 \text{ volts}$$

Hence, voltage across 5-ohm resistor =  $V_C - V_B = 11.765 - 1.283 = 10.482$  volts. Obviously,  $B$  is positive w.r. to  $A$ . From these node potentials, current through 100-ohm resistor is 0.118 amp; (i) current through 20 ohm resistor is 1.294 amp.




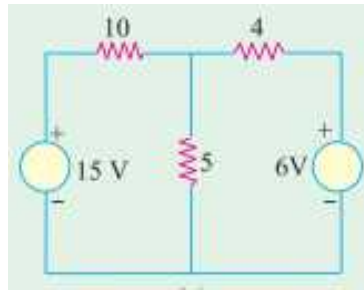6. State Thevenin's theorem and give a proof. Apply this theorem to calculate the current through the 4 Ω resistor of the circuit of Fig.



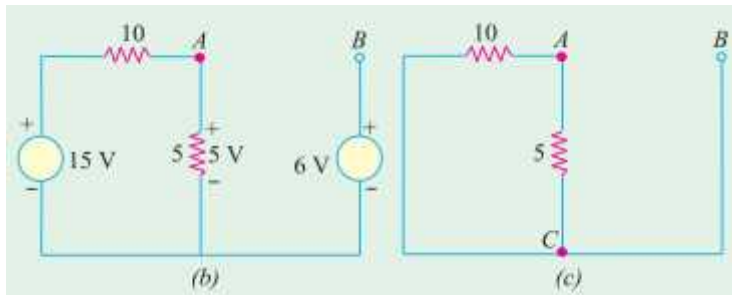**Solution.**

As shown in Fig. 2.130 (b), 4ohm resistance has been removed thereby open-circuiting the terminals A and B. We will now find  $V_{AB}$  and  $R_{AB}$  which will give us  $V_{th}$  and  $R_{th}$  respectively. The potential drop across 5 Ω resistor can be found with the help of voltage-divider rule. Its value is  $= 15 \times 5/(5 + 10) = 5 \text{ V}_{th}$



For finding  $V_{AB}$ , we will go from point B to point A in the clockwise direction and find the algebraic sum of the voltages met on the way.

$$\therefore V_{AB} = -6 + 5 = -1 \text{ V.}$$

It means that point A is negative with respect to point E, or point B is at a higher potential than point A by one volt.

In Fig. 2.130 (c), the two voltage source have been short-circuited. The resistance of the network as viewed from points A and B is the same as viewed from points A and C.

$$\therefore R_{AB} = R_{AC} = 5 \parallel 10 = 10/3 \Omega$$

Thevenin's equivalent source is shown in Fig. 2.131 in which 4

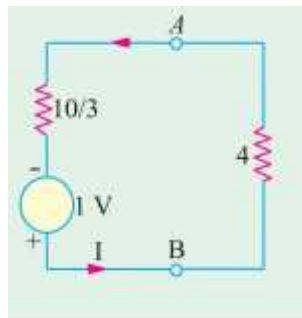



Fig. 2.131

Ω resistor has been joined back across terminals A and B. Polarity of the voltage source is worth nothing.


$$\therefore I = \frac{1}{(10/3) + 4} = \frac{3}{22} = 0.136 \text{ A} \quad \text{From E to A}$$



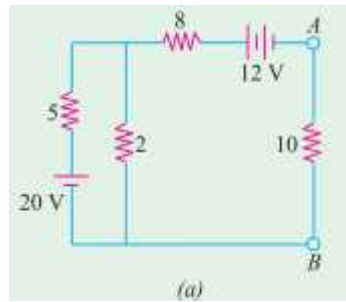7. For the circuit shown in Fig. 2.135 (a), calculate the current in the 10 ohm resistance. Use Thevenin's theorem only.



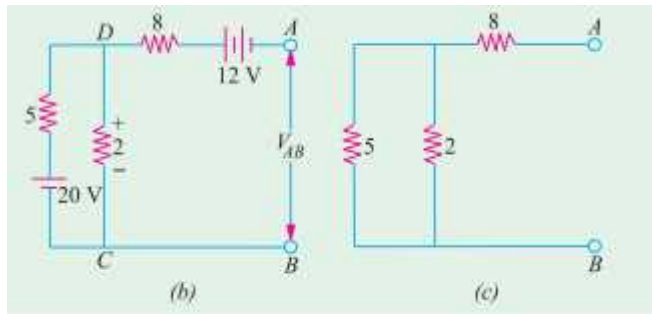**Solution.** When the 10 Ω resistance is removed, the circuit becomes as shown in Fig. 2.135 (b).



Now, we will find the open-circuit voltage  $V_{AB} = V_{th}$ . For this purpose, we will go from point B to point A and find the algebraic sum of the voltages met on the way. It should be noted that with terminals A and B open, there is no voltage drop on the 8 Ω resistance. However the two resistances of 5 Ω and 2 Ω are connected in series across the 20-V battery. As per voltage-divider rule, drop on 2 Ω resistance =  $20 \times \frac{2}{2 + 5} = 5.71$  V with the polarity as shown in figure. As per the sign convention of Art.

$$V_{AB} = V_{th} = + 5.71 - 12 = -6.29 \text{ V}$$

The negative sign shows that point A is negative with respect to point B or which is the same thing, point B is positive with respect to point A.

For finding  $R_{AB} = R_{th}$ , we replace the batteries by short-circuits as shown in Fig. 2.128 (c).

$$\therefore R_{AB} = R_{th} = 8 + 2 \parallel 5 = 9.43 \text{ } \Omega$$

Hence, the equivalent Thevenin's source with respect to terminals A and B is as shown in Fig. 2.136. When 10 Ω resistance is reconnected across A and B, current through it is  $I = 6.24 / (9.43 + 10) = 0.32 \text{ A}$ .


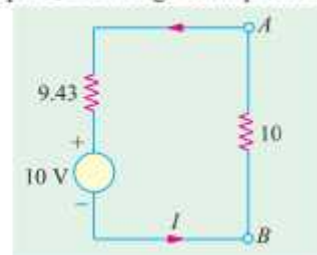



Fig. 2.136 (a)

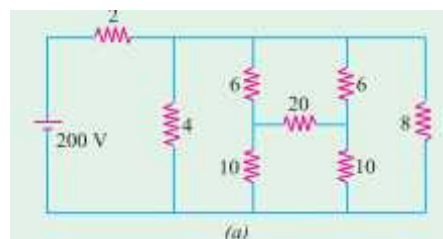8. State Norton's theorem and find current using Norton's theorem through a load of 8 Ω in the circuit shown in Fig. 2.191(a)



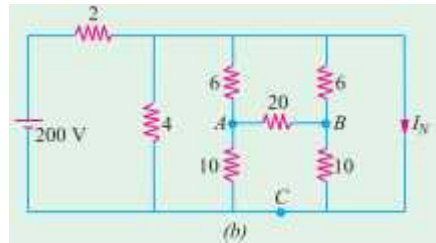**Solution.**


In Fig. 2.191 (b), load impedance has replaced by a short-circuit.  $I_{SC} = I_N = 200/2 = 100 \text{ A}$



Norton's resistance  $R_N$  can be found by looking into the open terminals of Fig. 2.191 (a). For this purpose  $\Delta ABC$  has been replaced by its equivalent Star. As seen,  $R_N$  is equal to  $8/7 \Omega$


Hence, Norton's equivalent circuit consists of a 100 A source having a parallel resistance of  $8/7\Omega$  as shown in Fig. 2.192 (c). The load current  $I_L$  can be found by using the Current Divider rule.

$$I_L = 100 \times \frac{(8/7)}{8 + (8/7)} = 12.5 \text{ A}$$

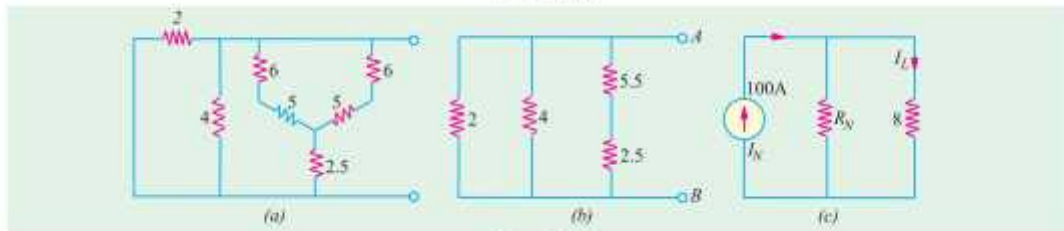


**Fig. 2.192**

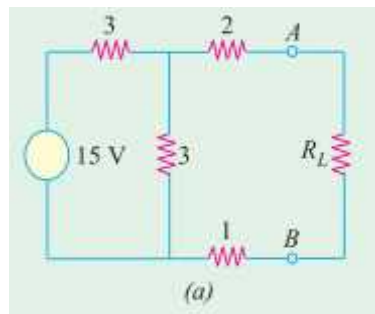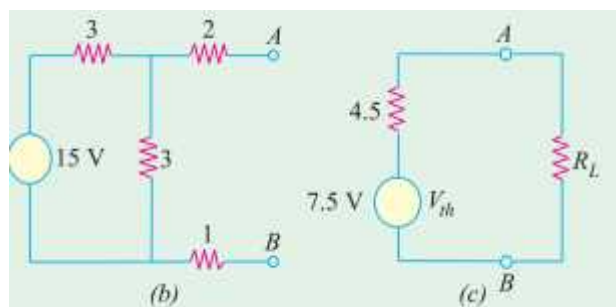**9. In the network shown in Fig. 2.231 (a), find the value of  $R$  such that maximum possible power will be transferred to  $R_L$ . Find also the value of the maximum power and the power supplied by source under these conditions.**




**Solution.** We will remove  $R_L$  and find the equivalent Thevenin's source for the circuit to the left of terminals  $A$  and  $B$ . As seen from Fig. 2.231 (b)  $V_{th}$  equals the drop across the vertical resistor of  $3\Omega$  because no current flows through  $2\Omega$  and  $1\Omega$  resistors. Since  $15 \text{ V}$  drops across two series resistors of  $3\Omega$  each,  $V_{th} = 15/2 = 7.5 \text{ V}$ . Thevenin's resistance can be found by replacing  $15 \text{ V}$  source with a short-circuit. As seen from Fig. 2.231 (b),  $R_{th} = 2 + (3 \parallel 3) + 1 = 4.5 \Omega$ . Maximum power transfer to the load will take place when  $R_L = R_{th} = 4.5 \Omega$




Maximum power drawn by  $R_L = V_{th}^2/4 \times R_L = 7.5^2/4 \times 4.5 = 3.125$  W,

Since same power is developed in  $R_{th}$ , power supplied by the source =  $2 \times 3.125 = 6.250$  W.

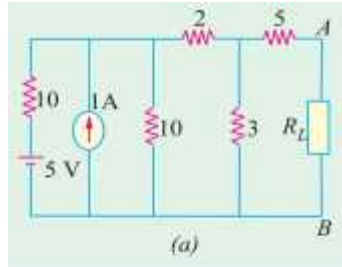10. In the circuit shown in Fig. 2.232 (a) obtain the condition from maximum power transfer to the load  $R_L$ . Hence determine the maximum power transferred.



**Solution**

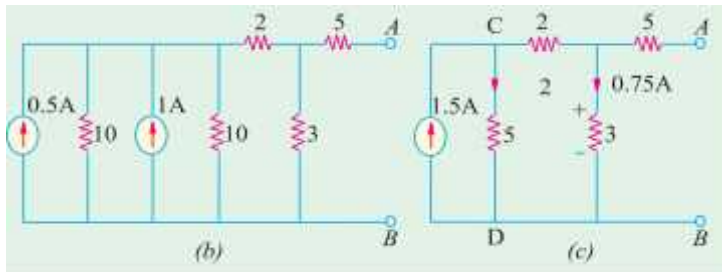

**Solution.** We will find Thevenin's equivalent circuit to the left of terminals  $A$  and  $B$  for which purpose we will convert the battery source into a current source as shown in Fig. 2.232 (b). By combining the two current sources, we get the circuit of Fig. 2.232 (c). It would be seen that open circuit voltage  $V_{AB}$  equals the drop over  $3\Omega$  resistance because there is no drop on the  $5\Omega$  resistance connected to terminal  $A$ . Now, there are two parallel path across the current source each of resistance  $5\Omega$ . Hence, current through  $3\Omega$  resistance equals  $1.5/2 = 0.75$  A. Therefore,  $V_{th} = 3 \times 0.75 = 2.25$  V with point  $A$  positive with respect to point  $B$ .

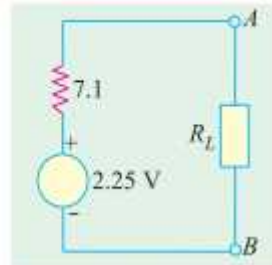


Fig. 2.233


For finding  $R_{th}$ , current source is replaced by an infinite resistance.

$$\therefore R_{th} = R_{th} = 5 + 3 \parallel (2 + 5) = 7.1 \Omega$$


The Thevenin's equivalent circuit along with  $R_L$  is shown in Fig. 2.233. As per Art. 2.30, the condition for MPT is that  $R_L = 7.1 \Omega$

$$\text{Maximum power transferred} = V_{th}^2 / 4R_L = 2.25^2/4 \times 7.1 = 0.178 \text{ W} = 178 \text{ mW.}$$

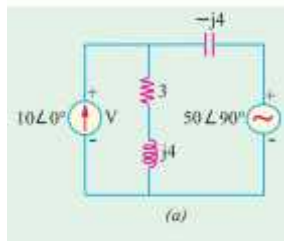11. Use Superposition theorem to find the voltage  $V$  in the network shown in Fig



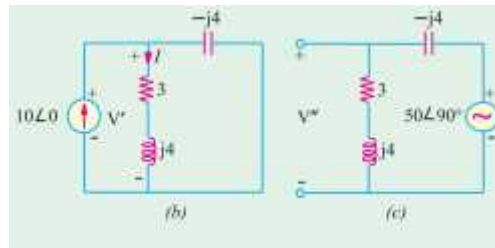**Solution.** When the voltage source is killed, the circuit becomes as shown in the Fig. 15.27 (b) Using current-divider rule,



$$I = 10\angle 0^\circ \times \frac{-j4}{(3+j4)-j4}, \text{ Now, } V' = I(3+j4)$$

$$\therefore V' = 10 \frac{-j4(3+j4)}{3} = 53.3 - j40$$

Now, when current source is killed, the circuit becomes as shown in Fig. 15.27 (c). Using the voltage-divider rule, we have

$$V'' = 50\angle 90^\circ \times \frac{(3+j4)}{(3+j4)-j4} = -66.7 + j50$$

$$\therefore \text{ drop } V = V' + V'' = 53.3 - j40 - 66.7 + j50 = -13.4 + j10 = 16.7 \angle 143.3^\circ V$$

## AC CIRCUITS PART A

### 1. Define Impedance.

Impedance is defined as the opposition of circuit to flow of alternating current. It is denoted by Z and its unit is ohms.

### 2. Define Resonance.

Resonance is defined as a phenomenon in which applied voltage and resulting current are in-phase. In other words, an AC circuit is said to be in resonance if it exhibits unity power factor condition, that means applied voltage and resulting current are in phase.

### 3. What is a Resonant frequency?

The frequency at which resonance occurs is called resonant frequency. i.e.  $X_L = X_C$ .

### 4. What is the series resonance?

The inductive reactance increases as the frequency increases ( $X_L = \omega L$ ) but the capacitive reactance decreases with frequency ( $X_C = 1/\omega C$ ). Thus inductive and capacitive reactances have opposite properties. So, for any LC combination there must be one frequency at which  $X_L = X_C$ . This case of equal and opposite reactance is called **series resonance**.

### 5. What is a parallel resonance?

The parallel circuit is said to be in resonance, when the power factor is unity. This is true when the imaginary part of the total admittance is zero.

### 6. Determine the power factor of a RLC series circuit with $R=5\text{ohm}$ , $X_L=8\text{ohm}$ and $X_C=12\text{ohm}$ . (JUNE, '12)

$$\cos\phi = \frac{R}{Z} = \frac{5}{\sqrt{5^2 + (8 - 12)^2}} = 0.78$$

### 7. What are the three types of power used in AC circuits?

i) Real or Active or True power  $P=EI \cos\phi$  ii) Reactive power  $Q=EI \sin\phi$  iii) Apparent power  $S=EI$

### 8. Define Real power.

The actual power consumed in an AC circuits is called real power. And  $P=EI \cos\phi$

### 9. Define Reactive power.

The power consumed by the pure reactance ( $X_L$  or  $X_C$ ) in an AC circuit is called reactive power. The unit is VAR. and  $Q=EI \sin\phi$

### 10. Define Apparent power and Power factor.

The Apparent power (in VA) is the product of the rms values of voltage and current.  $S = V_{\text{rms}} I_{\text{rms}}$

The Power factor is the cosine of the phase difference between voltage and current. It is also the cosine of the load impedance. And Power factor =  $\cos\phi$

The pf is lagging if the current lags voltage (inductive load) and is leading when the current leads voltage (capacitive load).

### 11. What is meant by Complex power?

Complex power (in VA) is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. As a complex quantity, its real part is real power, P and its imaginary part is reactive power, Q. and  $S = P + jQ$

### 12. What are the advantages of 3 phase circuits over single phase circuits?

1. Generation, transmission and distribution of 3 phase power is cheaper 2. More efficient 3. Uniform torque production occurs

### 13. State the relationship between line voltage & phase voltage and line current & phase current of a 3 phase delta connected system.

$$V_{\text{ph}} = V_L ; I_{\text{ph}} = I_L / \sqrt{3}$$

### 14. State the relationship between line voltage & phase voltage and line current & phase current of a 3 phase star connected system.

$$V_{\text{ph}} = V_L / \sqrt{3}; I_{\text{ph}} = I_L$$

### 15. Write the expression for the instantaneous values of emfs in a 3 phase circuit.

$$V_R = V_m \sin \omega t; V_Y = V_m \sin (\omega t - 120^\circ); V_B = V_m \sin (\omega t - 240^\circ)$$


**16. Give some method available for measuring three-phase power.**

i. Single wattmeter method. 2. Two-wattmeter method. 3. Three-wattmeter method.

**17. A star connected load has  $6 + j8$  ohm impedance per phase. Determine the line current if it is connected to 400V, three phase, and 50Hz supply. Ans:  $Z_{ph} = 10 \angle 53.1^\circ / \text{ph}$ ,  $I_{ph} = 23.094 \text{ A} = I_L$ . (JUNE, '12)**

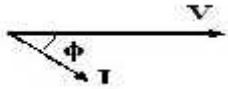**18. Define power factor.**

Power factor is defined as the cosine of angle between voltage and current. If  $\phi$  is the angle between voltage and current then  $\cos \phi$  is called as the power factor.



**19. Explain the concept of balanced load.**

The load is said to be balanced when magnitudes of all impedances  $Z_{ph1}$ ,  $Z_{ph2}$  and  $Z_{ph3}$  are equal and the phase angles of all of them are equal and of same nature either all inductive or all capacitive or all resistive.

**20. What is phase sequence?**

The order in which the voltage in the three phases reach their maximum positive values is called the phase sequence.

**21. Define Phasor and Phase angle.**

A sinusoidal wave form can be represented or in terms of a Phasor. A Phasor is a vector with definite magnitude and direction. From the Phasor the sinusoidal wave form can be reconstructed.

Phase angle is the angular measurement that specifies the position of the alternating quantity relative to a reference.



## Part B

1. An alternating voltage is given by  $V=230\sin314t$ . Calculate i) frequency, ii) maximum value, iii) average value, iv) RMS value. (N/D-2016)

**Solution:**

Frequency  $F = 1/T = 43.5 \text{ Hz}$

Maximum value  $V_m = V_{rms}/2 = 230/2 = 115 \text{ V}$



Average value: 35.6V

RMS value = Avg value / form factor =  $35.6 / 1.11 = 32.07 \text{ V}$

2. Explain about Single Phase Circuit with relevant diagrams.

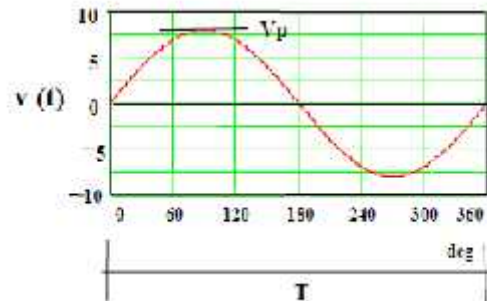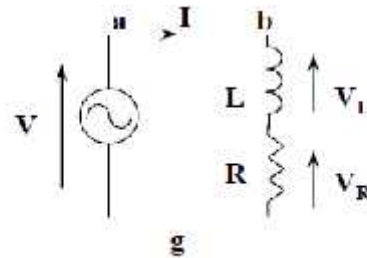**Single phase circuit components:**

- Voltage or current sources
- Impedances (resistance, inductance, and capacitance)
- The components are connected in series or in parallel.
- The figure shows a simple circuit where a voltage source (generator) supplies a load (resistance and inductance in series).



- The voltage source produces a sinusoidal voltage wave

$$v(t) = \sqrt{2} V_{rms} \sin(\omega t)$$

where:  $V_{rms}$  is the rms value of the voltage (volts)

$\omega$  is the angular frequency of the sinusoidal function (rad/sec)

$$\omega = 2\pi f = \frac{2\pi}{T} \text{ rad/sec} \quad f = \frac{1}{T} \text{ Hz}$$

$f$  is the frequency (60 Hz in USA, 50 Hz in Europe).

$T$  is the time period (seconds).


- The peak value (max value) of the voltage is  $V_p = \sqrt{2} V_{rms}$



The rms value is calculated by

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

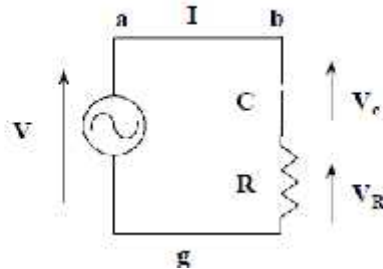- The voltage direction is indicated by an arrow from g to a. This means during the positive half cycle the potential of point a is larger than g.



- The current is also sinusoidal

$$i(t) = \sqrt{2} I_{\text{rms}} \sin(\omega t - \phi)$$

where:  $I_{\text{rms}}$  is the rms value of the current.

$\phi$  is the phase-shift between current and voltage.

The rms current is calculated by the Ohm's Law:

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

where:  $Z$  is the impedance.

- The impedances (in Ohms) are :

a) Resistance (R)

– b) Inductive reactance

$$X_L = \omega L$$

– c) Capacitive reactance

$$X_C = \frac{1}{\omega C}$$

### 3. Explain about Star and Delta connected three phase balanced circuits


#### Wye-Connected System

- The neutral point is grounded
- The three-phase voltages have equal magnitude.
- The phase-shift between the voltages is 120 degrees.

$$V_{an} = V \angle 0^\circ = V$$

$$V_{bn} = |V| \angle -120^\circ = |V| e^{-j120 \text{ deg}}$$

$$V_{cn} = |V| \angle -240^\circ = |V| e^{-j240 \text{ deg}}$$

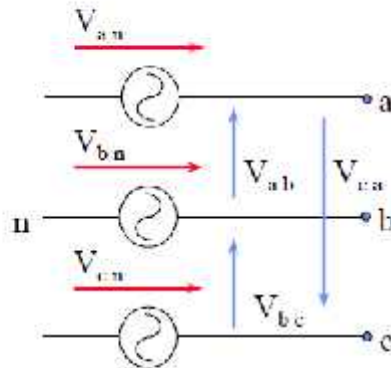


#### Wye-Connected System

- Line-to-line voltages are the difference of the phase voltages

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V e^{j30 \text{ deg}}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V e^{-j90 \text{ deg}}$$
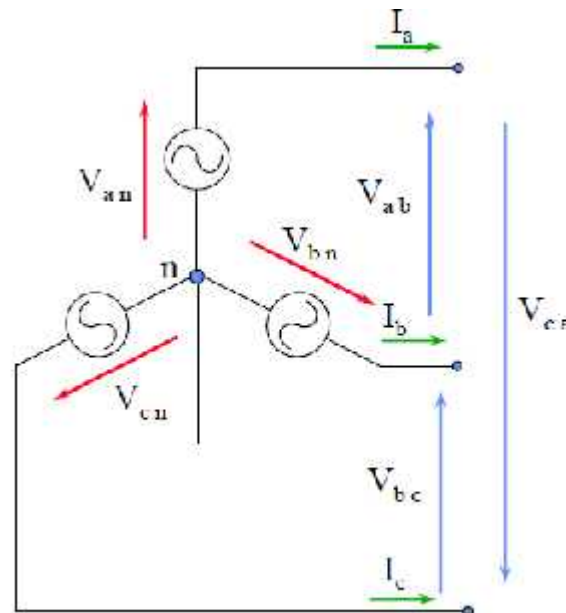
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V e^{j150 \text{ deg}}$$




#### Wye-Connected Loaded System

- The load is  $Z_a, Z_b, Z_c$
- Each phase voltage drives current through the load.
- The phase current expressions are:

$$I_a = \frac{V_{an}}{Z_a} \quad I_b = \frac{V_{bn}}{Z_b} \quad I_c = \frac{V_{cn}}{Z_c}$$

- The system has ground current defined as:

$$I_0 = I_a + I_b + I_c$$

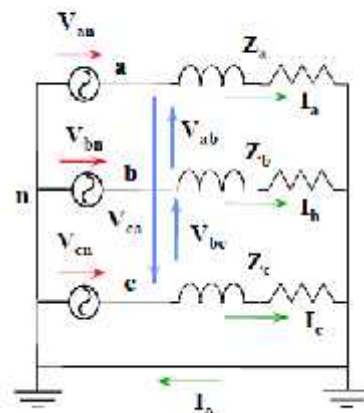


## Wye-Connected Loaded System

- If the load is balanced ( $Z_a = Z_b = Z_c$ ) then:

$$I_0 = I_a + I_b + I_c = 0$$

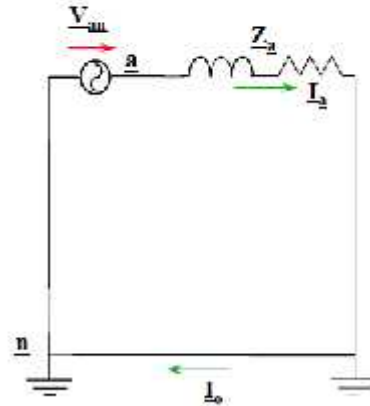- This case single phase equivalent circuit can be used (phase a, for instance, only)
- Phase b and c are eliminated



## Wye-Connected System with balanced load


- A single-phase equivalent circuit is used
- Only phase **a** is drawn, because the magnitude of currents and voltages are the same in each phase. Only the phase angles are different ( $-120^\circ$  phase shift)
- The supply voltage is the line to neutral voltage.
- The single phase loads are connected to neutral or ground.


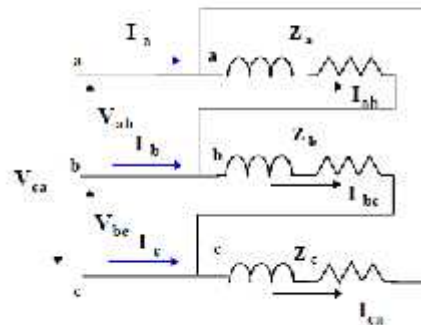
## Balanced Delta-Connected System

- The system has only one voltage : the line-to-line voltage ( $V_{LL}$ )
- The system has two currents :
  - line current
  - phase current
- The phase currents are:

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} \quad I_{bc} = \frac{V_{bc}}{Z_{bc}} \quad I_{ca} = \frac{V_{ca}}{Z_{ca}}$$



## Delta-Connected System

The line currents are:

$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$


$$I_c = I_{ca} - I_{bc}$$

- In a balanced case the line currents are:

$$I_a = \sqrt{3} I_{ab} e^{-i30\text{deg}}$$

or
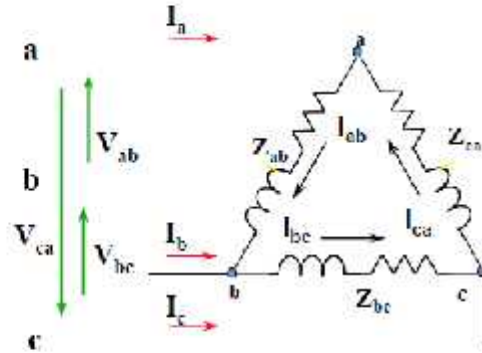
$$I_{\text{line}} = \sqrt{3} I_{\text{phase}} e^{-i30\text{deg}}$$



## Power Calculation

- The three phase power is equal the sum of the phase powers

$$P = P_a + P_b + P_c$$

- If the load is balanced:

$$P = 3 P_{\text{phase}} = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi)$$

- Wye system:  $V_{\text{phase}} = V_{\text{LN}}$   $I_{\text{phase}} = I_L$   $V_{\text{LL}} = \sqrt{3} V_{\text{LN}}$

$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi) = \sqrt{3} V_{\text{LL}} I_L \cos(\phi)$$


- Delta system:  $I_{\text{Line}} = \sqrt{3} I_{\text{phase}}$   $V_{\text{LL}} = V_{\text{phase}}$

$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi) = \sqrt{3} V_{\text{LL}} I_L \cos(\phi)$$
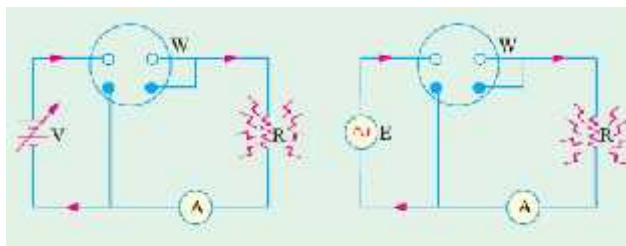
## 4. Write short notes on RMS Value of AC waveforms.

The r.m.s. value of an alternating current *is given by that steady (d.c.) current which when flowing through a given circuit for a given time produces the same heat as produced by the alternating current when flowing through the same circuit for the same time.*

It is also known as the *effective* or *virtual* value of the alternating current, the former term being used more extensively. For computing the r.m.s. value of symmetrical sinusoidal alternating currents, either mid-ordinate method or analytical method may be used, although for symmetrical but non sinusoidal waves, the midordinate method would be found more convenient






A simple experimental arrangement for measuring the equivalent d.c. value of a sinusoidal current is shown in Fig.11.15.

The two circuits have identical resistances but one is connected to battery and the other to a sinusoidal generator. Watt meters are used to measure heat power in each circuit. The voltage applied to each circuit is so adjusted that heat power production in each circuit is the same. In that case, the direct current will equal  $I_m/2$  which is called r.m.s. value of the sinusoidal current.

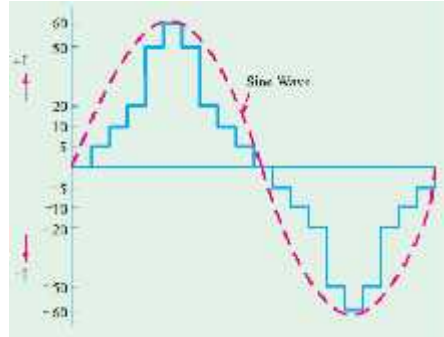5. Calculate the r.m.s. value, the form factor and peak factor of a periodic voltage having the following values for equal time intervals changing suddenly from one value to the next : 0, 5, 10, 20, 50, 60, 50, 20, 10, 5, 0, -5, -10 V etc. What would be the r.m.s value of sine wave having the same peak value ?

**Solution.** The waveform of the alternating voltage is shown in Fig. 11.19.



Obviously, it is not sinusoidal but it is symmetrical. Hence, though r.m.s value may be full one cycle, the average value has necessarily to be considered for half-cycle only, otherwise the symmetrical negative and positive half-cycles will cancel each other out.

$$\text{Mean value of } v^2 = \frac{0^2 + 5^2 + 10^2 + 20^2 + 50^2 + 60^2 + 50^2 + 20^2 + 10^2 + 5^2}{10} = 965 \text{ V}$$

$$\therefore \text{ r.m.s. value} = \sqrt{965} = 31 \text{ V (approx.)}$$

$$\text{Average value (half-cycle)} = \frac{0 + 5 + 10 + 20 + 50 + 60 + 50 + 20 + 10 + 5}{10} = 23 \text{ V}$$

$$\text{Form factor} = \frac{\text{r.m.s. value}}{\text{average value}} = \frac{31}{23} = 1.35. \text{ Peak factor} = 60/31 = 2 \text{ (approx.)}$$

$$\text{R.M.S. value of a sine wave of the same peak value} = 0.707 \times 60 = 42.2 \text{ V}$$

6. In a series circuit containing pure resistance and a pure inductance, the current and the voltage are expressed as :

$$i(t) = 5 \sin(314t + 2\pi/3) \text{ and } v(t) = 15 \sin(314t + 5\pi/6)$$

(a) What is the impedance of the circuit ? (b) What is the value of the resistance ? (c) What is the inductance in henrys ? (d) What is the average power drawn by the circuit ? (e) What is the power factor ?

**Solution.** Phase angle of current  $= 2\pi/3 = 2 \times 180^\circ/3 = 120^\circ$  and phase angle of voltage  $= 5\pi/6 = 5 \times 180^\circ/6 = 150^\circ$ . Also,  $Z = V_m/I_m = 3 \Omega$

Hence, current lags behind voltage by  $30^\circ$ . It means that it is an R-L circuit. Also  $314 = 2\pi f$  or  $f = 50 \text{ Hz}$ . Now,  $R/Z = \cos 30^\circ = 0.866$ ,  $R = 2.6 \Omega$ ;  $X_L/Z = \sin 30^\circ = 0.5$

$$\therefore X_L = 1.5 \, \Omega \quad 314L = 1.5, \quad L = 4.78 \, \text{mH}$$

$$(a) Z = 3 \, \Omega \quad (b) R = 2.6 \, \Omega \quad (c) L = 4.78 \, \text{mH}$$


$$(d) P = I^2 R = (5/\sqrt{2})^2 \times 2.6 = 32.5 \, \text{W} \quad (e) \text{p.f.} = \cos 30^\circ = 0.866 \, (\text{lag}).$$

## Unit II - ELECTRICAL MACHINES


### PART-A

1. Draw the circuit for various types of d.c motor. (N/D-2016)


#### Separately Excited DC Motor

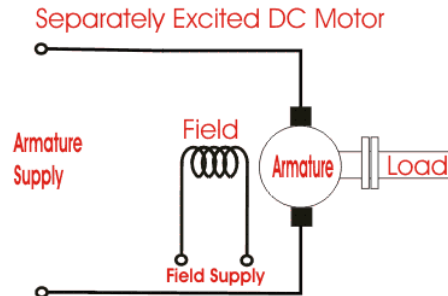


#### DC Shunt Motor

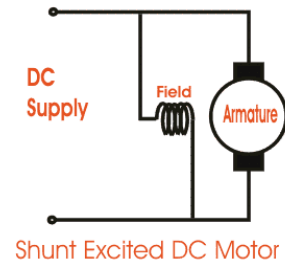

#### DC Series Motor

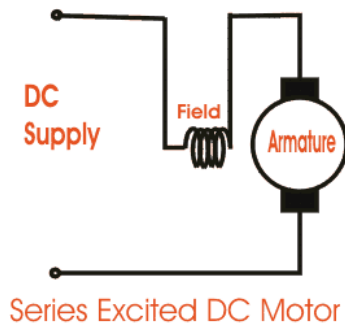

#### DC Compound Motor

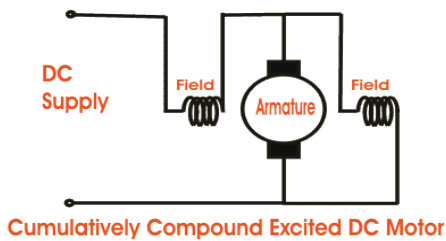

2. Define voltage regulation of transformer. (N/D-2016, M/J-2016)


The voltage regulation of the transformer is the percentage change in the output voltage from no-load to full-load.



### 3. Sketch the O.C.C of dc shunt generator.(M/J-2016)
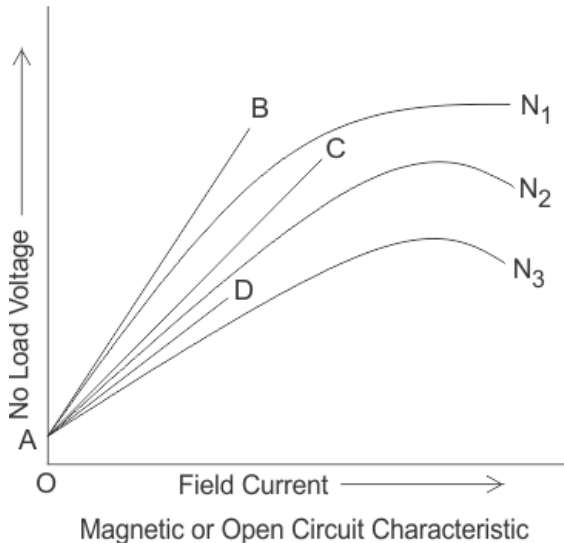
#### Critical Load Resistance of Shunt Wound DC Generator

This is the minimum external load resistance which is required to excite the shunt wound generator



### 4. Write down the EMF equation of a transformer..(M/J-2016)

$$E_1 = 4.44 \cdot N_1 \cdot f \cdot B_m \cdot A \text{ and } E_2 = 4.44 \cdot N_2 \cdot f \cdot B_m \cdot A$$

### 5. list out the types of induction motor.(N/D-2015)

#### Induction motor types:

- Polyphase cage rotor.
- Polyphase wound rotor.
- Two-phase servo motor.
- Single-phase induction motor.
- Polyphase synchronous motor.
- Single-phase synchronous motor.
- Hysteresis synchronous motor.

### 6. Give some application of D.C motor.(A/M-2015,N/D-2016)

**Shunt** :driving constant speed, lathes, centrifugal pumps, machine tools, blowers and fans, reciprocating pumps

**Series** :electric locomotives, rapid transit systems, trolley cars, cranes and hoists, conveyors

**Compound** :elevators, air compressors, rolling mills, heavy planners

### 7. Why a single phase induction motor does not self start?(A/M-2015,A/M-2017,N/D-2016)

When a single phase supply is fed to the single phase induction motor. Its stator winding produces a flux which only alternates along one space axis. It is not a synchronously revolving field, as in the case of a 2 or 3phase stator winding, fed from 2 or 3 phase supply.

### 8. Mention the application of DC generator?(A/M-2017)

- general lighting.

- Used to charge [battery](#) because they can be made to give constant output voltage.
- They are used for giving the excitation to the [alternators](#).
- used for small power supply.

**9. What is the significance of back EMF?(A/M-2017)**

- When the motor is running on no load, small torque is required to overcome the friction and windage losses. Therefore, the armature current  $I_a$  is small and the back emf is nearly equal to the applied voltage.
- If the motor is suddenly loaded, the first effect is to cause the armature to slow down. Therefore, the speed at which the armature conductors move through the field is reduced and hence the back emf  $E_b$  falls. The decreased back emf allows a larger current to flow through the armature and larger current means increased driving torque. Thus, the driving torque increases as the motor slows down. The motor will stop slowing down when the armature current is just sufficient to produce the increased torque required by the load.
- If the load on the motor is decreased, the driving torque is momentarily in excess of the requirement so that armature is accelerated. As the armature speed increases, the back emf  $E_b$  also increases and causes the armature current  $I_a$  to decrease. The motor will stop accelerating when the armature current is just sufficient to produce the reduced torque required by the load.

**10. Write the principle of DC Motor?(N/D-2015)**

Fleming's left hand rule to determine the direction of force acting on the armature conductors of DC motor. If a current carrying conductor is placed in a magnetic field perpendicularly, then the conductor experiences a force in the direction mutually perpendicular to both the direction of field and the current carrying conductor. Fleming's left hand rule says that if we extend the index finger, middle finger and thumb of our left hand perpendicular to each other, in such a way that the middle finger is along the direction of current in the conductor, and index finger is along the direction of magnetic field i.e. north to south pole, then thumb indicates the direction of created

**11. What is the main purpose of commutator and brushes?**

**Commutator:**

The commutator converts the alternating emf into unidirectional or direct emf.

**Brushes:**

The brushes collect the current from the commutator

**12. State the principle of operation of a transformer.**

Transformer operates on the principle of mutual induction between inductively coupled coils. When A.C source is connected to one coil flux is produced in the core which links both the coils. As per the Faraday's laws of electromagnetic induction EMF is induced in the secondary coil also. if the external circuit is closed power is supplied.

**13. Write down the EMF equation of a single phase transformer.**

EMF induced in primary,  $E_1 = 4.44 \phi f N_1$  volts where

$f$  = Frequency of supply main

$\phi$  = Flux linking both the primary and secondary winding

**14. Write any two differences between single phase and three phase transformers.**

i. Single phase transformer has two windings. Three phase transformer has six windings. ii. Single phase supply is directly connected across the single primary winding whereas the 3-phase transformer windings are connected in star or delta according to the design.

**15. Distinguish between induction motor and synchronous motor? (A/M 2015)**

- A three phase Synchronous motor is a doubly excited machine, whereas an induction motor is a single excited machine.
- The armature winding of the Synchronous motor is energized from an AC source and its field winding from a DC source. The stator winding of Induction Motor is energized from an AC source.
- Synchronous Motor always runs at synchronous speed, and the speed of the motor is independent of load, but an induction motor always runs less than the synchronous speed. If the load increased the speed of the induction motor decreases.
- The induction motor has self-starting torque whereas the synchronous motor is not self starting. It has to be run up to synchronous speed by any means before it can be synchronized to AC supply.

**16. What is the working principle of Synchronous generator?**

The principle of operation of synchronous generator is electromagnetic induction. If there exists a relative motion between the flux and conductors, then an emf is induced in the conductors.

**17. Write the EMF equation of an alternator? (N/D-2016)**

$$E = 4.44 \times f \Phi T_{ph} \text{ volts}$$

This is the basic e.m.f. equation for an induced e.m.f. per phase for full pitch, concentrated type of winding.

Where  $T_{ph}$  = Number of turns per phase

$$T_{ph} = Z_{ph} / 2$$

Total flux cut in one revolution is  $\Phi \times P$

Time taken for one revolution is  $60/N_s$  seconds.

$$\therefore e_{avg} \text{ per conductor} = \Phi P / (60/N_s) = \Phi (PN_s/60) \dots\dots\dots (1)$$

But  $f = PN_s/60$

$$\therefore PN_s/60 = 2f$$

**18. Define voltage regulation of the alternator?**

It is defined as the increase in terminal voltage when full load is thrown off, assuming field current and speed remaining the same.

$$\% \text{ reg} = [(E - V)/V] \times 100$$

Where E = no load terminal voltage      V = full load rated terminal voltage

**19. What is meant by armature reaction in Alternators?**

The interaction between flux set up by the current carrying armature and the main flux is defined as the armature reaction.

**20. Why a synchronous motor is a constant speed motor?**

Synchronous motor works on the principle of force developed due to the magnetic attraction established between the rotating magnetic field and the main pole field. Since the speed of rotating magnetic field is directly proportional to frequency the motor operates at constant speed.

**21. Name any two methods of starting synchronous motors**

- By an extra 3 phase cage induction motor
- By providing damper winding in pole phases
- By operating the pilot excitor as a dc motor

**22. State the principle of 3 phase IM?**

While starting, rotor conductors are stationary and they cut the revolving magnetic field

and so an emf is induced in them by electromagnetic induction. This induced emf produces a current if the circuit is closed. This current opposes the cause by Lenz's law and hence the rotor starts revolving in the same direction as that of the magnetic field.

**23. What type of single phase induction motor would you use for the following applications?** (i) Ceiling fan (ii) Wet grinder  
 Ceiling fan – capacitor start and run motor  
 Grinder – capacitor start motor

**PART-B**

**1. With a neat circuit diagram Explain the construction and principle of operation of DC Motor.**  
 (N/D-2016,N/D-2015,M/J-2017)

**DC MOTOR – INTRODUCTION:**

A machine that converts dc power into mechanical energy is known as dc motor. Its operation is based on the principle that when a current carrying conductor is placed in a magnetic field, the conductor experiences a mechanical force. The direction of the force is given by Fleming's left hand rule.

**WORKING OF DC MOTOR:**

There are different kinds of D.C. motors, but they all work on the same principles. When a permanent magnet is positioned around a loop of wire that is hooked up to a D.C. power source, we have the basics of a D.C. motor. In order to make the loop of wire spin, we have to connect a battery or DC power supply between its ends, and support it so it can spin about its axis.

To allow the rotor to turn without twisting the wires, the ends of the wire loop are connected to a set of contacts called the commutator, which rubs against a set of conductors called the brushes. The brushes make electrical contact with the commutator as it spins, and are connected to the positive and negative leads of the power source, allowing electricity to flow through the loop. The electricity flowing through the loop creates a magnetic field that interacts with the magnetic field of the permanent magnet to make the loop spin

**PRINCIPLES OF OPERATION:**

It is based on the principle that when a current-carrying conductor is placed in a magnetic field, it experiences a mechanical force whose direction is given by Fleming's Left- hand rule and whose magnitude is given by


$$\text{Force, } F = B I l \text{ newton}$$

Where,

B is the magnetic field in weber/m<sup>2</sup>

I is the current in amperes and

l is the length of the coil in meter

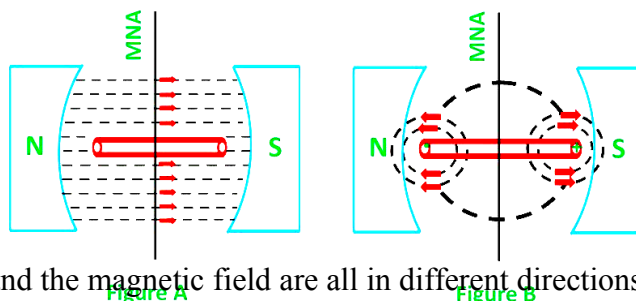

The force, current and the magnetic field are all in different directions. If an Electric current flows through two

copper wires that are between the poles of a magnet, an upward force will move one wire up and a downward force will move the other wire down.

## 2. Explain the construction, working principle of single phase Induction motor.(N/D-2016)

Single phase motors are very widely used in home, offices, workshops etc. as power delivered to most of the houses and offices is single phase. In addition to this, single phase motors are reliable, cheap in cost, simple in construction and easy to repair.


Single phase electric motors can be classified as:

1. Single phase induction motor (Split phase, Capacitor and shaded pole etc)
2. Single phase synchronous motor
3. Repulsion motor etc.

### Single Phase Induction Motor
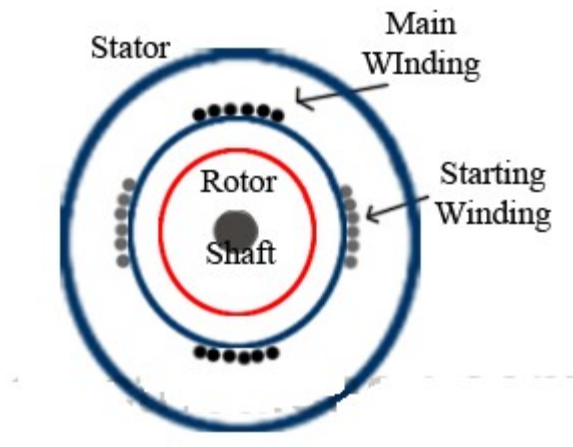
#### CONSTRUCTION:

Construction of a single phase induction motor is similar to the construction of three phase induction motor having squirrel cage rotor, except that the stator is wound for single phase supply. Stator is also provided with a 'starting winding' which is used only for starting purpose. This can be understood from the schematic of single phase induction motor at the left.



#### Working Principle Of Single Phase Induction Motor:

When the stator of a single phase motor is fed with single phase supply, it produces alternating flux in the stator winding. The alternating current flowing through stator winding causes induced current in the rotor bars (of the squirrel cage rotor) according to Faraday's law of electromagnetic induction.

This induced current in the rotor will also produce alternating flux. Even after both alternating fluxes are set up, the motor fails to start (the reason is explained below). However, if the rotor is given a initial start by external force in either direction, then motor accelerates to its final speed and keeps running with its rated speed. This behavior of a single phase motor can be explained by double-field revolving theory.


## 3. Describe various types self excited of DC generator with their circuit layout.(M/J-2016)

DC generators are classified based on their method of excitation. So on this basis there are two types of DC generators:-

Self excited DC generator can again be classified as 1) DC Series generator 2) DC Shunt generator and 3) DC Compound generator.
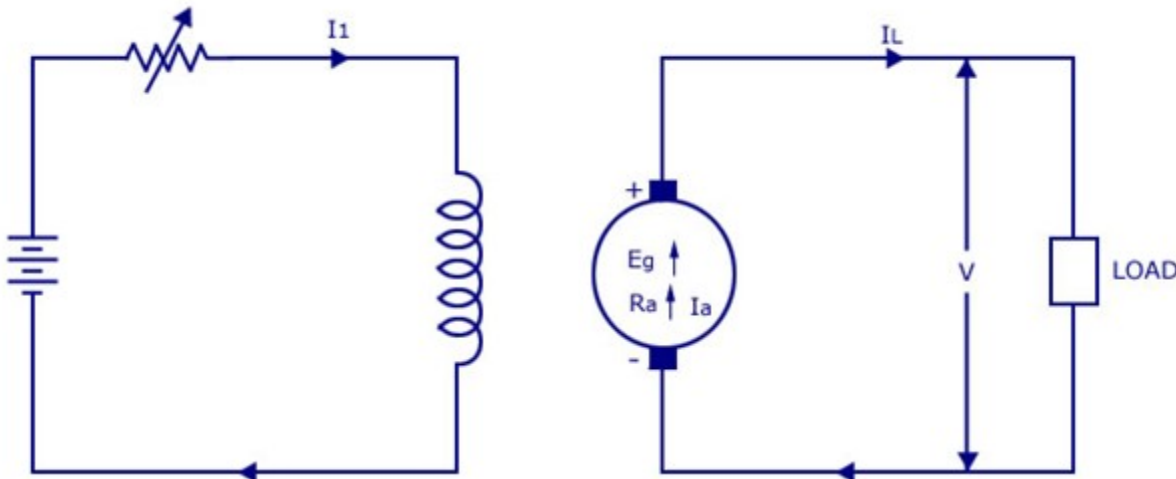
### 1. Separately excited DC generator

As you can guess from the name itself, this dc generator has a field magnet winding which is excited using a separate voltage source (like battery). You can see the representation in the below image. The output voltage depends on the speed of rotation of armature and field current. The higher the speed of rotation and current – the higher the output e.m.f




### 2. Self Excited DC Generator

These are generators in which the field winding is excited by the output of the generator itself. As described before – there are three types of self excited dc generators – they are 1) Series 2) Shunt and 3) Compound.

**A series DC generator** is shown below in fig (a) – in which the armature winding is connected in series with the field winding so that the field current flows through the load as well as the field winding. Field winding is a low resistance, thick wire of few turns. Series generators are also rarely used!

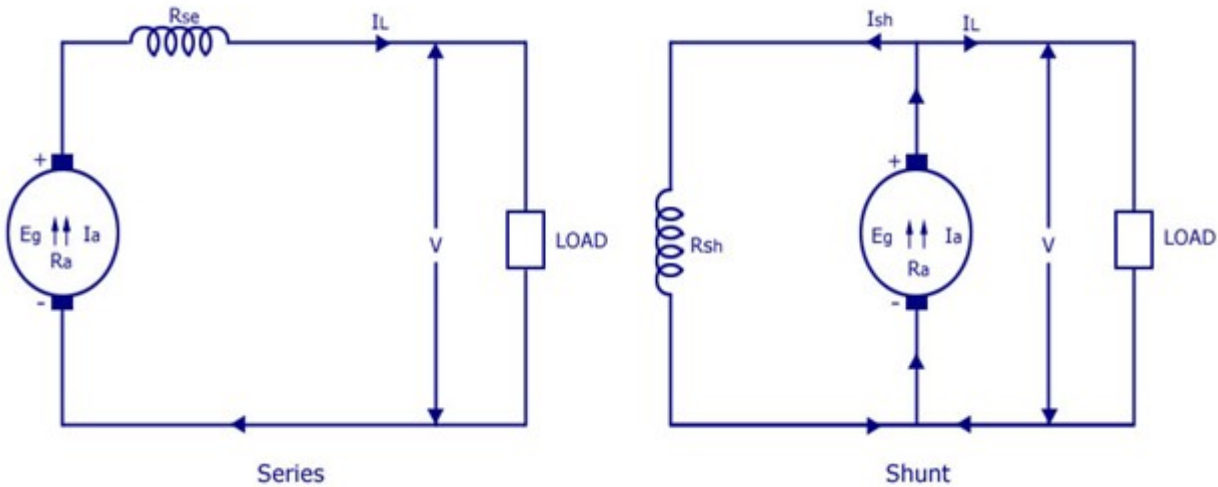
**A shunt DC generator** is shown in figure (b), in which the field winding is wired parallel to armature winding so that the voltage across both are same. The field winding has high resistance and more number of turns so that only a part of armature current passes through field winding and the rest passes through load.



A **compound generator** is shown in figure below. It has two field windings namely  $R_{sh}$  and  $R_{se}$ . They are basically shunt winding ( $R_{sh}$ ) and series winding ( $R_{se}$ ). Compound generator is of two types – 1) Short shunt and 2) Long shunt

**Short shunt:-** Here the shunt field winding is wired parallel to armature and series field winding is connected in series to the load. It is shown in fig (1)

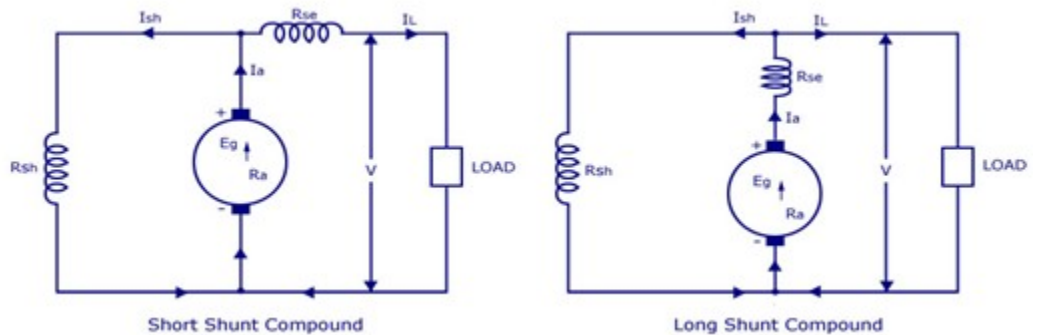**Long shunt:-** Here the shunt field winding is parallel to both armature and series field winding ( $R_{se}$  is wired in series to the armature). It is shown in figure (2)




#### 4. Explain the characteristics of dc shunt motor.(M/J-2016)

Characteristics of DC Shunt Motor:

The three important shunt characteristic curves are

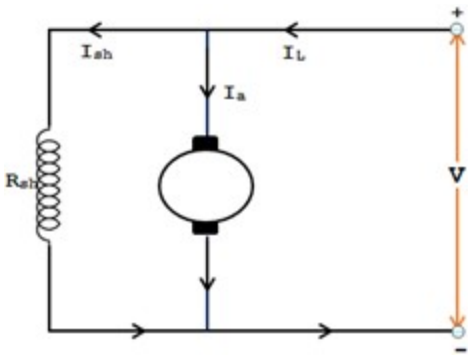1. Torque  $V_s$  Armature current characteristic ( $T_a/I_a$ )
2. Speed  $V_s$  Armature current characteristic ( $N/I_a$ )
3. Speed  $V_s$  Torque characteristic ( $N/T_a$ )






The fig above shows the circuit diagram of shunt motor. In this circuit the field winding is directly connected to the source voltage, so the field current  $I_{sh}$  and the flux in a shunt motor are constant.

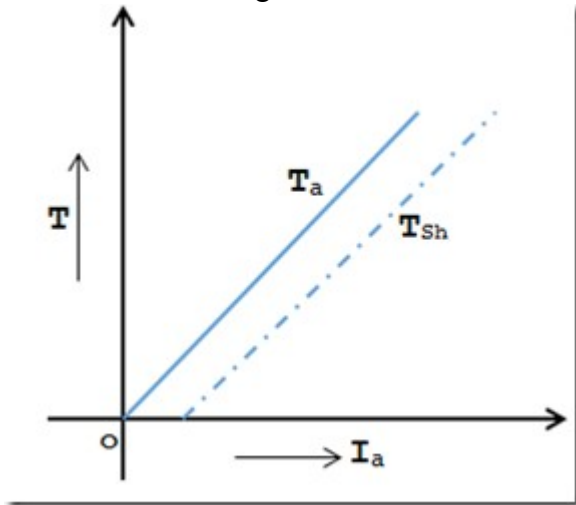
1. Torque  $V_s$  Armature current characteristic ( $T_a/I_a$ )

We know that in a DC Motor  $T_a \propto \Phi I_a$ . In this the flux  $\Phi$  is constant by ignoring the [armature reaction](#), since the motor is working from a continual source voltage.



Therefore the curve drawn between torque  $V_s$  armature current is a straight line transitory through the origin which is shown in fig. The shaft torque ( $T_{sh}$ ) is a smaller amount than armature torque and is shown in the fig by a dotted line. From this curve it is proved that to start a heavy load very large current is requisite. Hence the shunt DC motor should not be started at full load.

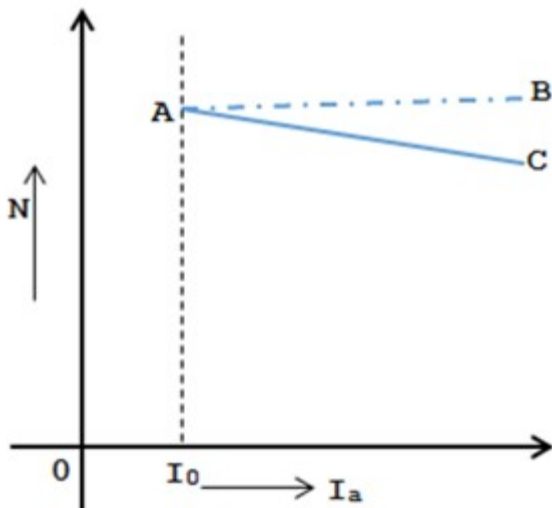
2. Speed  $V_s$  Armature current characteristic ( $N/I_a$ )



At normal condition the [back EMF](#)  $E_b$  and Flux  $\Phi$  both are constant in a DC Shunt motor. Hence the armature current differs and the speed of a [DC Shunt motor](#) will continue constant which is shown in the fig (dotted Line AB).

Whenever the shunt motor load is increased  $E_b = V - I_a R_a$  and flux reduces as a result drop in the armature resistance and armature reaction. On the other hand, back EMF reduces marginally more than that the speed of the shunt motor decreases to some extent with load.
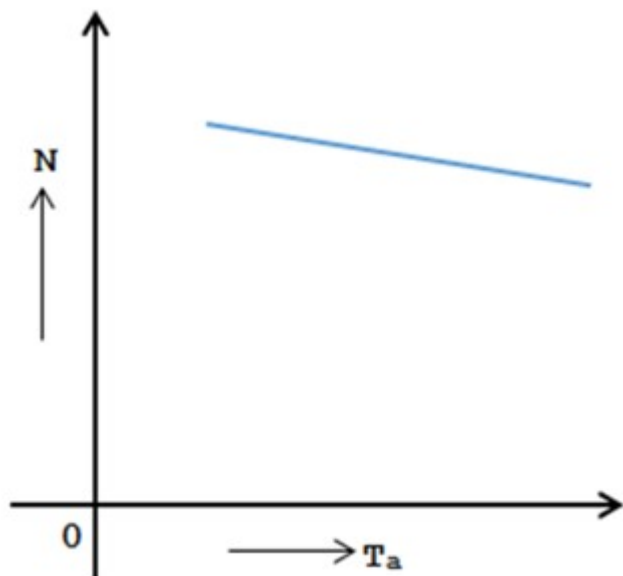
### 3. Speed $V_s$ Torque characteristic (N/ $T_a$ )



This curve is drawn between the speed of the motor and armature current with various amps as shown in the fig. From the curve it is understood that the speed reduces when the load torque increases.

With the above three characteristic it is clearly understood that when the shunt motor runs from no load to full load there is slight change in speed. Thus, it is essentially a constant speed motor. Since the armature torque is directly proportional to the armature current, the starting torque is not high

### 5. Explain the tests on a single phase transformer and develop an equivalent from the above tests. (M/J-2016)


#### 1. Open Circuit Test on Transformer

The connection diagram for open circuit test on transformer is shown in the figure. A [voltmeter](#), [wattmeter](#), and an [ammeter](#) are connected in LV side of the transformer as shown. The [voltage](#) at rated frequency is applied to that LV side with the help of a variac of variable ratio [auto transformer](#).

The HV side of the transformer is kept open. Now with the help of variac, applied voltage gets slowly increased until the voltmeter gives reading equal to the rated voltage of the LV side. After reaching at rated LV side voltage, all three instruments reading (Voltmeter, Ammeter and Wattmeter readings) are recorded.

The ammeter reading gives the no load current  $I_e$ . As no load current  $I_e$  is quite small compared to rated [current](#) of the [transformer](#), the [voltage drops](#) due to this current that can be taken as negligible. Since, voltmeter reading  $V_1$  can be considered equal to secondary induced voltage of the transformer, the input power during test is indicated by watt-meter reading. As the transformer is open circuited, there is no output, hence the input power here consists of core [losses in transformer](#) and copper loss in transformer during no load condition. But as said earlier, the no load current in the transformer is quite small compared to full load current, so copper loss due to the small no load current can be neglected. Hence, the wattmeter reading can be taken as equal to core losses in transformer. Let us consider wattmeter reading is  $P_o$ .

$$P_o = \frac{V_1}{R_m^2}$$

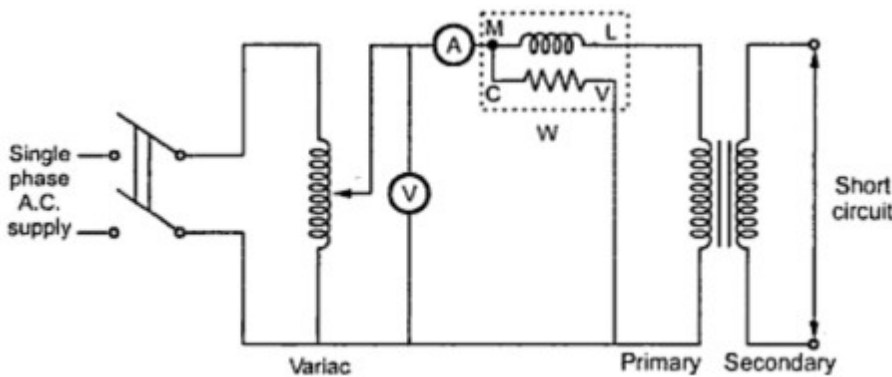


Therefore, if shunt branch reactance of transformer is  $X_m$ ,

$$\text{Then, } \left(\frac{1}{X_m}\right)^2 = \left(\frac{1}{Z_m}\right)^2 - \left(\frac{1}{R_m}\right)^2$$
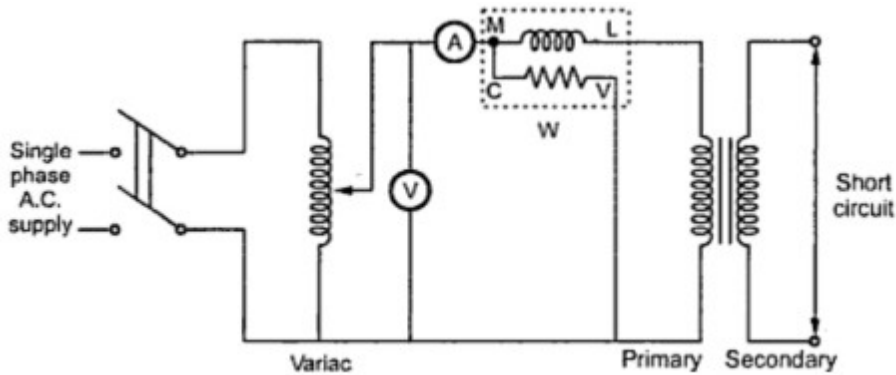
## 2. Short Circuit Test on Transformer:

The connection diagram for short circuit test on transformer is shown in the figure. A voltmeter, wattmeter, and an ammeter are connected in HV side of the transformer as shown. The voltage at rated frequency is applied to that HV side with the help of a variac of variable ratio [auto transformer](#).

The LV side of the transformer is short circuited. Now with the help of variac applied voltage is slowly increased until the ammeter gives reading equal to the rated current of the HV side. After reaching at rated current of HV side, all three instruments reading (Voltmeter, Ammeter and Watt-meter readings) are recorded. The ammeter reading gives the primary equivalent of full load current  $I_L$ . As the voltage applied for full load current in short circuit test on transformer is quite small compared to the rated primary voltage of the transformer, the core [losses in transformer](#) can be taken as negligible here.



Let's say, voltmeter reading is  $V_{sc}$ . The input power during test is indicated by watt-meter reading. As the transformer is short circuited, there is no output; hence the input power here consists of copper losses in transformer. Since, the applied voltage  $V_{sc}$  is short circuit voltage in the transformer and hence it is quite small compared to rated voltage, so core loss due to the small applied voltage can be neglected. Hence the wattmeter reading can be taken as equal to copper losses in transformer. Let us consider wattmeter reading is  $P_{sc}$ .

$$P_{sc} = R_e I_L^2$$

These values are referred to the HV side of transformer as because the test is conducted on HV side of transformer. These values could easily be referred to LV side by dividing these values with square of transformation ratio.

Therefore it is seen that the short circuit test on transformer is used to determine copper loss in transformer at full load and parameters of approximate [equivalent circuit of transformer](#)

## 6. Describe the construction details of single phase transformer.(A/M-2017,M/J-2017,N/D-2015,A/M-2015)

### TRANSFORMER – INTRODUCTION


A TRANSFORMER is a device that transfers electrical energy from one circuit to another by electromagnetic induction (transformer action). The electrical energy is always transferred without a change in frequency, but may involve changes in magnitudes of voltage and current. Because a transformer works on the principle of electromagnetic induction, it must be used with an input source voltage that varies in amplitude. There are many types of power that fit this description; for ease of explanation and understanding, transformer action will be explained using an ac voltage as the input source.

#### ➤ BASIC OPERATION OF A TRANSFORMER:

Its most basic form a transformer consists of: A primary

- Coil or winding.
- A secondary coil or winding.
- A core that supports the coils or windings


The primary winding is connected to a 60 hertz ac voltage source. The magnetic field (flux) builds up (expands) and collapses (contracts) about the primary winding. The expanding and contracting magnetic field around the primary winding cuts the secondary winding and induces an alternating voltage into the winding. This voltage causes alternating current to flow through the load. The voltage may be stepped up or down depending on the design of the primary and secondary windings.

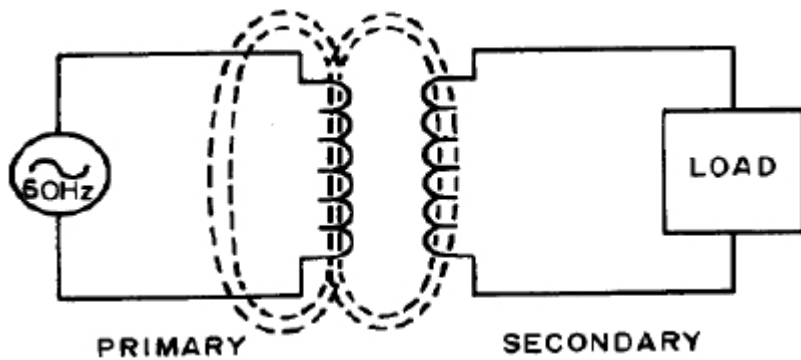
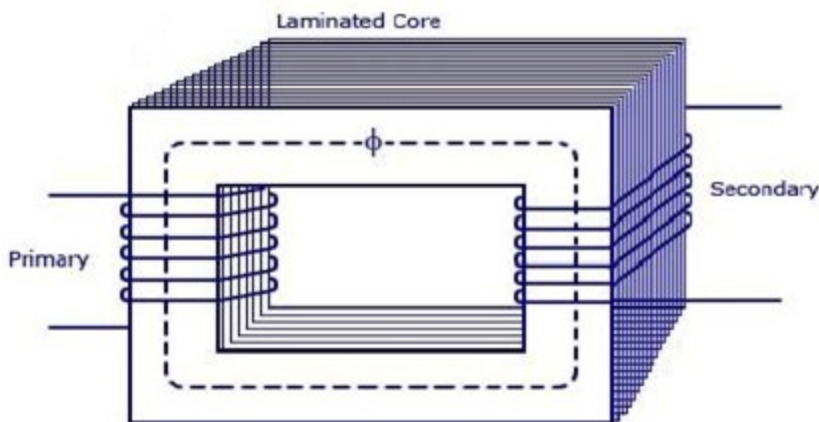
### BASIC WORKING PRINCIPLE OF TRANSFORMER

A transformer can be defined as a static device which helps in the transformation of electric power in one circuit to electric power of the same frequency in another circuit. The voltage can be raised or lowered in a circuit, but with a proportional increase or decrease in the current ratings.

The main principle of operation of a transformer is mutual inductance between two circuits which is linked by a common magnetic flux. A basic transformer consists of two coils that are electrically separate and inductive, but are magnetically linked through a path of reluctance. The working principle of the transformer can be understood from the figure below



As shown above the transformer has primary and secondary windings. The core laminations are joined in the form of strips in between the strips you can see that there are some narrow gaps right through the cross-section of the core. These staggered joints are said to be 'imbricated'. Both the coils have high mutual inductance

Faraday's laws of Electromagnetic Induction as


$$e = M \cdot \frac{dI}{dt}$$

### TRANSFORMER CONSTRUCTION:

Two coils of wire (called windings) are wound on some type of core material. In some cases the coils of wire are wound on a cylindrical or rectangular cardboard form. In effect, the core material is air and the transformer is called an air-core transformer. Transformers used at low frequencies, such as 60 hertz and 400 hertz, require a core of low-reluctance magnetic material, usually iron. This type of transformer is called an iron-core transformer. Most power transformers are of the iron-core type.

The principle parts of a transformer and their functions are:

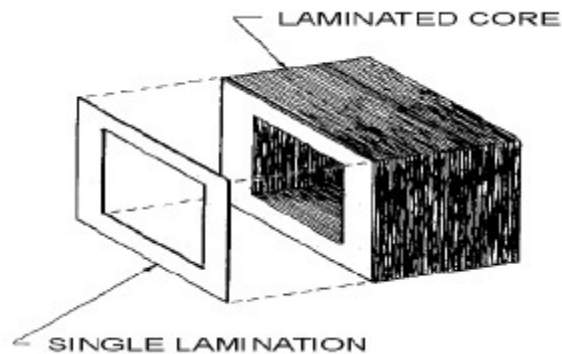- The core, which provides a path for the magnetic lines of flux.
- The primary winding, which receives energy from the ac source.
- The secondary winding, which receives energy from the primary winding and delivers it to the load.
- The enclosure, which protects the above components from dirt, moisture



## CORE

There are two main shapes of cores used in laminated-steel-core transformers. One is the HOLLOWCORE, so named because the core is shaped with a hollow square through the center. This shape of core. Notice that the core is made up of many laminations of steel it shows how the transformer windings are wrapped around both sides of the core.

## WINDINGS

As stated above, the transformer consists of two coils called WINDINGS which are wrapped around a core. The transformer operates when a source of ac voltage is connected to one of the windings and a load device is connected to the other. The winding that is connected to the source is called the PRIMARY WINDING. The winding that is connected to the load is called the secondary winding. The primary is wound in layers directly on a rectangular cardboard form.

7. **Explain the different types of dc motor with neat sketch.(N/D-2016)**


### ❖ DC MOTOR TYPES

- Shunt Wound
- Series Wound
- Compound wound
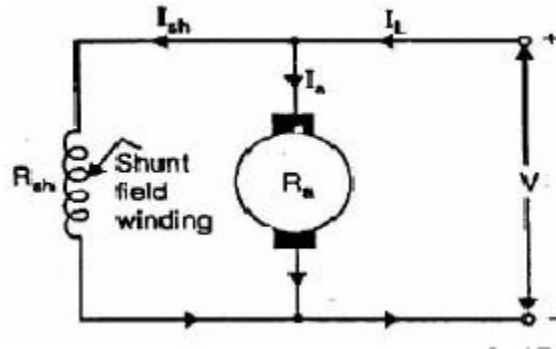
#### 1.Shunt Motor


In shunt wound motor the field winding is connected in parallel with armature. The current through the shunt field winding is not the same as the armature current. Shunt field windings are designed to produce the necessary m.m.f. by means of a relatively large number of turns of wire having high resistance. Therefore, shunt field current is relatively small compared with the armature current





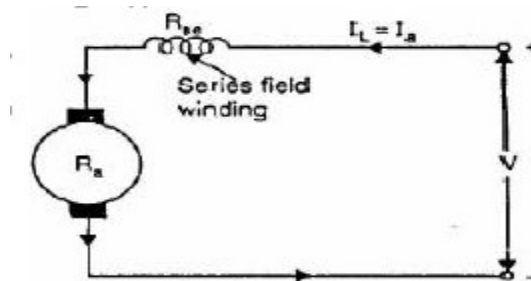**2.Series Motor:**


In series wound motor the field winding is connected in series with the armature. Therefore, series field winding carries the armature current. Since the current passing through a series field winding is the same as the armature current, series field windings must be designed with much fewer turns than shunt field windings for the same mmf. Therefore, a series field winding has a relatively small number of turns of thick wire and, therefore, will possess a low resistance.




**3.Compound Wound Motor:**Compound wound motor has two field windings; one connected in parallel with the armature and the other in series with it. There are two types of compound motor connections

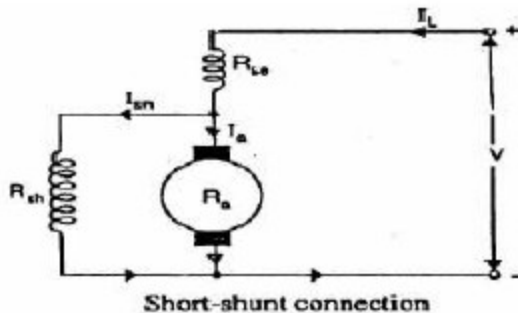1. Short-shunt connection
2. Long shunt connection

When the shunt field winding is directly connected across the armature terminals it is called short-shunt connection.



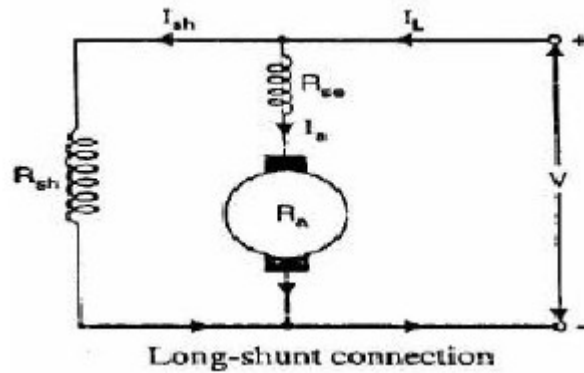When the shunt winding is so connected that it shunts the series combination of armature and series field it is called long-shunt connection.




**8. Explain the working principle of various types of single phase induction motor with neat circuit diagram.(M/J-2016)**

The [single phase induction motors](#) are made self starting by providing an additional flux by some additional means. Now depending upon these additional means the single phase induction motors are classified as:

1. Split phase induction motor.
2. Capacitor start [inductor](#) motor.
3. Capacitor start [capacitor](#) run [induction motor](#) (two value capacitor method).
4. Permanent split capacitor (PSC) motor .
5. Shaded pole induction motor.

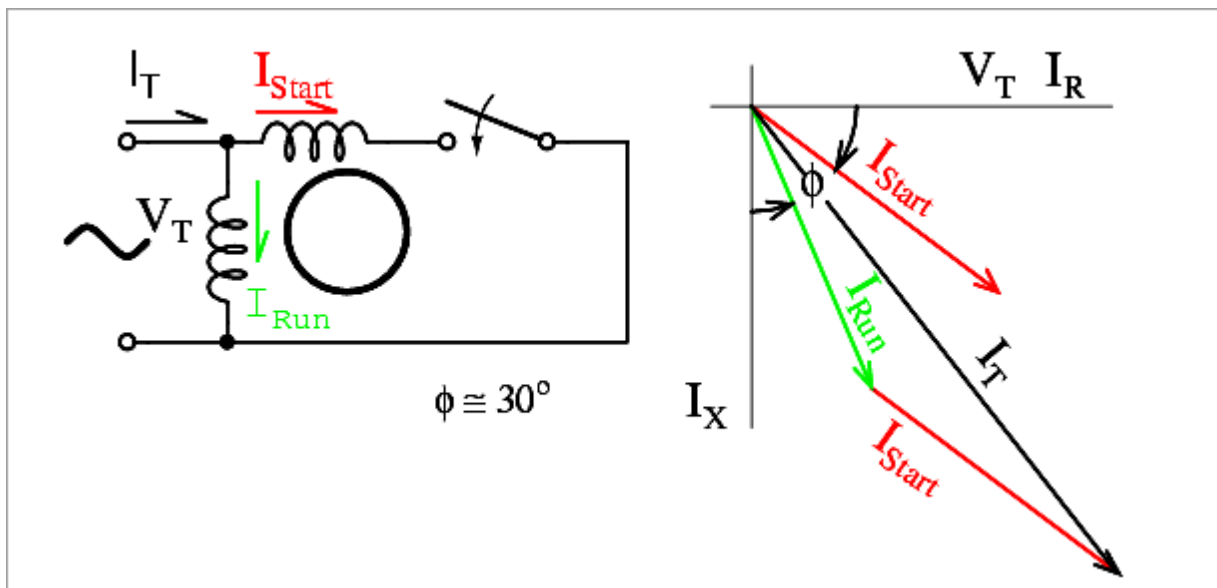
**1.Split Phase Induction Motor** In addition to the main winding or running winding, the stator of single phase induction motor carries another winding called auxiliary winding or starting winding. A centrifugal switch is connected in series with auxiliary winding. The purpose of this switch is to disconnect the auxiliary winding from the main circuit when the motor attains a speed up to 75 to 80% of the synchronous speed.

We know that the running winding is inductive in nature. Our aim is to create the phase difference between the two winding and this is possible if the starting winding carries high resistance.



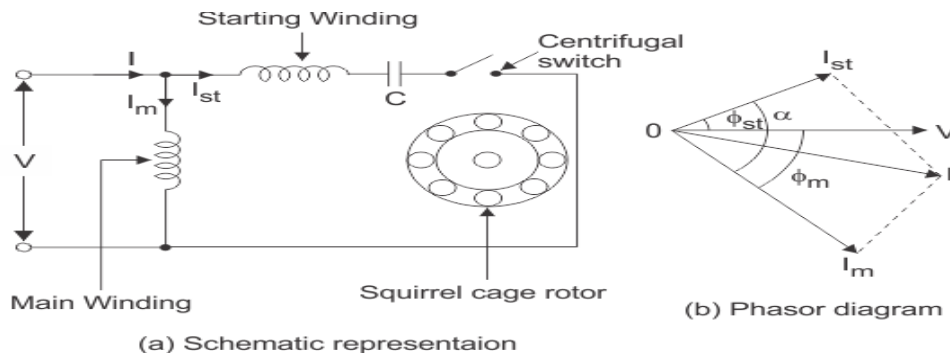
## 2. Capacitor Start IM and Capacitor Start Capacitor Run IM

The working principle and construction of Capacitor start inductor motors and capacitor start capacitor run induction motors are almost the same. We already know that single phase induction motor is not self starting because the magnetic field produced is not rotating type. In order to produce rotating magnetic field there must be some phase difference. In case of split phase induction motor we use resistance for creating phase difference but here we use capacitor for this purpose. We are familiar with this fact that the **current** flowing through the capacitor leads the voltage. So, in **capacitor start inductor motor** and **capacitor start capacitor run induction motor**


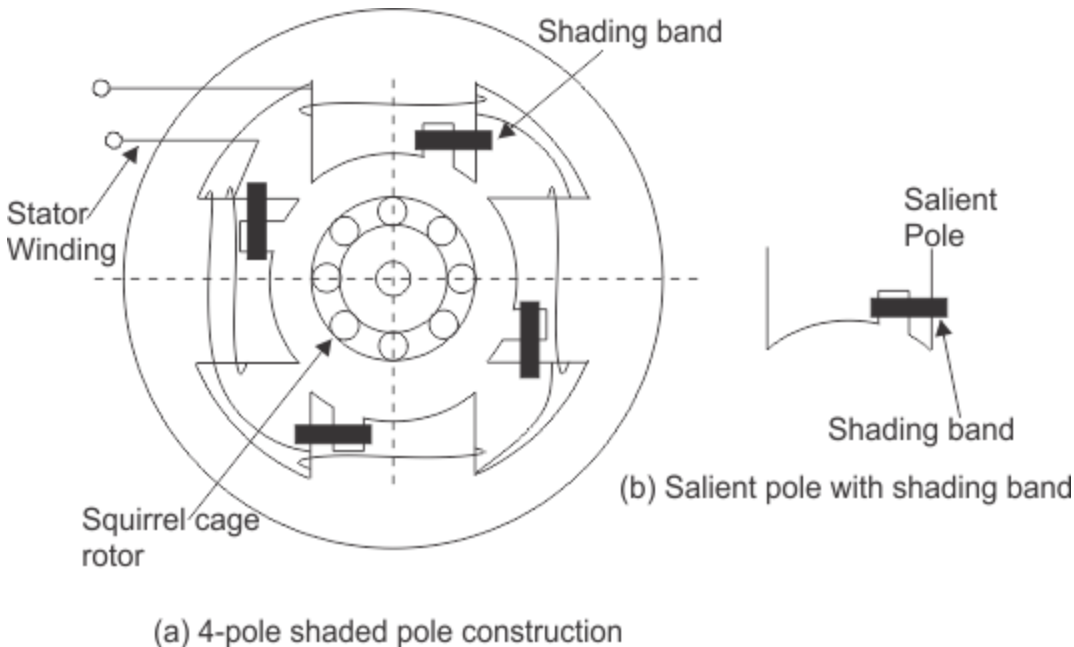
## 3. Shaded Pole Single Phase Induction Motors



The stator of the shaded pole single phase induction motor has salient or projected poles. These poles are shaded by copper band or ring which is inductive in nature. The poles are divided into two unequal halves. The smaller portion carries the copper band and is called as shaded portion of the pole.

**ACTION:** When a single phase supply is given to the stator of shaded pole induction motor an alternating flux is produced. This change of flux induces emf in the shaded coil. Since this shaded portion is short circuited, the current is produced in it in such a direction to oppose the main flux. The flux in shaded pole lags behind the flux in the unshaded pole.

The phase difference between these two fluxes produces resultant rotating flux. We know that the stator winding current is alternating in nature and so is the flux produced by the stator current. In order to clearly understand the working of shaded pole induction motor consider three regions-

1. When the flux changes its value from zero to nearly maximum positive value.
2. When the flux remains almost constant at its maximum value.
3. When the flux decreases from maximum positive value to zero.

## 9. Write shorts notes on the types of dc machines.(N/D-2015)

TYPES OF DC MACHINES:

- i) DC generator
- ii) DC motor

### i) DC generator

An electrical generator is a rotating machine which usually converts mechanical energy into electrical energy for doing work. The energy changing is based on the principle of electromagnetic induction. According to Faraday's laws of electromagnetic induction, Whenever a conductor is feel motion in a magnetic field, emf induced dynamically in the conductor. When an external load is connected to the conductor this induced emf make a current flow in the load.

Thus the mechanical energy which is given in the form of movement to the conductor is converted into electrical energy.

Dc generators can be classified as per their methods of field excitation. There are two types of dc generators on the basis of excitation.

Power delivered to the source is  $V \cdot I(a)$ . **Separately excited Dc generators:-**

If the field winding is excited by a separate dc supply from the external source, then the generator is called separately excited dc generators.

**Self excited Dc generators:-**

If the field winding energy is supplied from the armature of the generator it self, then it is called self excited dc **generators**. Self excited dc generators are further classified as

**Series generator:-**

In series generator field winding is connected series to the **armature** it self.

The voltage generated in series field generator is  $E(\text{generated}) = V(\text{terminal voltage}) + I(a) \cdot R(a) + I(\text{se}) \cdot R(\text{se}) + V(\text{brush})$ .

Power generated is  $E(g) \cdot I(a)$ .

**Shunt generator:**

In shunt generator field winding is connected across the armature or parallel to the armature.

The generated emf in shunt field generator is  $E(\text{generated}) = V(\text{terminal voltage}) + I(a) \cdot R(a)$ .

Power generated is  $E(g) \cdot I(a)$ .

Power delivered to the source is  $V \cdot I(a)$ .

**Compound generator**

The compound generator consists of both shunt field and series field winding on its structure. One winding is series and other is in parallel with the armature of the generator.

## ii)DC Motor:

electric motors are everywhere around us. Almost all the electro-mechanical movements we see around us are caused either by a AC or a **DC motor**. Here we will be exploring DC motors. This is a device that converts DC electrical energy to a mechanical energy.


### Principle of DC Motor

This DC or direct current motor works on the principal, when a current carrying conductor is placed in a magnetic field, it experiences a torque and has a tendency to move.

This is known as motoring action. If the direction of current in the wire is reversed, the direction of rotation also reverses. When magnetic field and electric field interact they produce a mechanical force, and based on that the working principle of DC motor is established.

The direction of rotation of a this motor is given by Fleming's left hand rule, which states that if the index finger, middle finger and thumb of your left hand are extended mutually perpendicular to each other and if the index finger represents the direction of magnetic field, middle finger indicates the direction of current, then the thumb represents the direction in which force is experienced by the shaft of the DC motor.

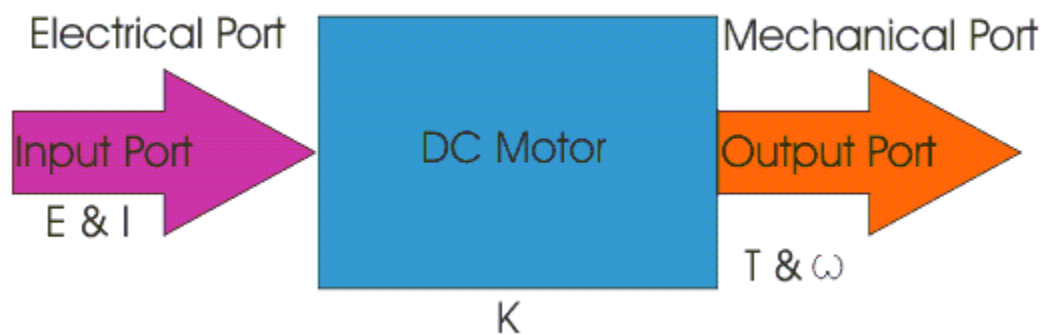Structurally and construction wise a direct current motor is exactly similar to a DC generator, but electrically it is just the opposite. Here we unlike a generator we supply electrical energy to the input port and derive mechanical energy from the output port. We can represent it by the block diagram shown below.




Here in a DC motor, the supply voltage E and current I is given to the electrical port or the input port and we derive the mechanical output i.e. torque T and speed  $\omega$  from the mechanical port or output port.

The input and output port variables of the direct current motor are related by the parameter K.  
 $T = KI$  and  $E = K\omega$

So from the picture above we can well understand that motor is just the opposite phenomena of a DC generator, and we can derive both motoring and generating operation from the same machine by simply reversing the ports.
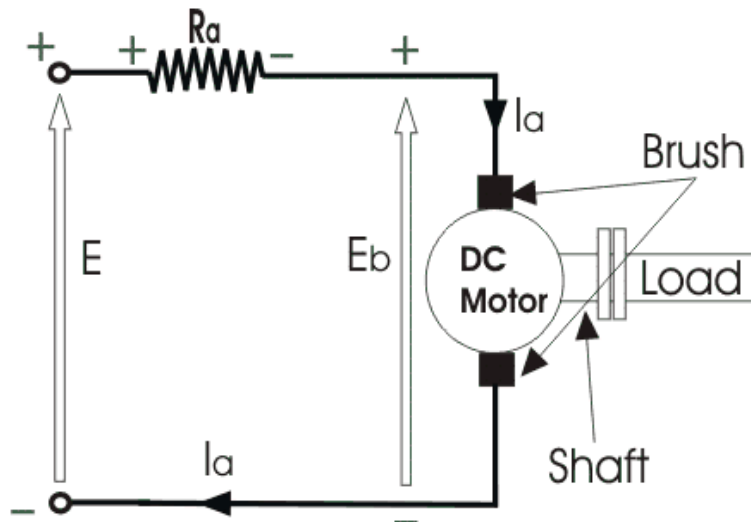
## Detailed Description of a DC Motor

The direct current motor is represented by the circle in the center, on which is mounted the brushes, where we connect the external terminals, from where supply voltage is given. On the mechanical terminal we have a shaft coming out of the Motor, and connected to the armature, and the armature-shaft is coupled to the mechanical load. On the supply terminals we represent the armature resistance  $R_a$  in series.



**10. With a neat circuit diagram Explain the construction and principle of operation of DC Generator. (N/D-2015)**


### DC Generator:

A dc generator is an electrical machine which converts mechanical energy into direct current electricity. This energy conversion is based on the principle of production of dynamically induced emf. This article outlines basic construction and working of a DC generator.
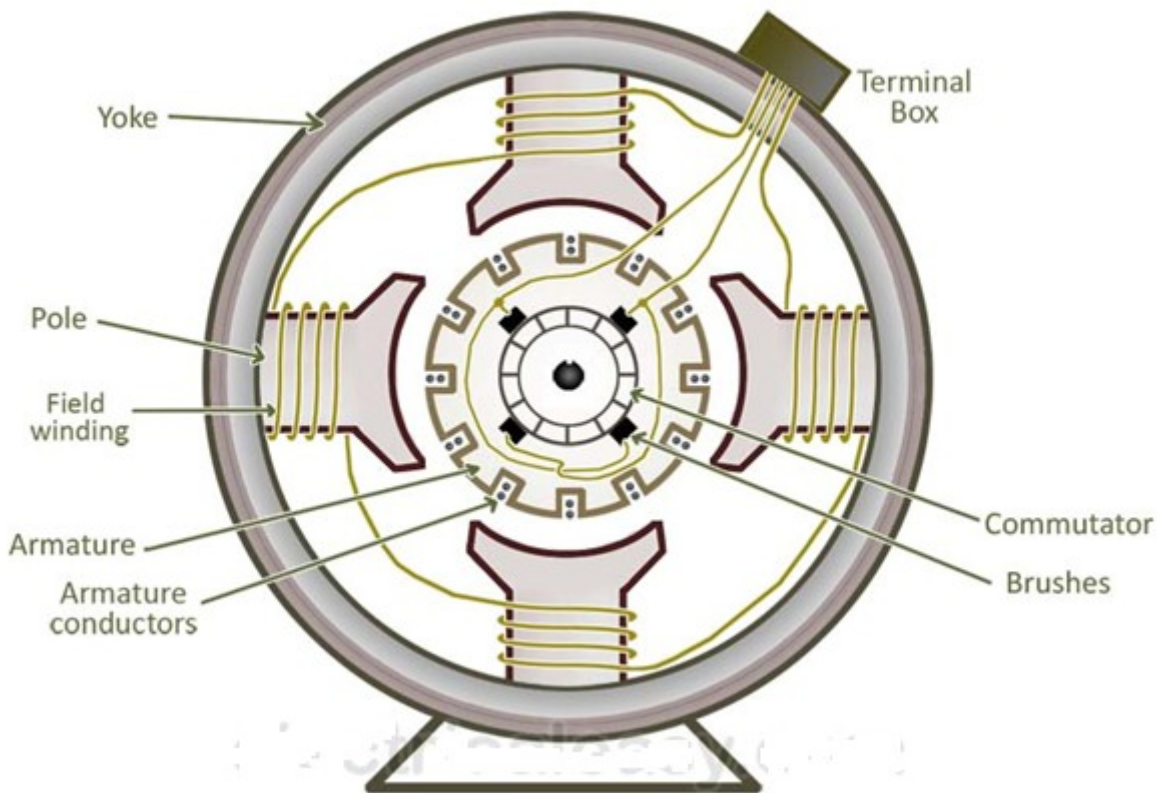
### Construction of a DC generator:

A DC generator can be used as a DC motor without any constructional changes and vice versa is also possible. Thus, a DC generator or a DC motor can be broadly termed as a DC machine. These basic constructional details are also valid for the construction of a DC motor. Hence, let's call this point as construction of a DC machine instead of just 'construction of a dc generator'.





The above figure shows the constructional details of a simple **4-pole DC machine**. A DC machine consists two basic parts; stator and rotor. Basic constructional parts of a DC machine are described below.


1. **Yoke:** The outer frame of a dc machine is called as yoke. It is made up of cast iron or steel. It not only provides mechanical strength to the whole assembly but also carries the magnetic flux produced by the field winding.
2. **Poles and pole shoes:** Poles are joined to the yoke with the help of bolts or welding. They carry field winding and pole shoes are fastened to them. Pole shoes serve two purposes; (i) they support field coils and (ii) spread out the flux in air gap uniformly.
3. **Field winding:** They are usually made of copper. Field coils are former wound and placed on each pole and are connected in series. They are wound in such a way that, when energized, they form alternate North and South poles.
4. **Armature core:** Armature core is the rotor of the machine. It is cylindrical in shape with slots to carry armature winding. The armature is built up of thin laminated circular steel disks for reducing eddy current losses. It may be provided with air ducts for the axial air flow for cooling purposes. Armature is keyed to the shaft.
5. **Armature winding:** It is usually a former wound copper coil which rests in armature slots. The armature conductors are insulated from each other and also from the armature core. Armature winding can be wound by one of the two methods; lap winding or wave winding. Double layer lap or wave windings are generally used. A double layer winding means that each armature slot will carry two different coils.
6. **Commutator and brushes:** Physical connection to the armature winding is made through a commutator-brush arrangement. The function of a commutator, in a dc generator, is to collect the current

generated in armature conductors. Whereas, in case of a dc motor, commutator helps in providing current to the armature conductors. A commutator consists of a set of copper segments which are insulated from each other. The number of segments is equal to the number of armature coils. Each segment is connected to an armature coil and the commutator is keyed to the shaft. Brushes are usually made from carbon or graphite. They rest on commutator segments and slide on the segments when the commutator rotates keeping the physical contact to collect or supply the current.
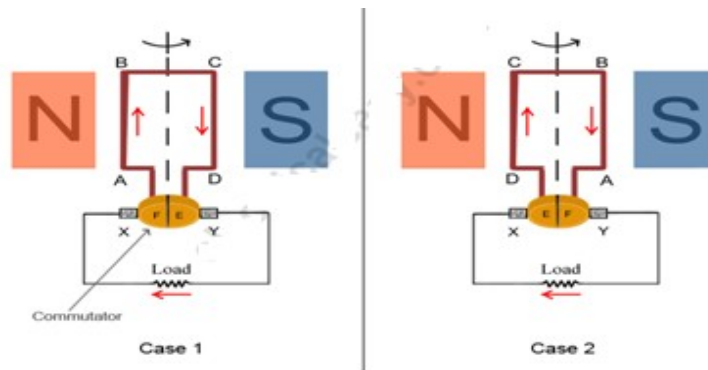
### Working principle of a DC generator:

According to [Faraday's laws of electromagnetic induction](#), whenever a conductor is placed in a varying magnetic field (OR a conductor is moved in a magnetic field), an emf (electromotive force) gets induced in the conductor. The magnitude of induced emf can be calculated from the [emf equation of dc generator](#). If the conductor is provided with the closed path, the induced current will circulate within the path. In a DC generator, field coils produce an electromagnetic field and the armature conductors are rotated into the field. Thus, an electromagnetically induced emf is generated in the armature conductors. The direction of induced current is given by [Fleming's right hand rule](#).

according to Fleming's right hand rule, the direction of induced current changes whenever the direction of motion of the conductor changes. Let's consider an armature rotating clockwise and a conductor at the left is moving upward. When the armature completes a half rotation, the direction of motion of that particular conductor will be reversed to downward.



Hence, the direction of current in every armature conductor will be alternating. If you look at the above figure, you will know how the direction of the induced current is alternating in an armature conductor. But with a split ring commutator, connections of the armature conductors also gets reversed when the current reversal occurs. And therefore, we get unidirectional current at the terminals.

### 11. Describe the construction of an induction motor with neat diagrams. (M/J 2016)

Explain the construction of three phase induction motor with neat diagram? (A/M 2017)

#### Construction of Induction Motor

The three phase induction motor is a preferable type of motor. It is mostly used in industrial drives because it is very reasonable and vigorous, economical and reliable. It is also called asynchronous motor because it does not run at a synchronous speed. The induction motor requires very little maintenance and also it has high overloading capacity.


- Construction of Stator
- Construction of Rotor

A three phase **Induction motor** mainly consists of two parts called as the **Stator** and the **Rotor**. The stator is the stationary part of the induction motor, and the rotor is the rotating part. The construction of the stator is similar to the three-phase synchronous motor, and the construction of rotor is different for the different machine. The construction of the induction motor is explained below in detail.

### Construction of Stator


The stator is built up of high-grade alloy steel laminations to reduce eddy current losses. It has three main parts, namely outer frame, the stator core and a stator winding.

Outer frame

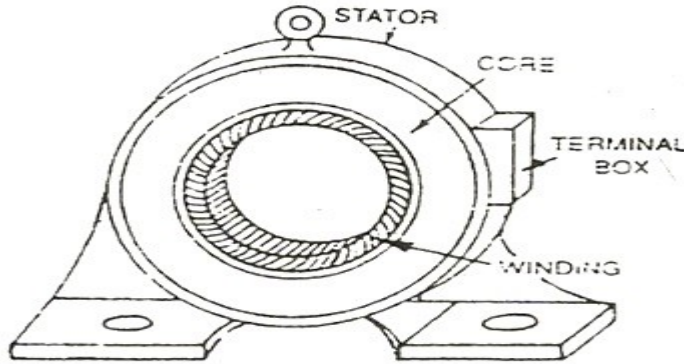
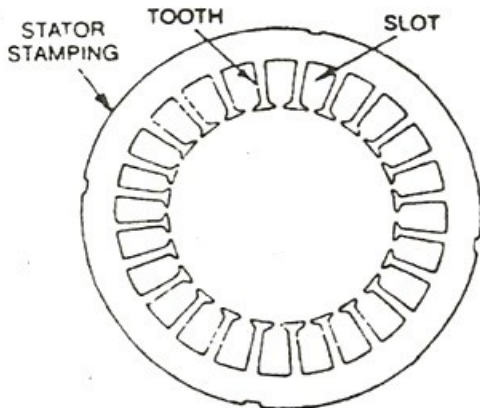
### Stator Core

The stator core is built of high-grade silicon steel stampings. Its main function is to carry the alternating magnetic field which produces hysteresis and eddy current losses. The stampings are fixed to the stator frame. Each stamping are insulated from the other with a thin varnish layer. The thickness of the stamping usually varies from 0.3 to 0.5 mm. Slots are punched on the inner side of the stampings as shown in the figure below.



### Stator windings

**The core of the** stator carries three phase windings which are usually supplied from a three-phase supply system. The six terminals of the windings (two of each phase) are connected in the terminal box of the machine. The stator of the motor is wound for a definite number of poles, depending on the speed of the motor. If the number of poles is greater, the speed of the motor will be less and if the number of poles is less than the speed will be high. As the relationship between the speed and the pole of the motor is given as

$$N_s \propto \frac{1}{P} \quad \text{or} \quad N_s = \frac{120f}{P}$$


The windings may be connected in start and delta.

### Construction of Rotor

The rotor is also built of thin laminations of the same material as the stator. The laminated cylindrical core is mounted directly on the shaft. These laminations are slotted on the outer side to receive the conductors. There are two types of rotor.
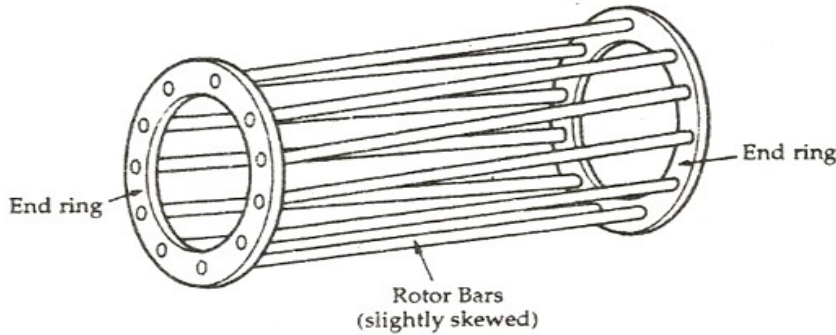
### Squirrel Cage Rotor

A squirrel cage rotor consists of a laminated cylindrical core. The circular slots at the outer periphery are semi-closed. Each slot contains uninsulated bar conductor of aluminium or copper. At the end of the rotor the conductors are short-circuited by a heavy ring of copper or aluminium. The diagram of the cage rotor is shown below.




The rotor slots are usually not parallel to the shaft but are skewed. The skewing of the rotor conductors has the following advantages given below.

- It reduces humming and provide smooth and noise free operation.
- It results in a uniform torque curve for different positions of the rotor.
- The locking tendency of the rotor is reduced. As the teeth of the rotor and the stator attract each other and lock.
- It increases the rotor resistance due to the increased length of the rotor bar conductors.
- Advantages of Squirrel Cage Rotor
- The following advantages of the cage rotor are given below.
- The cage rotor is cheaper, and the construction is robust.
- The absence of the brushes reduces the risk of sparking.
- Its Maintenance is less.
- The power factor is higher
- The efficiency of the cage rotor is higher.
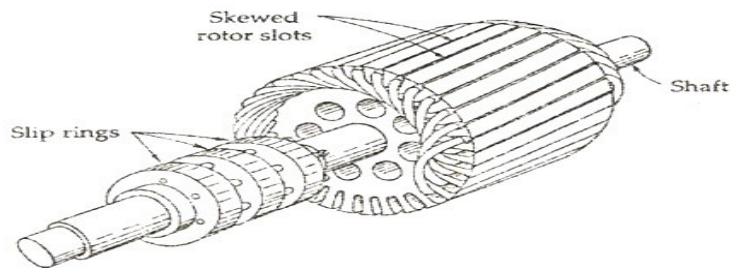
### Phase Wound Rotor

The Phase wound rotor is also called as Slip Ring Rotor. It consists of a cylindrical core which is laminated. The outer periphery of the rotor has a semi-closed slot which carries a 3 phase insulated windings. The rotor windings are connected in star.

The **slip ring induction motor** is shown in the figure below.



The slip rings are mounted on the shaft with brushes resting on them. The brushes are connected to the variable resistor. The function of the slip rings and the brushes is to provide a means of connecting external resistors in the rotor circuit. The resistor enables the variation of each rotor phase resistance to serve the following purposes given below.

- It increases the starting torque and decreases the starting current.
- It is used to control the speed of the motor.

- In this type also, the rotor is skewed. A mild steel shaft is passed through the center of the rotor and is fixed to it. The purpose of the shaft is to transfer mechanical power.
- Advantages of Phase Wound Rotor
- Following are the advantages of the Phase Wound Rotor.
- High starting torque and low starting current.
- For controlling the speed of the motor, an external resistance can be added in the circuit.

## 12. Derive the EMF equation for the alternator? (A/M 2017)

### EMF Equation of a Synchronous Generator

The generator which runs at a synchronous speed is known as the synchronous generator. The synchronous generator converts the mechanical power into electrical energy for the grid. The Derivation of **EMF Equation** of a synchronous generator is given below.

Let,

- P be the number of poles
- $\phi$  is Flux per pole in Webers
- N is the speed in revolution per minute (r.p.m)
- f be the frequency in Hertz
- $Z_{ph}$  is the number of conductors connected in series per phase
- $T_{ph}$  is the number of turns connected in series per phase
- $K_c$  is the coil span factor
- $K_d$  is the distribution factor

Flux cut by each conductor during one revolution is given as  $P\phi$  Weber. Time taken to complete one revolution is given by  $60/N$  sec

Average EMF induced per conductor will be given by the equation shown below

$$\frac{P\phi}{60/N} = \frac{P\phi N}{60} \text{ volts}$$

Average EMF induced per phase will be given by the equation shown below

$$\frac{P\phi N}{60} \times Z_{ph} = \frac{P\phi N}{60} \times 2T_{ph} \text{ and}$$

$$T_{ph} = \frac{Z_{ph}}{2}$$

$$\text{Average EMF} = 4 \times \phi \times T_{ph} \times \frac{PN}{120} = 4\phi f T_{ph}$$

The average EMF equation is derived with the following assumptions given below.

- Coils have got the full pitch.
- All the conductors are concentrated in one stator slot.

**Root mean square** (R.M.S) value of the EMF induced per phase is given by the equation shown below.

$E_{ph}$  = Average value x form factor

Therefore,

$$E_{ph} = 4\phi f T_{ph} \times 1.11 = 4.44 \phi f T_{ph} \text{ volts}$$

If the coil span factor  $K_c$  and the distribution factor  $K_d$ , are taken into consideration than the Actual EMF induced per phase is given as

$$E_{ph} = 4.44 K_c K_d \phi f T_{ph} \text{ volts ... .. (1)}$$

Equation (1) shown above is the EMF equation of the Synchronous Generator.

## UNIT-5 MEASUREMENTS AND INSTRUMENTATION

### **1.Mention 2 disadvantages of capacitive transducer? (May-11)**

- Output impedance of capacitive transducer is very high. So its measuring circuit becomes very complicated.
- The capacitance of capacitive transducer change with change in temperature or account of Presence of small external matter.

Example: dust particles, moisture.

### **2.Write the function of transducer (May-11)**

It converts one type of energy into another.

### **3..Define inverse transducer with example (May-10)**

- An inverse transducer is defined as device which converts an electrical quantity into a non electrical quantity.
- It is a precision actuator which has an electrical input and a low power non electrical output.

### **4.Mention any 4 types of analog to digital convertor? (May-10)**

- Flash type of convertor
- Staircase convertor
- Tracking convertor
- Successive approximation type

### **5.What is the need of sample and hold circuit in A/D convertor? (Dec-10)**

- Sample and hold circuits are the devices that store analog information and reduce the aperture time of an A/D convertor
- A sample hold is a simply a voltage memory device in which an input voltage is acquired and then stored on a high quality capacitor.

### **6.Define the primary and secondary transducers? (May 2010) Primary Transducer:**

When the input signal is directly sensed by the transducer and physical phenomenon is converted into electrical form directly then such a transducer is called the primary transducer.

#### **Secondary Transducer:**

When the input signal is sensed first by some detector or sensor and then its output being of some from other than input signals is given as input to a transducer for conversion into electrical form, then such a transducer falls in the category of secondary transducers.

### **7..State the performance parameters of ADC (May 2010)**

- Resolution.
- Quantization error.
- Conversion time.

### **8..How do you classify transducers? (Dec 2010)**

- On the basis of transduction form used.
- As primary and secondary transducers.



- As active and passive transducers.
- As analog and digital transducers.
- As transducers and inverse transducers.

**9..What is piezo-electric effect? (Dec 2010)**

A piezoelectric material is one in which an electric potential appears across certain surfaces of the crystal if the dimensions of the crystals are changed by the application of a mechanical force this potential is produced by the displacement of charges .

This effect is reversible.

This phenomenon is known as piezoelectric effect.

**10.Explain the working principle of capacitive transducers? (Dec 2010)**

The principle of capacitive transducer is based on the familiar equation of capacitance of parallel plate capacitor.

$$C= A /d$$

**11.What are the selection criteria for the transducer? (Jun 2009)**

- Operating range.
- Sensitivity.
- Environmental conditions
- Errors.
- Accuracy.

**12.What is meant by strain gauge? What for it is used? (Jun 2009)**

It is an example of a passive transducer that uses the variation in electrical resistance in wires to sense the strain produced by a force on the wires.

**13.What is POT? It is active or passive transducer? (Dec 2006)**

- POT is a resistive potentiometer used for the purpose of voltage division.
- It consists for a resistive element provided with a sliding contact called as wiper.
- The POT is a passive transducer since it requires an external power source for its operation.

**14.Name the transducer that uses sensing acceleration? (Jun 2006, May 2005) Piezo-electric transducer.**

**15.Write any four basic requirements of transducer? (Dec 2004)**

- RUGGEDNESS: It should be capable for withstanding overload.
- LINEARITY: The input-output characteristics should be linear.
- NO HYSTERISIS: It should not give any hysteresis during measurement while input signal is varied from low to high value and vice versa.
- RESIDUAL DEFORMATION: There should be no deformations on removal of load after long period of time

**16. Define current transformer& Potential transformer?**



A **current transformer (CT)** is a type of **transformer** that is used to measure alternating **current (AC)**. It produces a **current** in its secondary which is proportional to the **current** in its primary. ... The **current transformer** presents a negligible load to the primary circuit

### Potential transformer

**Voltage transformers (VT)**, also called **potential transformers (PT)**, are a parallel connected type of **instrument transformer**. They are designed to present negligible load to the supply being measured and have an accurate **voltage** ratio and phase relationship to enable accurate secondary connected metering.

## PART-B

### 1. Explain in detail about classifications of transducer.

#### TRANSDUCERS

Ø The input quantity for most instrumentation systems is non-electrical. In order to use electrical methods and techniques for measurement, the non-electrical quantity is converted into a proportional electrical signal by a device called transducer.

Ø Another definition states that transducer is a device which when actuated by energy in one system, supplies energy in the same form or in another form to a second system.


Ø When transducer gives output in electrical form it is known as electrical transducer. Actually, electrical transducer consists of two parts which are very closely related to each other.

Ø These two parts are sensing or detecting element and transduction element. The sensing or detecting element is commonly known as sensor.

Ø

Definition states that sensor is a device that produces a measurable response to a change in a physical condition.

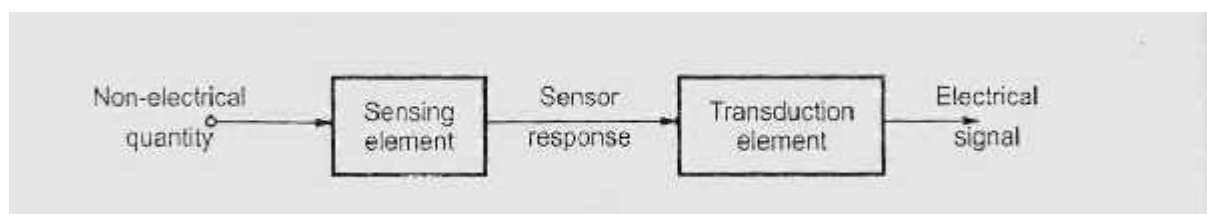Ø The transduction element transforms the output of the sensor to an electrical output, as shown in the Fig.




### Classification of Electrical Transducers

Transducers may be classified according to their structure, method of energy conversion and application. Thus we can say that transducers are classified

- As active and passive transducer
- According to transduction principle
- As analog and digital transducer
- As primary and secondary transducer
- As transducer and inverse transducer

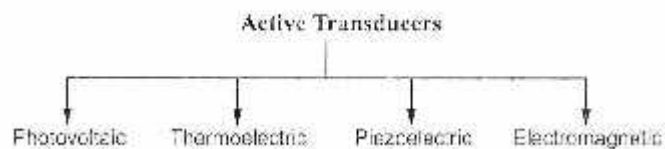
## Active and Passive Transducers

- Ø Active transducers are self-generating type of transducers.
- Ø These transducers develop an electrical parameter (i.e. voltage or current) which is proportional to the quantity under measurement.
- Ø These transducers do not require any external source or power for their operation.
- Ø They can be subdivided into the following commonly used types


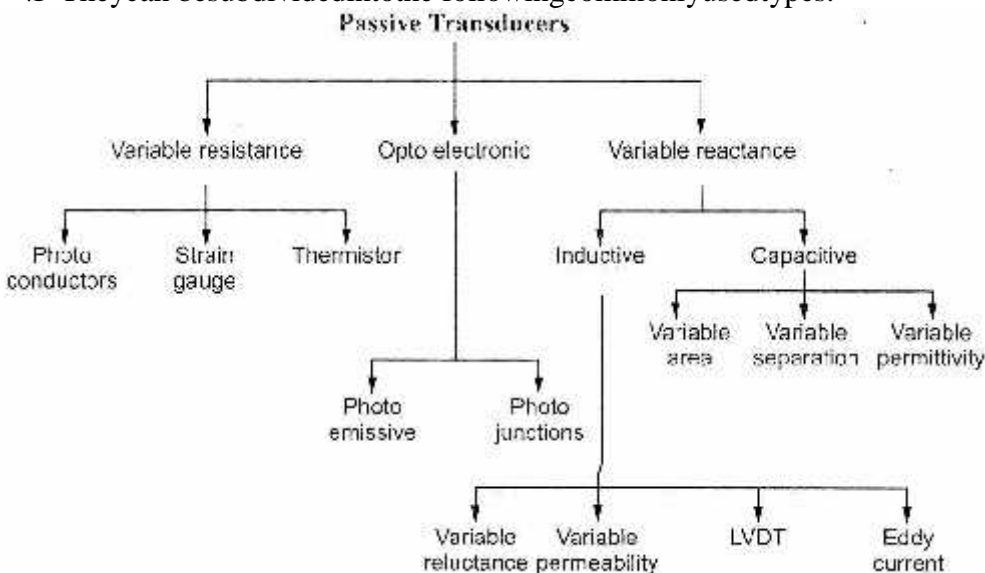
## Passive Transducers

- Ø Passive transducers do not generate any electrical signal by themselves.
- Ø To obtain an electrical signal from such transducers, an external source of power is essential.
- Ø Passive transducers depend upon the change in an electrical parameter (R, L, or C).
- Ø They are also known as externally power driven transducers.
- Ø They can be subdivided into the following commonly used types.



## According to Transduction Principle

The transducers can be classified according to principle used in transduction.

- Capacitive transduction
- Electromagnetic transduction
- Inductive transduction

- Piezoelectric transduction
- Photovoltaic transduction
- Photoconductive transduction

### Analog and Digital Transducers

The transducers can be classified on the basis of the output which may be a continuous function of time or the output may be in discrete steps.

#### Analog Transducers


- ∅ These transducers convert the input quantity into an analog output which is a continuous function of time.
- ∅ A strain gauge, LVDT, thermocouples or thermistors are called analog transducers as they produce an output which is a continuous function of time.

#### Digital Transducers

- ∅ Digital transducers produce an electrical output in the form of pulses which form a unique code.
- ∅ Unique code is generated for each discrete value sensed.
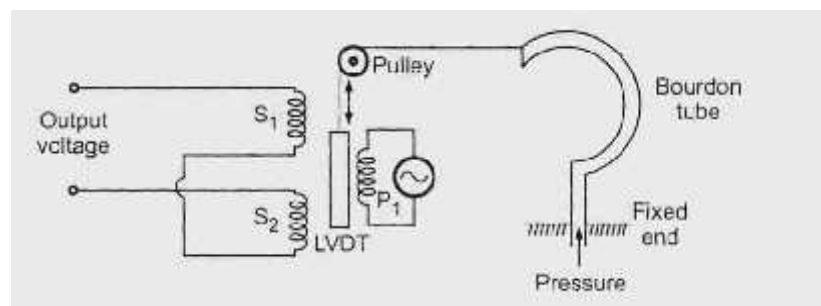
#### Primary or Secondary

- ∅ Some transducers consist of a mechanical device along with the electrical device.
  - ∅ In such transducers, the mechanical device acts as a primary transducer and converts a physical quantity into a mechanical signal.
  - ∅ The electrical device then converts the mechanical signal produced by the primary transducer into an electrical signal.
  - ∅ Therefore, the electrical device acts as a secondary transducer.
  - ∅ For example, in pressure measurement, a Bourdon tube acts as a primary transducer which converts a pressure into displacement, and an LVDT acts as a secondary transducer which converts this displacement into an equivalent electrical signal.



### Pressure Measurement

#### Transducer and Inverse Transducer

- ∅ Transducers convert a non-electrical quantity into an electrical quantity, whereas an inverse transducer converts an electrical quantity into a non-electrical quantity.

y into non-electrical quantity.

- Ø For example, microphone is a transducer which converts sound signal into an electrical signal whereas loudspeaker is an inverse transducer which converts electrical signal into sound signal.

## 2. Explain in detail about merits, demerits and characteristics of transducer.

### Advantages Transducers

1. Electrical signal obtained from electrical transducer can be easily processed (mainly amplified) and brought to a level suitable for output device which may be an indicator or recorder.
2. The electrical systems can be controlled with a very small level of power.
3. The electrical output can be easily used, transmitted, and processed for the purpose of measurement.
4. With the advent of IC technology, the electronics systems have become extremely small in size, requiring small space for their operation.
5. No moving mechanical parts are involved in the electrical systems. Therefore there is no question of mechanical wear and tear and no possibility of mechanical failure.

Electrical transducer is almost a must in

this modern world. Apart from the merits described above, some disadvantages do exist in electrical sensors.

### Disadvantages of Electrical Transducers

- Ø The electrical transducer is sometimes less reliable than mechanical type because of the ageing and drift of the active components.
- Ø Also, the sensing elements and the associated signal processing circuitry are

com

paratively expensive.

- Ø With the use of better materials, improved technology and circuitry, the range of accuracy and stability have been increased for electrical transducers.
- Ø Using negative feedback technique, the accuracy of measurement and the stability of the system are improved, but all at the expense of increased circuit complexity, more space, and obviously, more cost.

### Characteristic of Transducer

1. **Accuracy:** It is defined as the closeness with which the reading approaches an accepted standard value or ideal value or true value, of the variable being measured.
2. **Ruggedness:** The transducers should be mechanically rugged to withstand overloads. It should have overload protection.
3. **Linearity:** The output of the transducers should be linearly proportional to the input quantity under measurement. It should have linear input-output characteristic.
4. **Repeatability:** The output of the transducer must be exactly the same, under same environment conditions, when the same quantity is applied at the input repeatedly.
5. **High output:** The transducers should give reasonably high output signals so that it can be easily processed and measured. The output must be much larger than noise. Now-a-days, digital output is preferred in many applications;
6. **High Stability and Reliability:** The output of the transducer should be highly

stable and reliable so that there will be minimum error in measurement. The output must remain unaffected by environmental conditions such as change in temperature, pressure, etc.

7. **Sensitivity:** The sensitivity of the electrical transducer is defined as the electrical output obtained per unit change in the physical parameter of the input quantity. For example, for a transducer used for temperature measurement, sensitivity will be expressed in  $mV/^{\circ}C$ . A high sensitivity is always desirable for a given transducer.
8. **Dynamic Range:** For a transducer, the operating range should be wide, so that it can be used over a wide range of measurement conditions.
9. **Size:** The transducer should have the smallest possible size and shape with minimal weight and volume. This will make the measurement system very compact.

**Speed of Response:** It is the rapidity with which the transducer responds to changes in the measured quantity. The speed of response of the transducers should be as high as practicable.

### 3. Explain the selection criteria of transducer in detail.

1. Nature of measurement
  2. Loading effect
  3. Environmental considerations
  4. Measuring system
  5. Cost & Availability
- In a measurement system the transducer (or a combination of transducers) is the input element with the critical function of transforming some physical quantity to a proportional electrical signal. So selection of an appropriate transducer is most important for having accurate results.
  - The first step in the selection procedure is to clearly define the nature of quantity under measurement (measurand) and know the range of magnitudes and frequencies that the measurand is expected to exhibit. Next step will be to examine the available transducer principles for measurement of desired quantity. The type of transducer selected must be compatible with the type and range of the quantity to be measured and the output device.
  - In case one or more transducer principles are capable of generating a satisfactory signal, decision is to be taken whether to employ a commercially available transducer or build a suitable transducer. If the transducers are available in the market at a suitable price, the choice will probably be to purchase one of them, otherwise own transducer will have to be designed, built and calibrated.
  - The points to be considered in determining a transducer suitable for a specific measurement are as follows:

- *Range.* The range of the transducer should be large enough to encompass all the expected magnitudes of the measurand.
- *Sensitivity.* The transducer should give a sufficient output signal per unit of measured input in order to yield meaningful data.
- *Electrical Output Characteristics.* The electrical characteristics—the output impedance, the frequency response, and the response time of the transducer output signal should be compatible with the recording device and the rest of the measuring system equipment.
- *Physical Environment.* The transducer selected should be able to withstand the environmental conditions to which it is likely to be subjected while carrying out measurements and tests.
- Such parameters are temperature, acceleration, shock and vibration, moisture, and corrosive chemicals might damage some transducers but not others.
- *Errors.* The errors inherent in the operation of the transducer itself, or those errors caused by environmental conditions of the measurement, should be small enough or controllable enough that they allow meaningful data to be taken.
- However the total measurement error in a transducer-activated system may be reduced to fall within the required accuracy range by adopting the following techniques.

#### 4. Draw and explain resistive transducer in detail.

### Resistance Transducers

#### Temperature Sensors

Temperature is one of the fundamental parameters indicating the physical condition of matter, i.e. expressing its degree of hotness or coldness. Whenever a body is heated, various effects are observed. They include

- Change in the physical or chemical state, (freezing, melting, boiling etc.)
- Change in physical dimensions,
- Changes in electrical properties, mainly the change in resistance,
- Generation of an emf at the junction of two dissimilar metals.

One of these effects can be employed for temperature measurement purposes. Electrical methods are the most convenient and accurate methods of temperature measurement. These methods are based on change in resistance with temperature and generation of thermal emf. The change in resistance with temperature may be positive or negative. According to that there are two types


- Resistance Thermometers — Positive temperature coefficient
- Thermistors — Negative temperature coefficient

#### Construction of Resistance Thermometers

∅ The wire resistance thermometer usually consists of a coil wound on a mica or ceramic former, as shown in the Fig.

∅

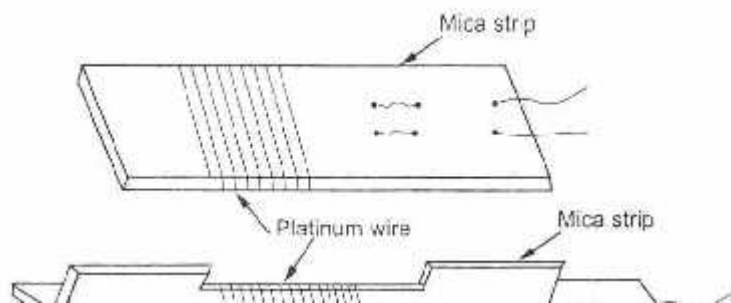The coil is wound in bifilar form so as to make it non-inductive. Such coils are available in different sizes and with different resistance values ranging from 10 ohms to 25,000 ohms.




### **Resistance Thermometers**

1. The measurement is accurate.
2. Indicators, recorders can be directly operated.
3. The temperature sensor can be easily installed and replaced.
4. Measurement of differential temperature is possible.
5. Resistance thermometers can work over a wide range of temperature from  $-20^{\circ}\text{C}$  to  $+650^{\circ}\text{C}$ .
6. They are suitable for remote indication.
7. They are smaller in size.
8. They have stability over long periods of time.
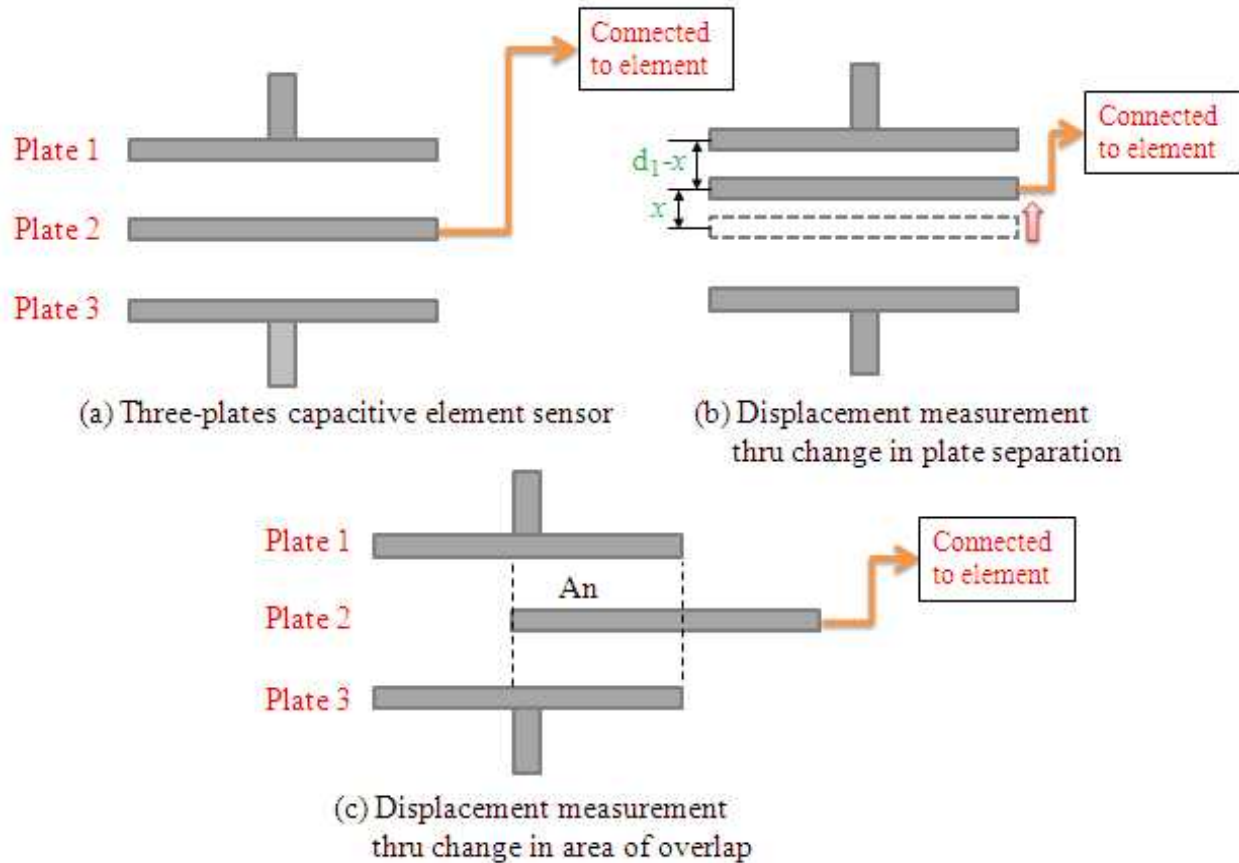
### **5. Draw and explain capacitive transducer in detail. Also mention its applications.**

- Capacitive sensor is of non-contact type sensor and is primarily used to measure the linear displacements from few millimeters to hundreds of millimeters. It comprises of three plates, with the upper pair forming one capacitor and the lower pair another. The linear displacement might take in two forms:
  - one of the plates is moved by the displacement so that the plate separation changes
  - area of overlap changes due to the displacement.





- The capacitance  $C$  of a parallel plate capacitor is given by,
- $C = \epsilon_r \epsilon_0 A / d$


where  $\epsilon_r$  is the relative permittivity of the dielectric between the plates,  $\epsilon_0$  permittivity of free space,  $A$  area of overlap between two plates and  $d$  the plate separation.

- As the central plate moves near to top plate or bottom one due to the movement of the element/workpiece of which displacement is to be measured, separation in between the plate changes. This can be given as,
- $C_1 = (\epsilon_r \epsilon_0 A) / (d + x)$
- $C_2 = (\epsilon_r \epsilon_0 A) / (d - x)$
- When  $C_1$  and  $C_2$  are connected to a Wheatstone's bridge, then the resulting out-of-balance voltage would be in proportional to displacement  $x$ .

#### APPLICATIONS

- Feed hopper level monitoring
- Small vessel pump control
- Grease level monitoring
- Level control of liquids
- Metrology applications
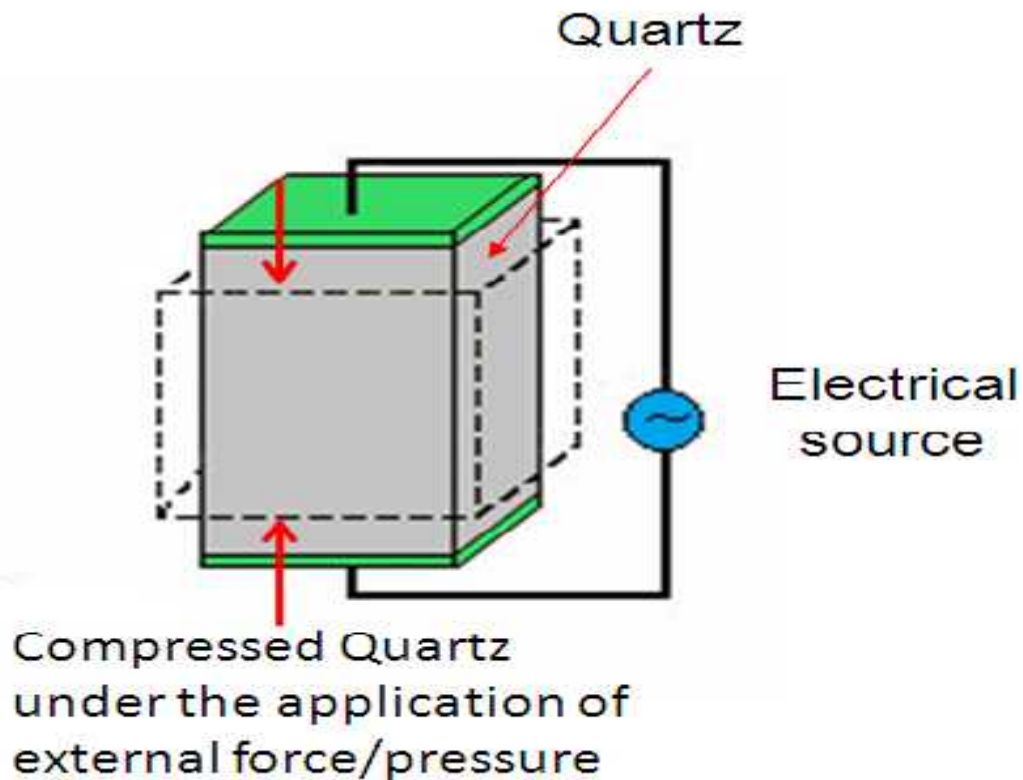
#### 6. Draw and explain Piezo electric transducer in detail.




- Piezoelectric sensor is used for the measurement of pressure, acceleration and dynamic forces such as oscillation, impact, or high speed compression or tension.
- It contains piezoelectric ionic crystal materials such as Quartz. On application of force or pressure these materials get stretched or compressed.
- During this process, the charge over the material changes and redistributes.
- One face of the material becomes positively charged and the other negatively charged. The net charge  $q$  on the surface is proportional to the amount  $x$  by which the charges have been displaced. The displacement is proportion to force. Therefore we can write,

**7. Draw and explain digital storage oscilloscope.**

**DigitalStorageOscilloscope**

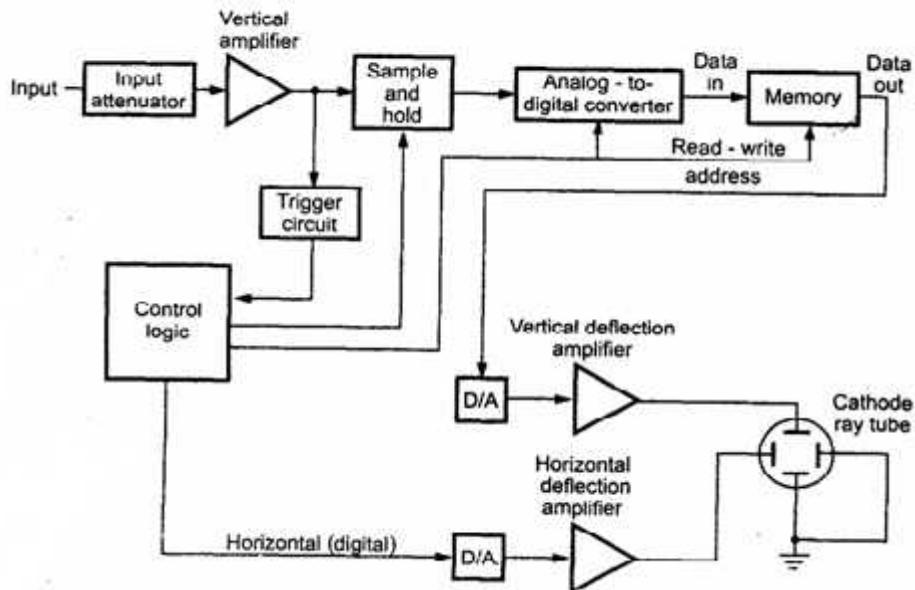**BlockDiagram**

The block diagram of digital storage oscilloscope is shown in the Fig.



- Ø The input signal is applied to the amplifier and attenuator section.
- Ø The oscilloscope uses the same type of amplifier and attenuator circuitry as used in the conventional oscilloscopes.
- Ø The attenuated signal is then applied to the vertical amplifier.
- Ø To digitize the analog signal, an analog-to-digital (A/D) converter is used.
- Ø The output of the vertical amplifier is applied to the A/D converter section.
- Ø The successive approximation type of A/D converter is most often used in the digital storage oscilloscopes.
- Ø The sampling rate and memory size are selected depending upon the duration & the waveform to be recorded.
- Ø Once the input signal is sampled, the A/D converter digitizes it. Ø The signal is then captured in the memory.
- Ø Once it is stored in the memory, many manipulations are possible as memory can be read out without being erased.
- Ø The digital storage oscilloscope has three modes:
  1. Roll mode
  2. Store mode
  3. Hold or save mode.


## Advantages

- i) It is easy to operate and has more capability.
- ii) The storage time is infinite.
- iii) The display flexibility is available. The number of traces that can be stored and recalled depends on the size of the memory.
- iv) The cursor measurement is possible.
- v) The characters can be displayed on screen along with the waveform which can indicate waveform information such as minimum, maximum, frequency, amplitude etc.
- vi) The X-Y plots, B-H curve, P-V diagrams can be displayed.
- vii) The pretrigger viewing feature allows to display the waveform before trigger pulse.
- viii) Keeping the records is possible by transmitting the data to computer system where the further processing is possible.
- ix) Signal processing is possible which includes translating the raw data into finished information e.g. computing parameters of a captured signal like r.m.s. value, energy stored etc.

### **8. Draw and explain CRT display in detail.**

The device which allows, the amplitude of such signals, to be displayed primarily as a function of time, is called cathode ray oscilloscope. The cathode ray tube (CRT) is the heart of the C.R.O. The CRT generates the electron beam, accelerates the beam, deflects the beam and also has a screen where the beam becomes visible as a spot. The main parts of the CRT are

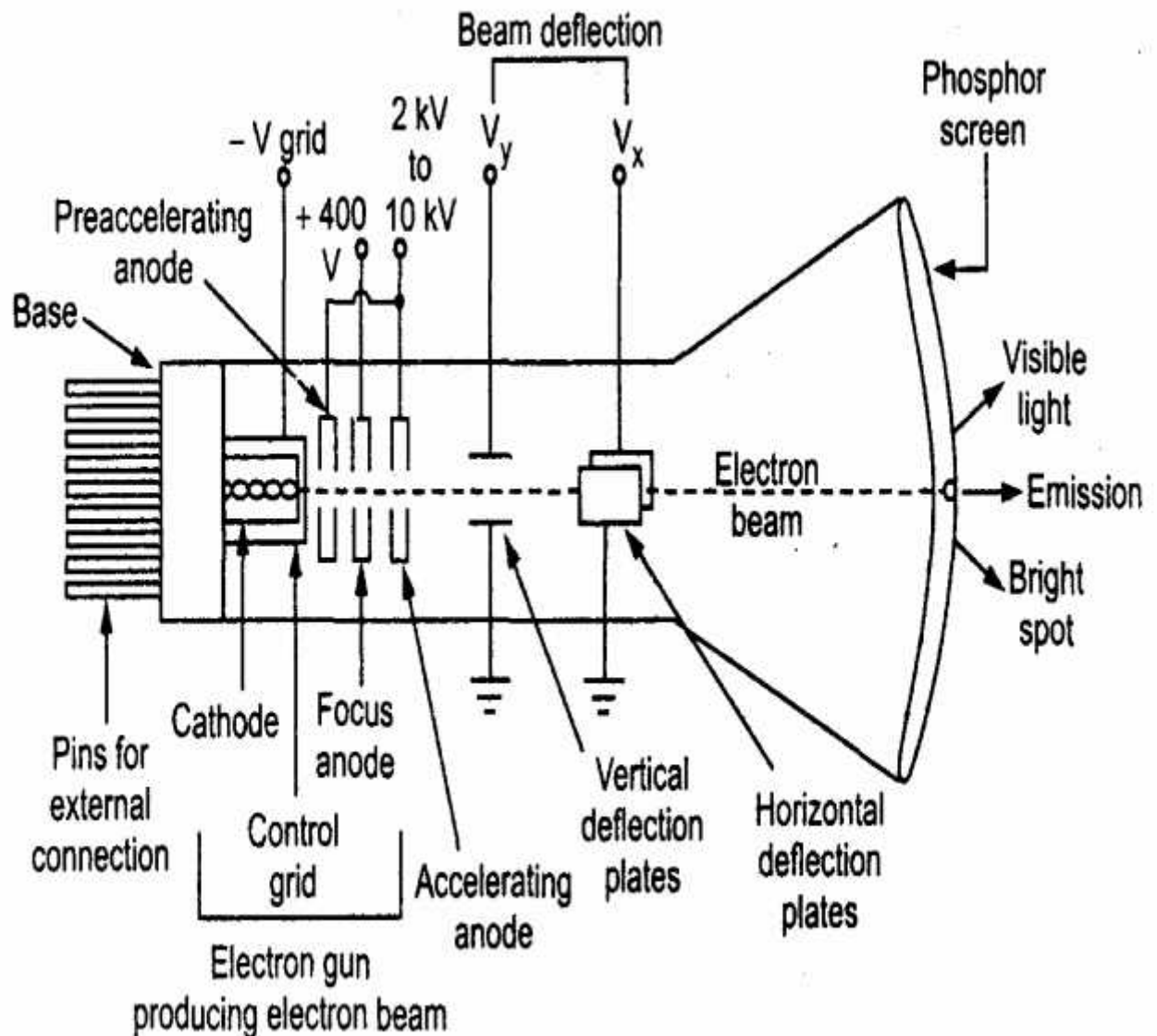- i) Electron gun
- ii) Deflection system
- iii) Fluorescent screen
- iv) Glass tube or envelope
- v) Base



### Electron gun

Ø

The electron gun section of the cathode ray tube provides a sharply focused, electron beam directed towards the fluorescent-coated screen.

Ø This section starts from thermally heated cathode, emitting the electrons. Ø The control grid is given negative potential with respect to cathode.

Ø This grid controls the number of electrons in the beam, going to the screen.

Ø

The momentum of the electrons (their number  $\times$  their speed) determines the intensity, or brightness, of the light emitted from the fluorescent screen due to the electron bombardment.

Ø The light emitted is usually of the green colour.

### **Deflection System**

Ø When the electron beam is accelerated it passes through the deflection system, with which beam can be positioned anywhere on the screen.

### **Fluorescent Screen**

Ø

The light produced by the screen does not disappear immediately when bombardment by electrons ceases, i.e., when the signal becomes zero.

Ø

The time period for which the tracer remains on the screen after the signal becomes zero is known as "persistence or fluorescence".

Ø The persistence may be as short as a

few microseconds, or as long as tens of seconds or even minutes.

Ø Medium persistence traces are mostly used for general purpose applications.

Ø Long persistence traces are used in the study of transients.

Ø

Long persistence helps in the study of transients since the trace is still seen on the screen after the transient has disappeared.

### **Glass Tube**

Ø All the components of a CRT are enclosed in an evacuated glass tube called envelope.

Ø This allows the emitted electron to move about freely from one end of the tube to the other end.

### **Base**

Ø The base is provided to the CRT through which the connections

## **9. Explain in detail about current transformer transformer?**

Instrument Transformers

### **Instrument Transformers**

- It is a transformer that is used in conjunction with any measuring instrument (i.e., Ammeter, Voltmeter, Wattmeter, Watt-hour-meter, ...etc.) or protective equipment (i.e., Relays).
- It utilizes the current-transformation and voltage transformation properties to measure high ac current and voltage.

### **Types of instrument transformers :**

These instrument transformers are of two types:-


1. Current transformers
2. Potential transformers

### **Applications of Instrument Transformers:**

- For measurement of high ac current, it is usual to use low range ac ammeter with suitable shunt.
- For measurement of high ac voltage, low range ac voltmeters are used with high resistances connected in series.
- For measurement of very high ac current and voltage, we cannot use these methods. Instead, we use specially constructed HV instrument transformers to insulate the high voltage circuit from the measuring circuit in order to protect the measuring instruments from burning.
- Application of Instrumentation Transformers In dc circuits for current and voltage measurement, we use low range dc ammeters and voltmeters with rectifiers connected in their secondary circuits.
- The vast primary application of Instrument Transformers is for the protection and control of

power system and power equipment of high and very high ratings.

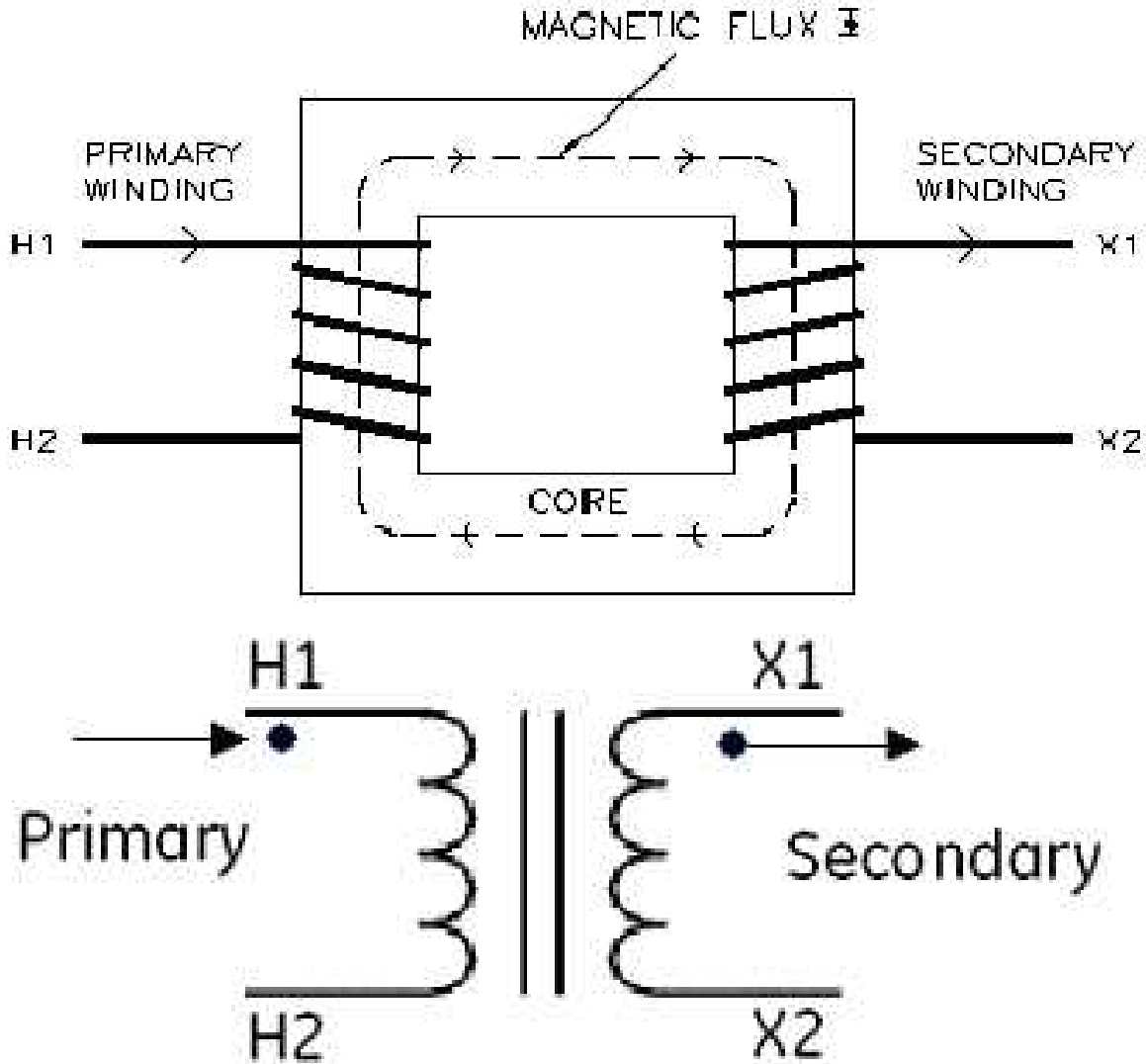- The working of these instrument transformers are similar to those of the ordinary transformers.



### Current Transformers

#### What is current Transformer (CT)

- A current transformer is a transformer, which produces in its secondary winding low current, which is proportional to the high current flowing in its primary winding.
- The secondary current is usually much smaller in magnitude than the primary current.
- The design of CT depends on which type of instrument is connected to its secondary winding.  
**Measuring instrument OR Protective instrument.**

-**Measuring instrument CT** is expected to give accurate results up to a maximum of 125% of its normal full-load rated current.

-**Protective instrument CT** is expected to be accurate for up to 20 times of its normal full-load rated current (about 2000% of its full-load rated current!!..??).

- Based on the type of equipment for which the Ct is used for, its saturation point will vary. At the same time it is expected to be linear in the entire working range.

#### Construction of C.T.:



- C.T. has a primary coil of one or more turns made of thick wire connected in series with the line whose current is to be measured.
- The secondary consists of a large number of turns made of fine wire and is connected across an ammeter or a relay's terminals.



#### **Function of CT:**

- The principal function of a CT is to produce a proportional current at a level of magnitude, which is suitable for the operation of low-range measuring or protective devices such as indicating or recording instruments and relays.
- The primary and secondary currents are expressed as a ratio such as 100/5 or 1000/5 .

With a 100/5 ratio CT, 100A flowing in the primary winding will result in 5A flowing in the secondary winding, provided that the correct rated burden is connected to the secondary winding

#### **10. Explain in detail about potential transformer?**

##### **Potential Transformers:**

##### **What is a Potential Transformer (PT) or (VT)?:**

- A PT or sometimes called VT is a step-down transformer having many primary turns but few secondary turns.
- In a step-down transformer the voltage decreases and the current increases, thus voltage can be easily measured by using a low-range voltmeter instrument.
- The voltage is stepped-down in a known ratio called the voltage ratio.

##### **Construction and working of P.T.:**

##### **Construction**

- A potential transformer has many primary winding turns but few number of secondary winding turns that makes it a step-down transformer.
- A Voltmeter is connected to the secondary winding is usually a voltmeter of 150 V.

##### **Working (Measurement):**

- Primary terminals are connected in parallel across the line to which the voltage is to be measured.
- The voltmeter reading gives the transformed value of the voltage across the secondary terminals.
- The deflection of the voltmeter when divided by the transformed ratio gives the actual voltage across the primary winding as:

The Line voltage = deflection / transformation-Ratio

Where transformation ratio =  $V_2/V_1$

##### **Precaution for P.T.:**

- Since the secondary of a p.t. is connected to relays, their ratings are usually 40 to 100 Watts.

- For safety purpose the secondary should be completely insulated from the high voltage primary and should be in addition grounded.

**Types of P.T. :**

Some types of p.t. are:

- Shell type
- Dry type
- Oil type

- | <u>Rating</u>    | <u>Type</u>           |
|------------------|-----------------------|
| 1. Below 5000 v  | Shell type            |
| 2. 5000-13800 v  | Dry type and oil type |
| 3. Above 13800 v | only oil type         |